


Q1

Set - A

(a)

Saturation: $V_{GS} \geq V_T$, $V_{DS} \geq V_{ov}$:

(b)

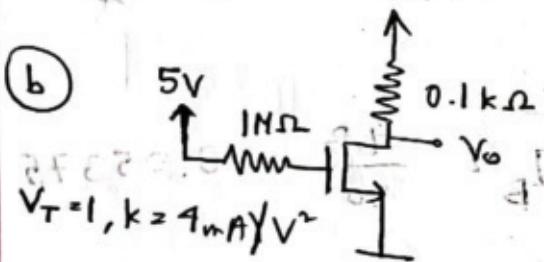

Saturation: $V_G = 5V$, $V_S = 0$, $V_D = x$
 $V_{GS} = 5V$
 $V_{ov} = 5 - 1 = 4V$

$$I_D = \frac{1}{2}(V_{ov})^2 = 2 \times 16 = 32 \text{ mA}$$


$$V_{D2} = 10 - 0.1I_D = 10 - 3.2$$

$$\rightarrow V_O = 6.8V > 5V$$

Thus, input HIGH gives output HIGH.

(c) As the ckt is malfunctioning, Nirmol was correct

(d)

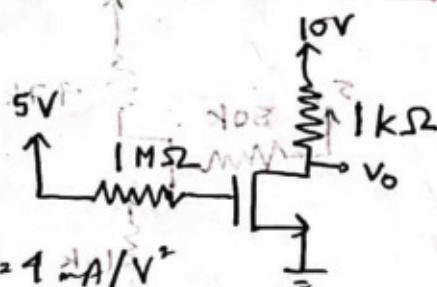

$$V_T = 1, k = 1 \text{ mA/V}^2$$

Saturation: $V_G = 5V$, $V_S = 0$, $V_D = x$

$$V_{DS} = x, V_{GS} = 5V, V_{ov} = 4V$$

$$I_D = \frac{1}{2}V_{ov}^2 = \frac{1}{2}(4)^2 = 8 \text{ mA}$$

$$I_D = \frac{k}{2}V_{ov}^2 = \frac{1}{2} \times 16 = 8 \text{ mA}$$

$$V_O = 10 - 8 = 2 \text{ V}$$

Triode:

$$I_D = \frac{1}{2}[V_{DS}V_{ov} - \frac{1}{2}V_{DS}^2]$$

$$I_D = \frac{10 - V_{D2}}{1} = \frac{10 - x}{1}$$

$$\therefore 10 - x = 16x - 2x^2 \quad \text{if } V_{DS} > V_{ov}$$

$$\Rightarrow 2x^2 - 17x + 10 = 0 \Rightarrow x = 7.861V$$

$$\therefore V_{out} = 0.636V < 5V$$

$$\therefore \text{output} = \text{LOW}$$

So, it's working properly after modification.

$$V_{DS} = V_D = V_{ov} = 1V$$

$$I_D = \frac{10 - 1}{R_D} = \frac{9}{R_D} = \frac{k}{2}V_{ov}$$

$$\therefore \frac{10 - 1}{(\frac{1}{2}) \cdot 1} = R_D \Rightarrow R_D = \frac{18}{0.5} = 36 \text{ k}\Omega$$


Q1

Set B

$$V_{GS} = 5V - 0.75V = 4.25V$$

Saturation: $\frac{i_L}{i_b} < \beta$

(b)

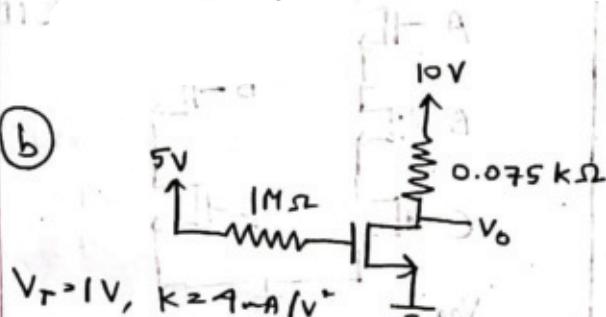

$$V_T = 1V, k = 1mA/V^2$$

$$\therefore V_G = 5V, V_S = 0V, V_D = x$$

$$V_{GS} = 5V, V_{ov} = 4V$$

Saturation: $I_D = \frac{1}{2}(1)^2$

$$= 32mA$$


$$V_o = 10 - 0.075 I_D = 7.6V > 5V$$

Input HIGH \rightarrow Output HIGH

Statement verified

Nirmol was correct

(c)

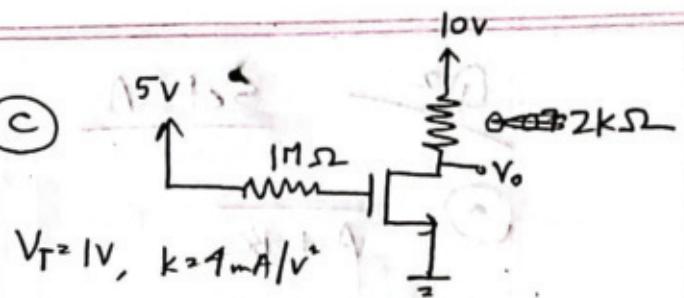

$$V_T = 1V, k = 1mA/V^2$$

$$V_G = 5V, V_S = 0V, V_D = x$$

$$V_{GS} = 5V, V_{ov} = 4V, V_{DS} = x$$

Saturation: $I_D = \frac{1}{2}(1)^2 = 32mA$

$$V_o = 10 - 2I_D = 5.4V$$

Triode:

$$I_D = 4 \left[4x - \frac{1}{2}x^2 \right]$$

Also, $I_D = \frac{10-x}{2}$

$$\frac{10-x}{2} = 4 \left[4x - \frac{1}{2}x^2 \right]$$

$$\Rightarrow 10-x = 32x - 4x^2$$

$$\Rightarrow 4x^2 - 33x + 10 = 0$$

$$\Rightarrow x = 7.935V \quad [V_{DS} > V_{ov}]$$

or,

$$0.315V$$

$$\therefore V_{out} = 0.315V < 5V \equiv \text{LOW}$$

So, the ckt is working properly after the modification

(d) $V_{DS} = V_D = V_{ov} = 4V$

$$I_D \cdot \frac{10-1}{R_D} = \frac{1}{2}(1)^2$$

$$\Rightarrow R_D = 0.1875 k\Omega$$


Q3

Set A

a

A.(B+C) + D.E

b

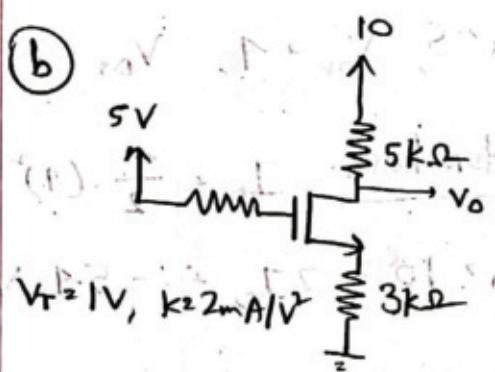

$$V_T = 1V, k = 2mA/V$$

$$V_G = 5V, V_D = 0, V_S = 0V$$

$$I_D = \frac{10-y}{5} = \frac{y-0}{3}, V_{GS} = 5-y$$

$$\Rightarrow y = 10 - \frac{5}{3}x, V_{OV} = 1-x$$

Saturation:

$$I_D = \frac{k}{2} V_{OV}^2$$

$$\Rightarrow \frac{y-0}{3} = \frac{k}{2} \times \frac{1}{2} \times (1-x)^2$$

$$\Rightarrow x = 3(16 - 8x + x^2)$$

$$\Rightarrow 3x^2 - 25x + 48 = 0$$

$$\Rightarrow x = 5.33V, 3V$$

$$V_{GS} = 5 - 5.33 = -0.33$$

$$V_{GS} = 5 - 3 = 2V$$

$$V_{OV} = 1V$$




$$V_{DS} = 10 - \frac{5}{3} \times 3 = 5V$$

$$V_D = 10 - \frac{5}{3} \times 3 = 5V$$

$$V_{OS} = V_D - V_S = 5 - 3 = 2V$$

$$V_{DS} > V_{OV}$$

c i

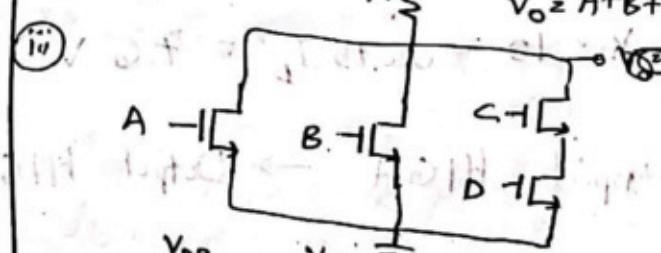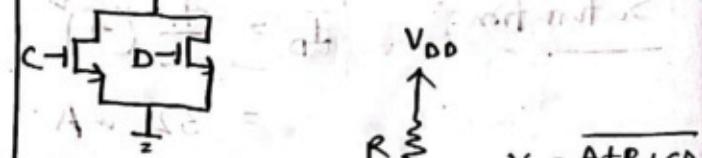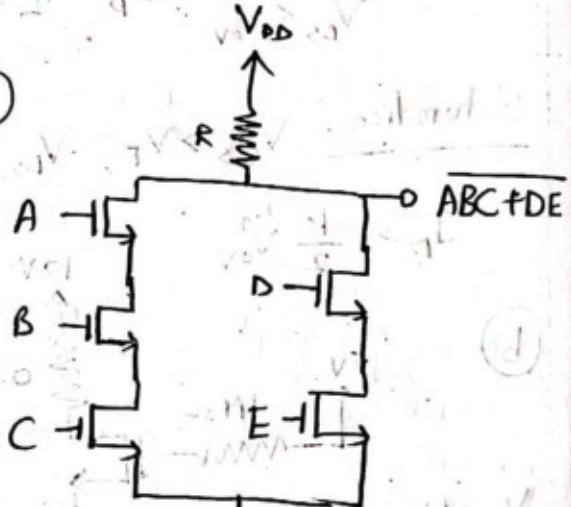


G³

Set B

$$\sqrt{1 - \alpha_0^2} = \sqrt{1 - \alpha^2} = \sqrt{1 - \alpha^2}$$

$$\overline{AB} + C(D+E)$$

b

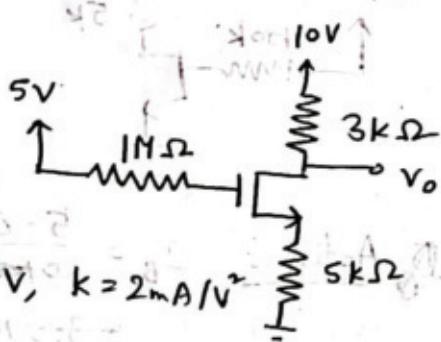

$$V_T = 1 \text{ V}, \quad k = 2 \text{ mA/V}^2 \quad 5 \text{ k}\Omega$$

$$V_G = 5V, V_D = y, V_S = x$$

$$V_{GS} = 5 - x, \quad V_{ov} = 4 - x$$

$$\underline{\text{Saturation:}} \quad I_D = \frac{2}{2} \times (1-x)^2$$

$$\frac{x-0}{5} = 1 \times \textcircled{2} (16 - 8x + x^2)$$

$$\Rightarrow x = 80 - 10x + 5x^2$$

$$5x^2 - 41x + 80 = 0$$

$$\therefore x = 5V, 3.2V$$

$$\begin{array}{l}
 V_{GS} = 5 - 5 \xrightarrow{\text{X}} \\
 \Rightarrow 0 < V_T \\
 \hline
 V_{GS} = 5 - 3.2 = 1.8V \\
 V_{GS} > V_T \xleftarrow{\text{---}} \\
 V_D = 10 - \frac{3}{5} \times 3.2 = 8.08V \\
 V_{DS} = 8.08 - 3.2 = 4.88V
 \end{array}$$

A + 2


$$V_{ova} = 4 - 3.2 = 0.8 \text{ V}$$

$$\therefore V_{DS} > V_{OV}$$


W.

[Saturation verified]


6

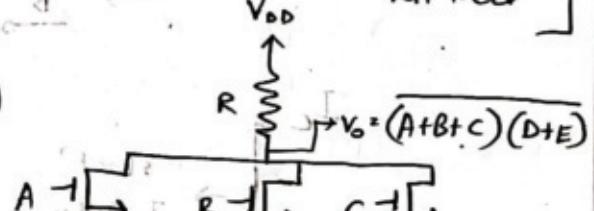


12

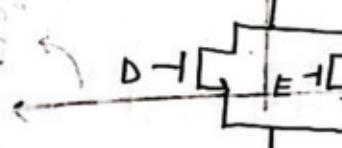


ii

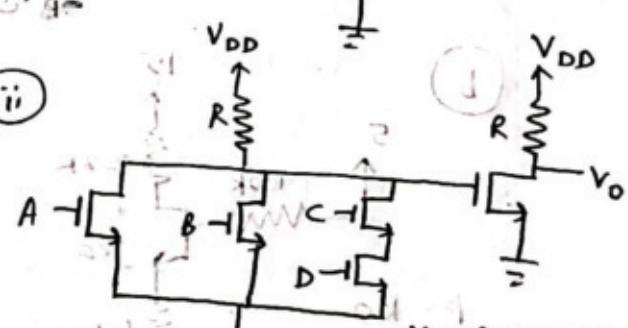

iii


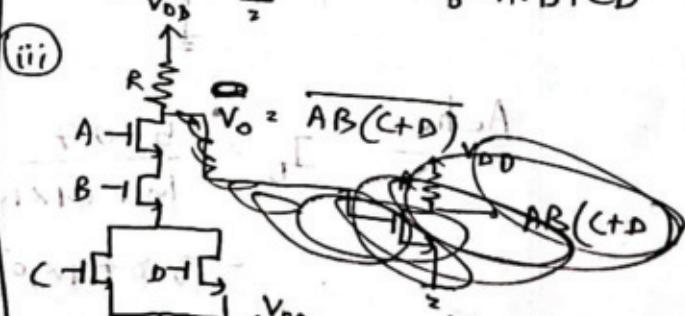


iv

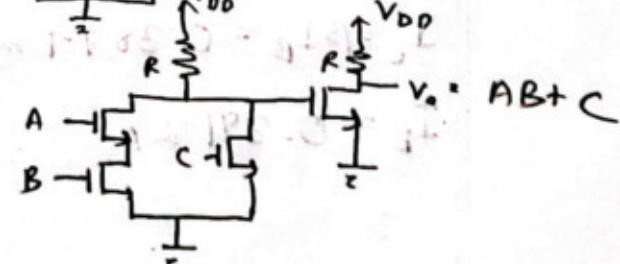

Q2

Set A

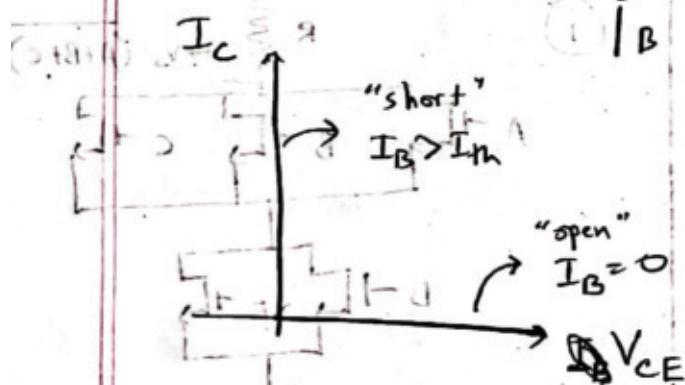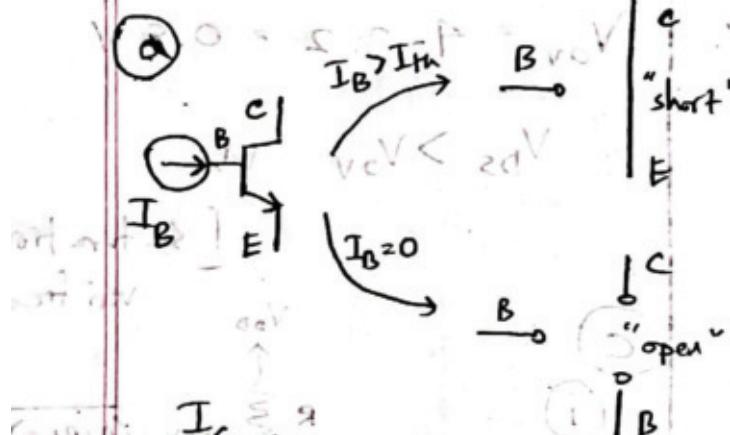

Active:


$$I_B = \frac{5 - 0.7}{100 + 101 \times 10} = 3.879 \times 10^{-3} \text{ mA}$$

$$I_C = \beta I_B = 0.3879 \text{ mA}$$

$$I_E = 0.391 \text{ mA}$$

$$V_{CE} = 15 - 2.2I_C - 10I_E$$

$$= 10.235 > 0.2$$

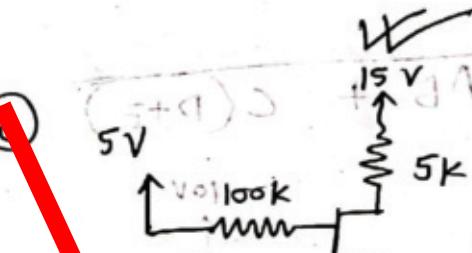

Active:

$$I_B = \frac{5 - 0.7}{100 + 101 \times 10} = 3.879 \times 10^{-3} \text{ mA}$$

$$I_C = 4.3 \text{ mA}$$

$$V_{CE} = 15 - 5I_C = 6.5 \text{ V}$$

∴ Saturation

Saturation:

$$I_B = \frac{5 - 0.8}{100} = 0.042 \text{ mA}$$

$$I_C = \frac{15 - 0.2}{5} = 2.96 \text{ mA}$$

$$\frac{I_C}{I_B} = 70.476 < \beta$$

$$I_E = 3.002 \text{ mA}$$

2c ==> Wrong solution.
Correct solution is in the next page.

Set A

2c) Assume Q_2 is active,

$$V_{BE} = 0.7V$$

$$V_E = 0V$$

$$5 - I_B(100) - 0.7 = 0$$

$$\therefore I_B = 0.043 \text{ mA}$$

$$I_C = \beta I_B = 100 \times 0.043 = 4.3 \text{ mA}$$

$$I_C = \frac{V_{CC} - V_C}{R_C}$$

$$\Rightarrow 4.3 \text{ mA} = \frac{15 - V_C}{2.2k\Omega}$$

$$\therefore V_C = 5.54V$$

$$V_{CE} = 5.54V$$

$$V_{CE} > 0.2V$$

$$\Rightarrow 5.54V > 0.2V$$

Q_2 is in active mode

Rahim was correct.

Set B

Q2

(a) Same as set A

(b) Active:

$$I_B = 3.795 \times 10^{-3} \text{ mA}$$

$$I_C = 0.3945 \text{ mA}$$

$$I_E = 0.398 \text{ mA}$$

$$V_{CE} = 9.16 > 0.2 \text{ V}$$

[same as set A]

(c) Active:

$$I_B = 0.05375 \text{ mA}$$

$$I_C = 375$$

$$V_{CE} = 15 - 3.75 = -1.125$$

∴ Must be
saturation

Saturation:

$$I_B = 0.0525 \text{ mA}$$

$$I_C = 2.96 \text{ mA}$$

$$I_E = 0.0125 \text{ mA}$$

$$\frac{I_C}{I_B} = 56.38 < 100$$

2c ==> Wrong solution.
Correct solution is in
the next page.

Set B

THE

2c) Assume active mode,

$$V_{BE} = 0.7V$$

$$5 - 80I_B - V_{BE} = 0$$

$$\therefore I_B = 0.05375 \text{ mA}$$

$$I_C = \beta I_B = 100 \times 0.05375 = 5.375 \text{ mA}$$

$$I_C = \frac{V_{CC} - V_C}{R_C}$$

$$\Rightarrow 5.375 = \frac{15 - V_C}{3k}$$

$$\therefore V_C = -1.125$$

$V_{CE} < 0.2$, so not active.

Assume saturation,

$$5 - 80I_B - 0.8 = 0$$

$$\therefore I_B = 0.0525 \text{ mA}$$

$$V_{CE} = 0.2V = V_C$$


$$I_C = \frac{15 - 0.2}{3} = 4.93 \text{ mA}$$

$$I_E = I_B + I_C = 4.9825 \text{ mA}$$

$$\frac{I_C}{I_B} = \frac{4.93}{0.0525} = 93.904 < \beta$$

So, in saturation mode.

Set-A saturation Question-04

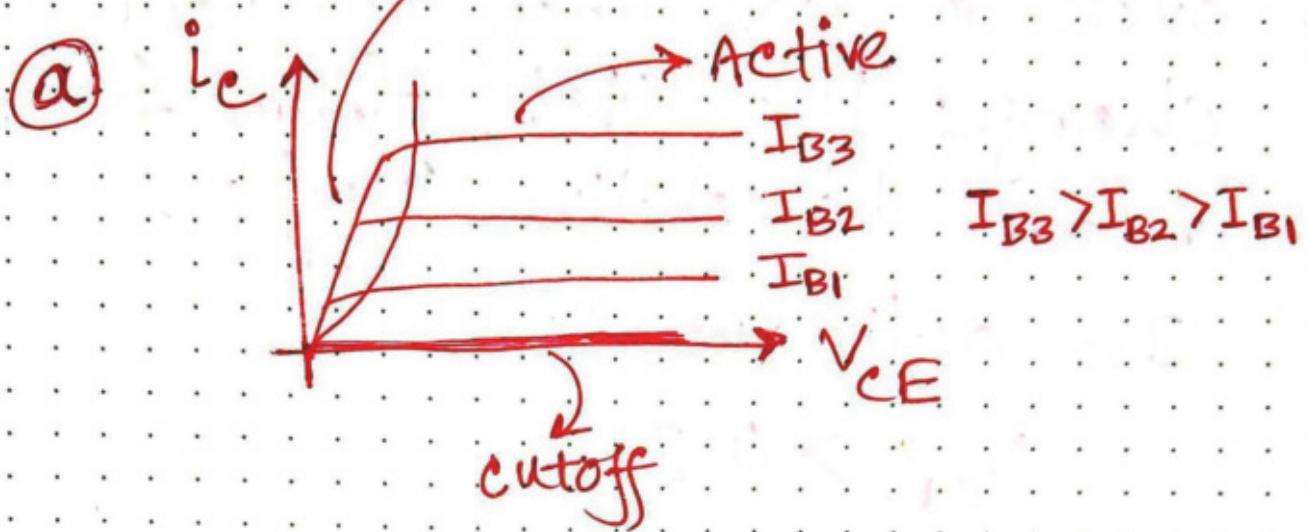

② $I_B = 0.04 \text{ mA}$ Sat. Mode

$$5 - R_C I_C - V_{CE} - R_E I_E = 0$$

$$\hookrightarrow 5 - (1\text{K}) I_C - 0.2 - (1\text{K}) (I_B + I_C) = 0$$

$$\hookrightarrow I_C = 2.38 \text{ mA.}$$

$$\therefore I_E = (0.04 + 2.38) \text{ mA} = 2.42 \text{ mA}$$

Verification $59.5 < 90 \rightarrow \text{True.}$

$$\frac{I_C}{I_B} < \beta$$

$$\hookrightarrow \frac{2.38}{0.04} < 90$$

$$\left. \begin{array}{l} I_B = 0.04 \text{ mA} \\ I_C = 2.38 \text{ mA} \\ I_E = 2.42 \text{ mA} \\ V_{CE} = 0.2 \text{ V} \end{array} \right\}$$

c) We need to change V_{ce} in such a way that the BJT changes its state from Sat. mode to Active Mode.

In active mode,

$$V_{ce} > 0.2$$

Applying KVL we get,

$$V_{ce} - R_c I_c - V_{ce} - I_E R_E = 0$$

$$\hookrightarrow V_{ce} = V_{cc} - R_c I_c - R_E I_E$$

We need to make sure that,

$$V_{cc} - I_c R_c - I_E R_E > 0.2$$

$$\hookrightarrow V_{cc} > I_c R_c + I_E R_E + 0.2$$

In active mode,

$$I_c = \beta I_B$$

$$\text{So, } V_{ce} > \beta I_B R_c + (I_c + I_B) R_E + 0.2$$
$$\rightarrow V_{ce} > \beta I_B R_c + (\beta I_B + I_B) R_E + 0.2$$


$$\rightarrow V_{cc} > 90 \times 0.04 \times 1 + (90 \times 0.04) \times 1 + 0.04$$

$$+ 0.2$$

$$\rightarrow V_{cc} > 7.44$$

So, we need to increase V_{cc} from 5V to more than 7.44V in order to change the operating state of the BJT from Sat. mode to active mode.

d

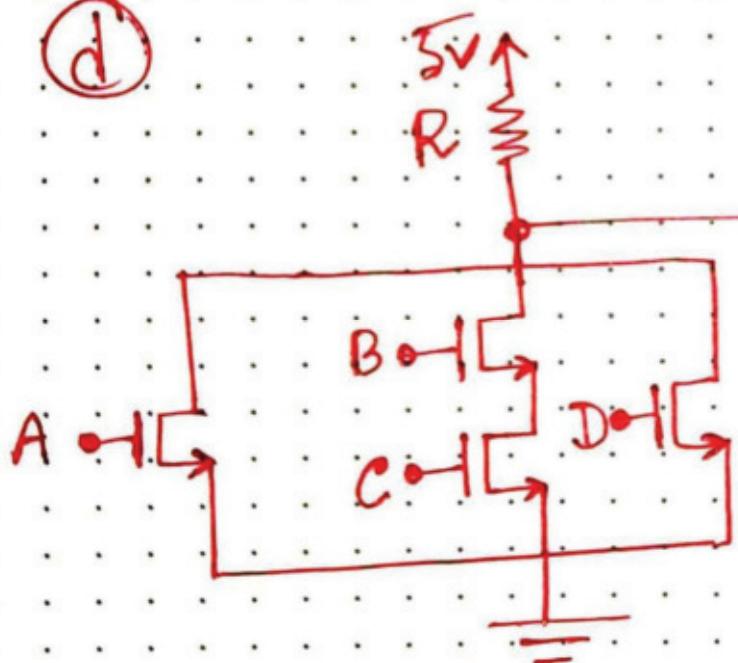


$$f = \overline{A + B \cdot C + D}$$

I mistakenly drew this logic ckt using MOSFETs instead of BJTs.

The correct ckt will look similar to this one. Each MOSFET will be replaced by a BJT with a resistor in the Base Terminal.

Set-B

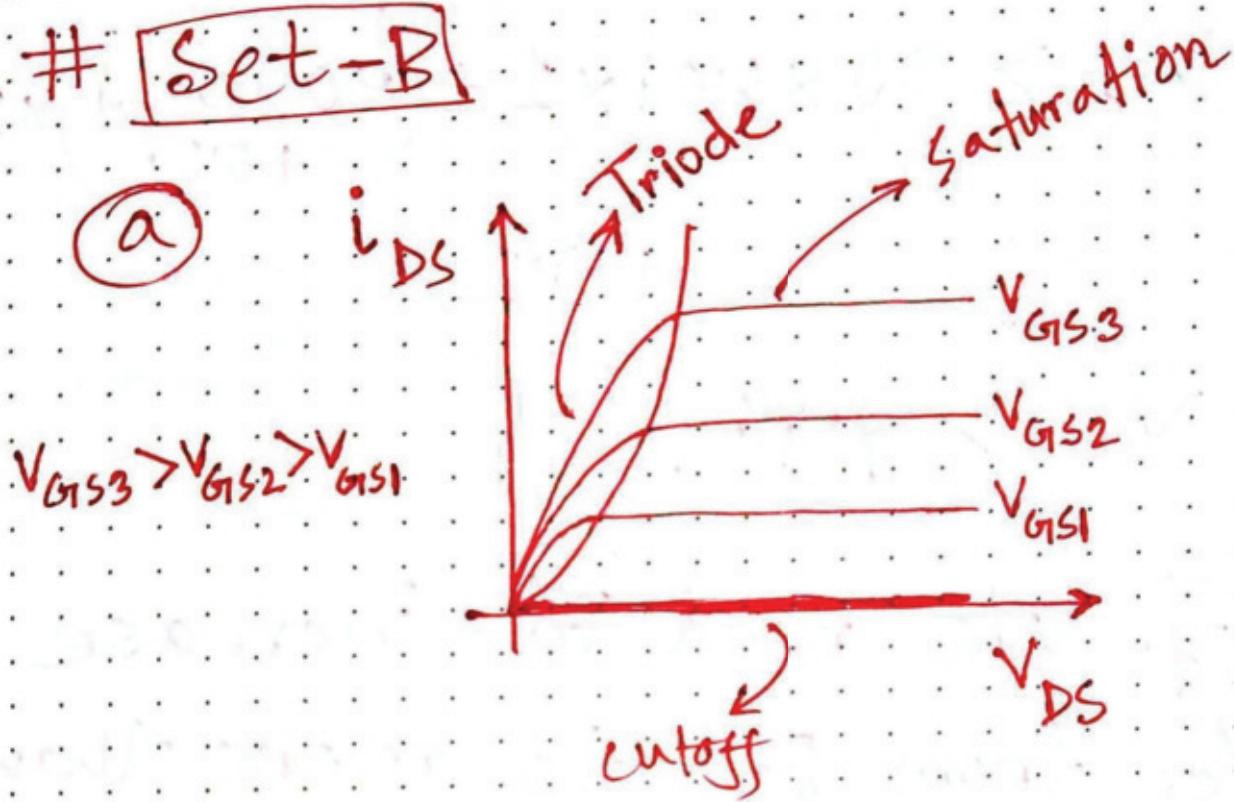

(b) Sat. Mode

$$I_B = 0.05 \text{ mA}$$

~~$$I_C = 2.375 \text{ mA}$$~~

$$I_E = 2.425 \text{ mA}$$

$$V_{CE} = 0.2 \text{ V}$$

Verification


$$\frac{I_C}{I_B} < \beta$$

$$47.5 < 110 \rightarrow \text{True}$$

③ Procedure \rightarrow Similar to Set-A.

$$V_{ce} > 11.25 \text{ V.}$$

④

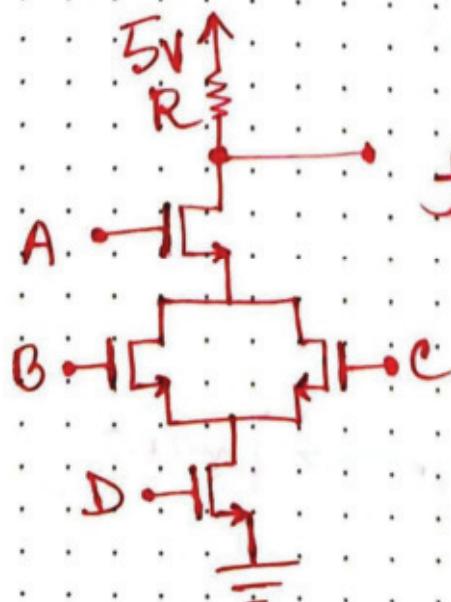

I mistakenly drew this logic ckt using MOSFETs instead of BJTs.

The correct ckt will look similar to this one. Each MOSFET will be replaced by a BJT with a resistor in the Base Terminal.