


Alternate ckt diagram or line representation helps us to draw ckt in a compact form. Plus in IRL designs, this type of representation is more preferred.

To change a regular ckt representation to line representation —

### Steps

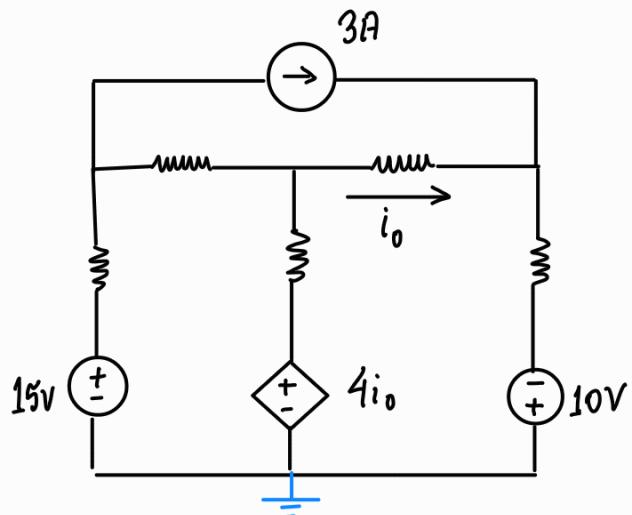
0. Place a ground in the ckt. Ignore this step if a ground is already present.

To select the ground node just follow the rule of thumbs introduced in nodal analysis during your 250 course




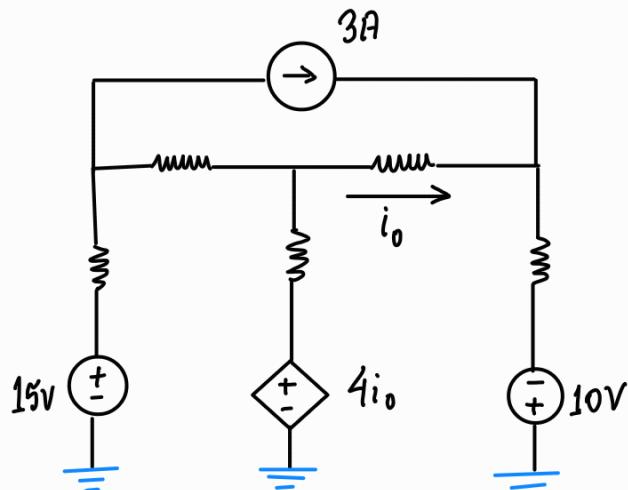1. Separate the grounded points.


Note that these points are still the same nodes



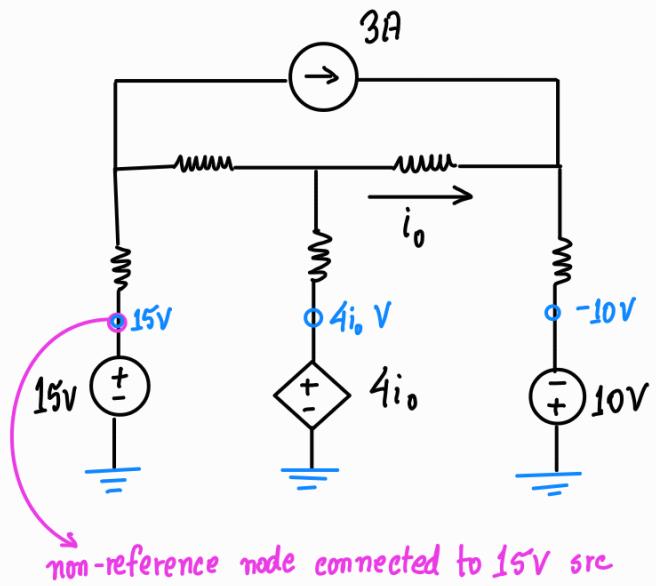
2. Replace all the voltage srcs connected to the ground ( $\text{---} + \text{---} \parallel$ ,  $\text{---} \text{---} \parallel$ ,  $\text{---} \diamond \text{---} \parallel$ ) with an arrow ( $\rightarrow$ ) or just a dot ( $\text{---} \bullet \text{---}$ ). Assign the node voltage at the non-reference node connected with these srcs to the arrow or the dot.



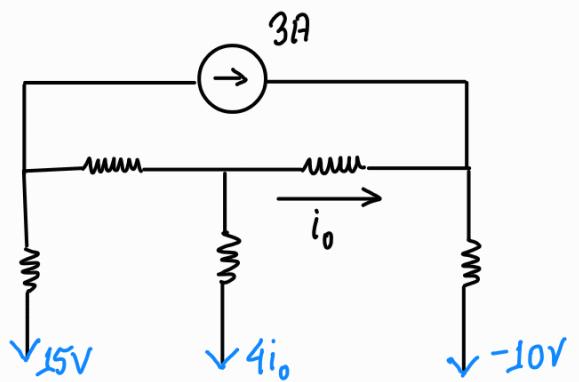
Note — You cannot convert current srcs; neither can you convert non-grounded voltage srcs. So keep them as they are.



One exception —

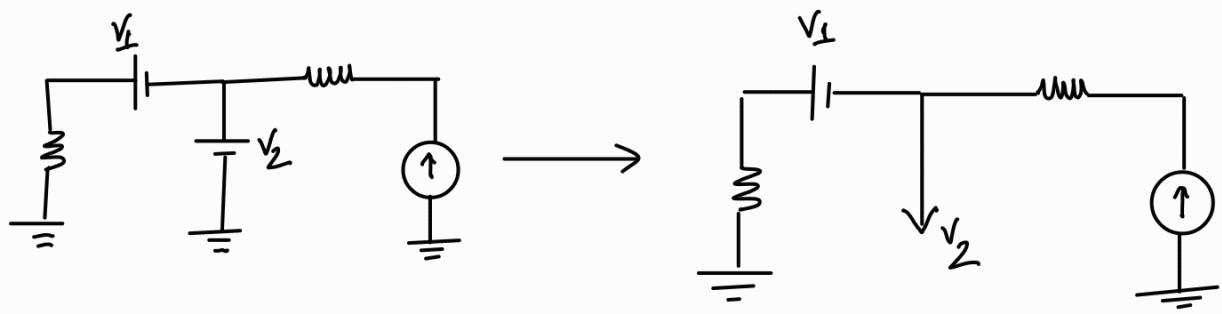

a bit of rearranging

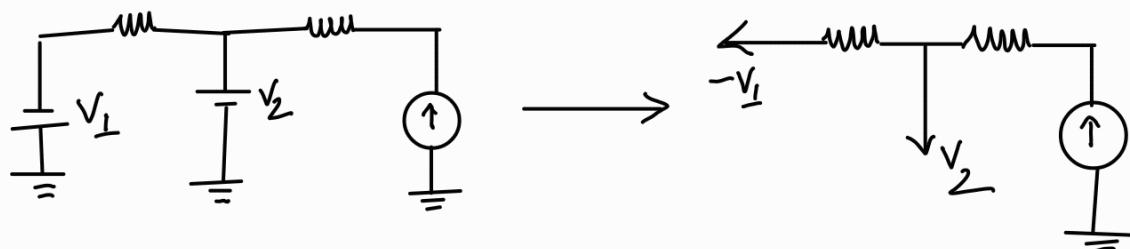


Sometimes a bit of ckt re-arrangement can allow to further simplify the ckt in alternate representation.


Should you do it? → Its upto you. Its fine even if you don't do it.

Nodal recap —

# Find all node voltages in the ckt —

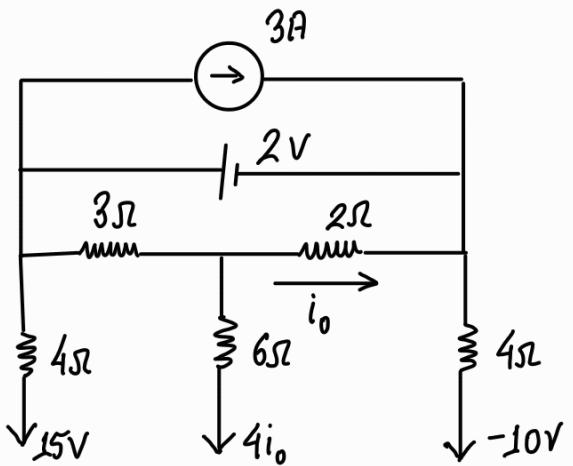

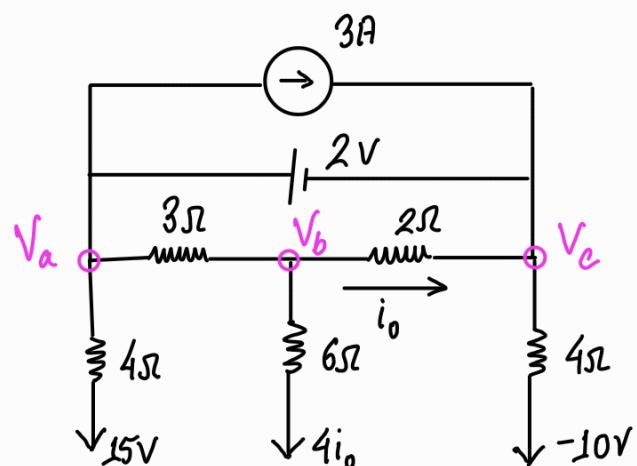1. Place voltage variables at all essential nodes with unknown node voltages



2. Write KCL equations for all the marked nodes and supernodes. Supernodes will also give you voltage relationship equations —

Voltage relationship equation @ SN a,c —

$$V_a - V_c = 2 \quad \text{--- (i)}$$

KCL @ SN a,c —

$$\frac{V_a - 15}{4} + \frac{V_a - V_b}{3} + \frac{V_c - V_b}{2} + \frac{V_c - (-10)}{1} = 0 \quad \text{[3A src shorted between the SN]}$$

$$\Rightarrow V_a(4^{-1} + 3^{-1}) - V_b(3^{-1} + 2^{-1}) + V_c(2^{-1} + 1^{-1}) = \frac{15}{4} - \frac{10}{4} \quad \text{--- (ii)}$$

KCL @ b —

$$\frac{V_b - V_a}{3} + \frac{V_b - 4i_o}{6} + \frac{V_b - V_c}{2} = 0$$

in the ckt  $i_o = \frac{V_b - V_c}{2}$

$$\therefore \frac{V_b - V_a}{3} + \frac{V_b - 4i_o}{6} + \frac{V_b - V_c}{2} = 0 \Rightarrow \frac{V_b - V_a}{3} + \frac{V_b - 2V_b + 2V_c}{6} + \frac{V_b - V_c}{2} = 0$$

(iii)

$$\Rightarrow -V_a(3^{-1}) + V_b(3^{-1} - 6^{-1} + 2^{-1}) - V_c(-3^{-1} + 2^{-1}) = 0$$


③ Solve the equations to get the values of  $V_a, V_b$  &  $V_c$

Some key points —

- ① If current enters the node  $\rightarrow$  -ve term  
current leaves the node  $\rightarrow$  +ve term
- ② for resistive branches, always consider outward current
- ③ Always replace extra variables in terms of node variables.

Voltage divider —

for any series string of resistances —

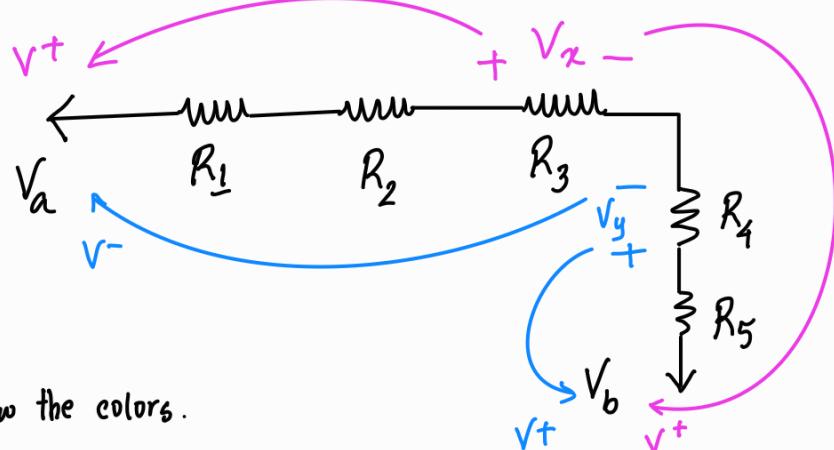

follow the colors.


$$V_x = \frac{R_3}{\sum R} \times (V^+ - V^-)$$

$$= \frac{R_3}{\sum R} (V_a - V_b)$$


$$V_y = \frac{R_4}{\sum R} (V^+ - V^-)$$

$$= \frac{R_4}{\sum R} (V_b - V_a)$$

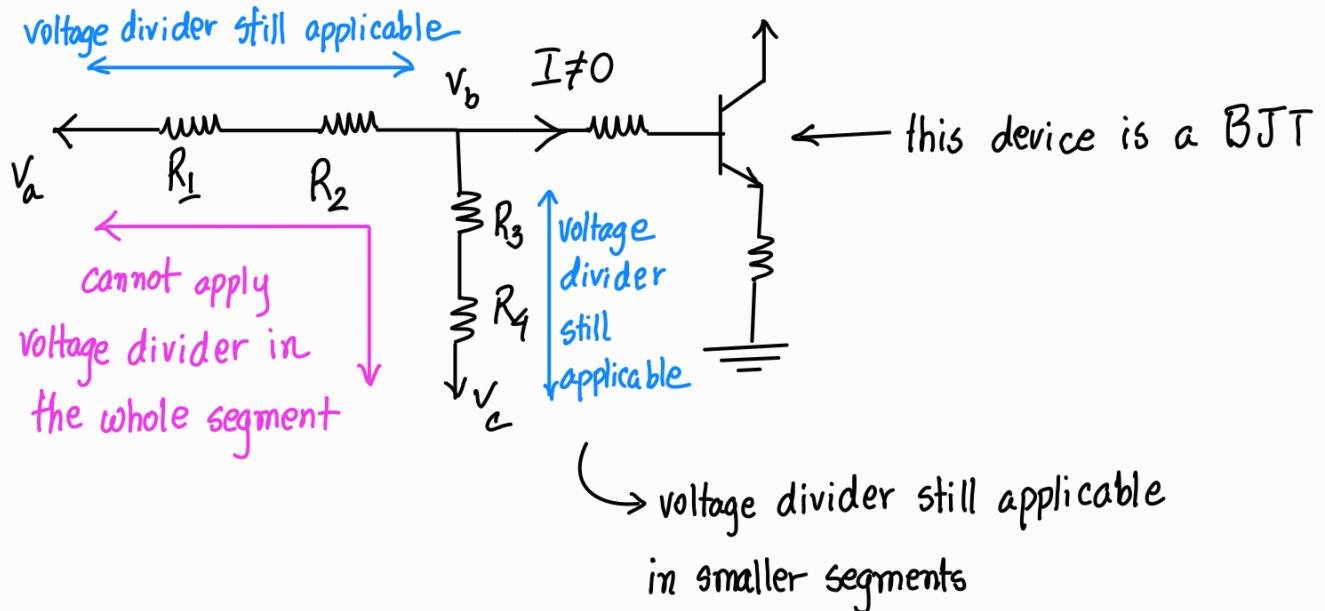
In case there is a branch connected to the string of resistors like this —



However for certain devices —

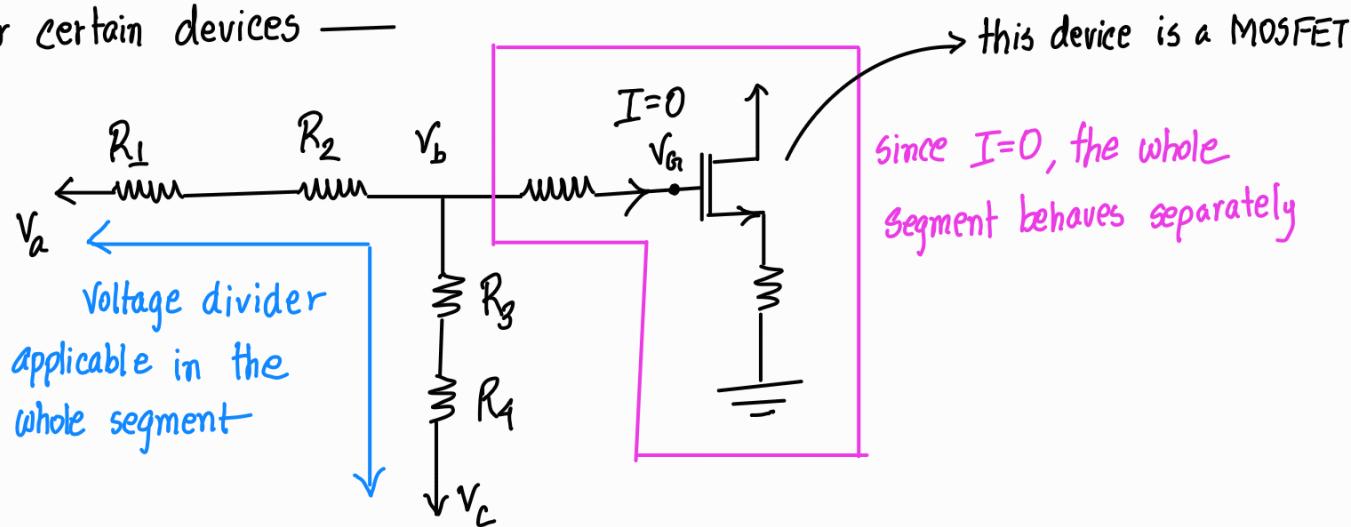

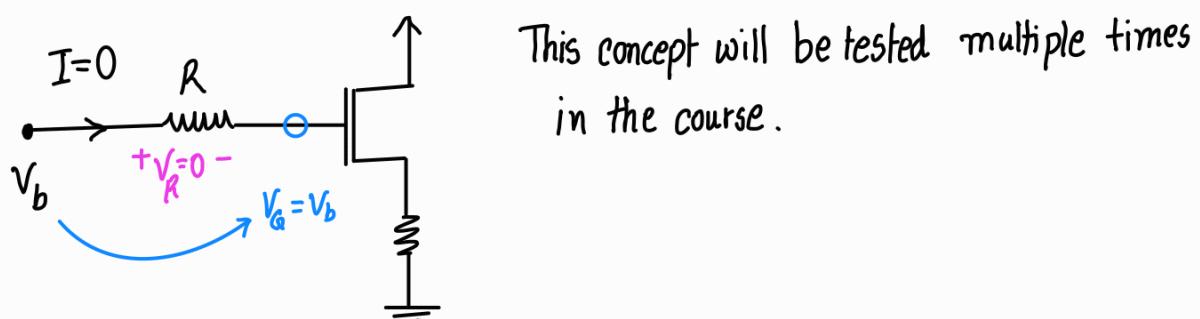
Since  $I=0$  in the connecting branch, the node voltage  $V_b$  can be transferred inward —



KVL in a line —

While voltage divider will help you out in some of the tricky case. KVL will remain a staple in the harder (read lengthy) but straight-forward problems.

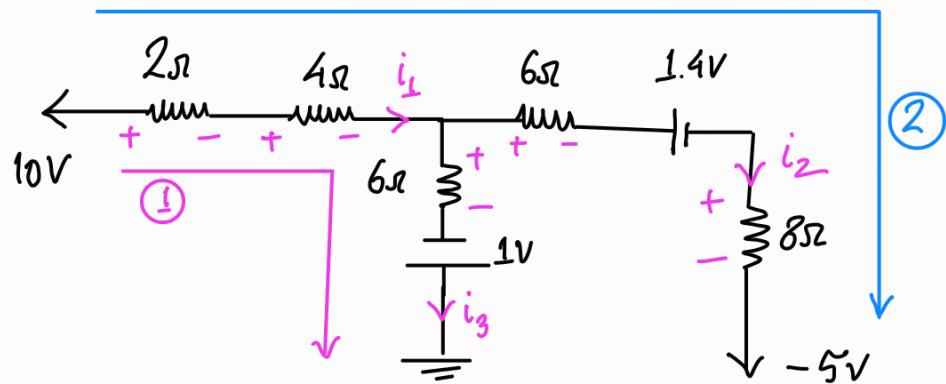Unlike 250 where we applied KVL in a loop, we will apply KVL in lines for 251.



KVL in (1) —

polarity placed following passive sign convention.

$$2i_1 + 4i_1 + 6i_3 - 1 = V_{\text{start}} - V_{\text{end}}$$

$$\Rightarrow 6i_1 + 6i_3 = 10 - 0 + 1 \Rightarrow 6i_1 + 6i_3 = 11$$


KVL in (2) —

$$2i_1 + 4i_1 + 6i_2 + 1.4 + 8i_2 = V_{\text{start}} - V_{\text{end}}$$

$$\Rightarrow 6i_1 + 14i_2 = 10 - (-5) - 1.4 \Rightarrow 6i_1 + 14i_2 = 13.6$$

KVL in line is more flexible than regular KVL. Lets take the above example and update line 2.

We can update the span of KVL freely

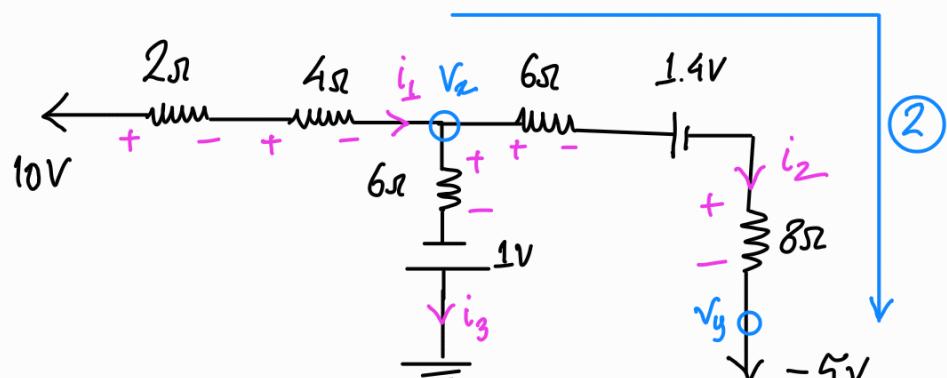

KVL in line 2 starting from node  $x$  to  $y$  —

optionally you can specify the range  $\rightarrow$  I generally do it.

Going ahead most ckts will have named nodes, so you will not have to name them all

$$6i_2 + 1.4 + 8i_2 = V_{\text{start}} - V_{\text{end}}$$


$$\Rightarrow 14i_2 = V_x + 5 - 1.4 \Rightarrow 14i_2 = V_x + 3.6$$

Some extra note —


Why do we need alternate representation?

Let me present a small logic function implemented with ckt —
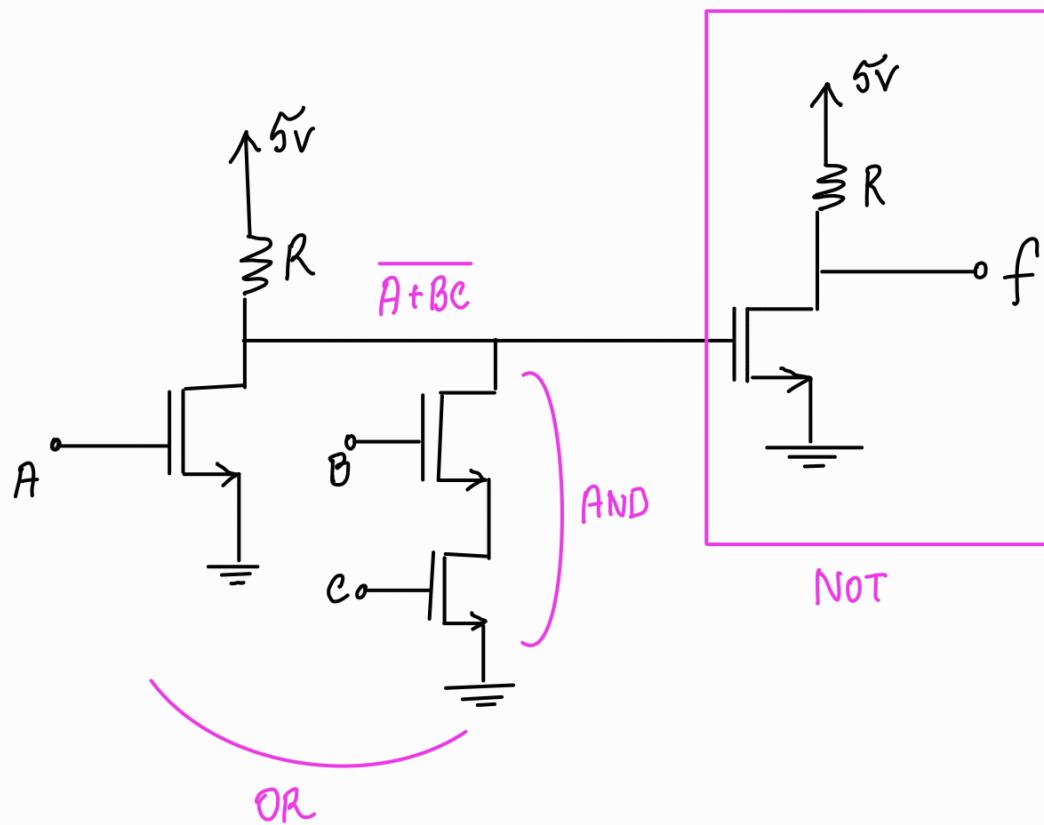
$$f = A + BC \quad [A \text{ OR } (B \text{ AND } C)]$$



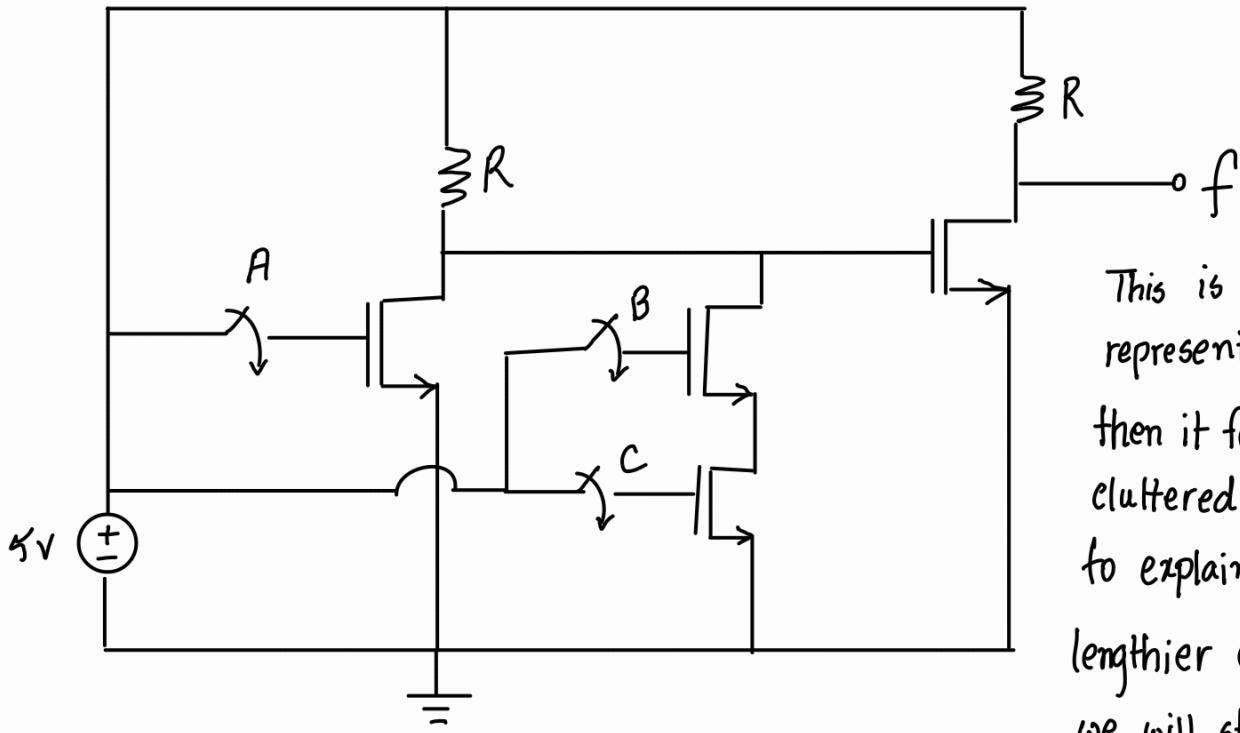
If you want to convert it to 250's representation it will look something like this —



This is a very optimized representation and even then it feels a bit cluttered and is harder to explain. You can try lengthier ckt (later when we will study them) and you will appreciate line representation more.

One last note — I personally treat all 251 ckt's like puzzles and generally try to solve them by node hopping, a bit of Ohm's law and a bit of KVL but I do realize most people find nodal analysis to be easier. I would suggest you to find your own comfort zone. I have left all the assignment problems open-ended except Q1, so feel free to go ham. If you are struggling with any of the maths, you can always consult me.
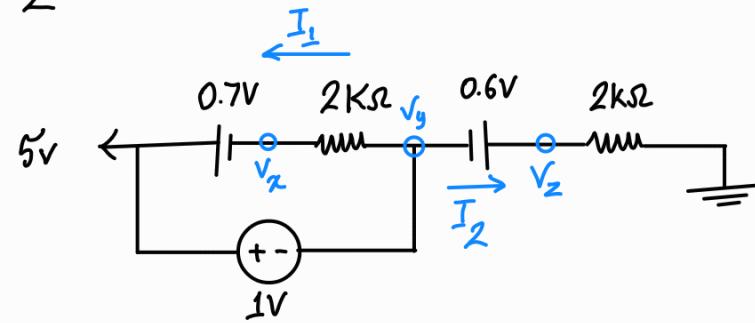
# For the given ckt, find  $V_x, V_y, V_z, I_1$  &  $I_2$  —




$$\textcircled{1} \rightarrow V_y = 5 - 1 = 4V$$

$$\textcircled{2} \rightarrow V_x = 5 - 0.7 = 4.3V$$

$$\textcircled{3} \rightarrow V_z = V_y + 0.6 = 4.6V$$

$$I_1 = \frac{V_y - V_x}{2} = \frac{4 - 4.3}{2} = -0.15mA$$

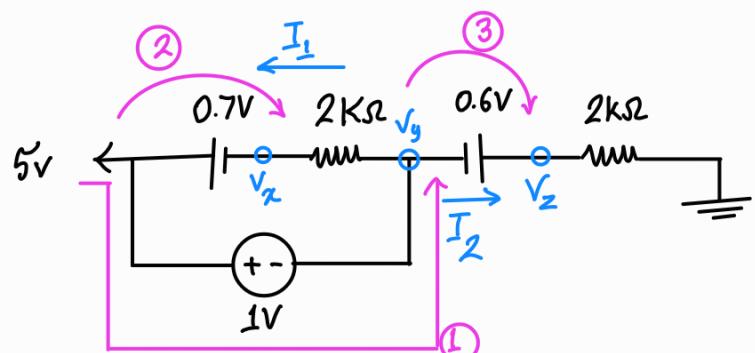
$$I_2 = \frac{V_z - 0}{2} = \frac{4.6}{2} = 2.3mA$$



the arrows represent node voltage transfer paths

You do NOT have to show the paths  
I am showing them for you to understand
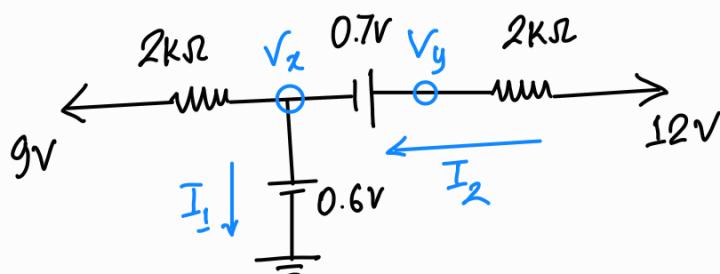
# For the following ckt find  $V_x, V_y, I_1$  &  $I_2$  —




$$\textcircled{1} \quad V_x = 0.6V$$

$$\textcircled{2} \quad V_y = V_x + 0.7 = 1.3V$$



$$I_x = \frac{9 - V_x}{2} = \frac{8.4}{2} = 4.2mA$$

$$I_2 = \frac{12 - V_y}{2} = \frac{10.7}{2} = 5.35mA$$


$$\therefore I_1 = I_x + I_2 = 9.55mA$$

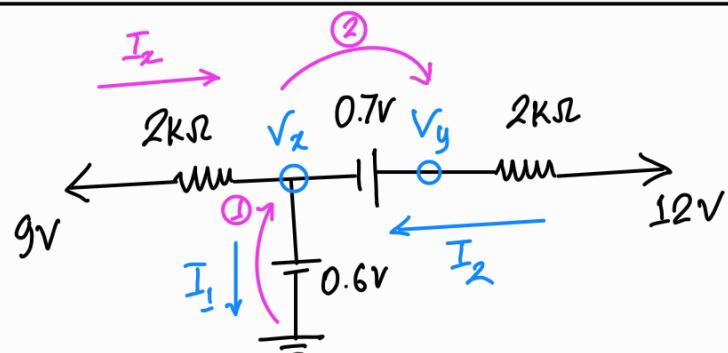

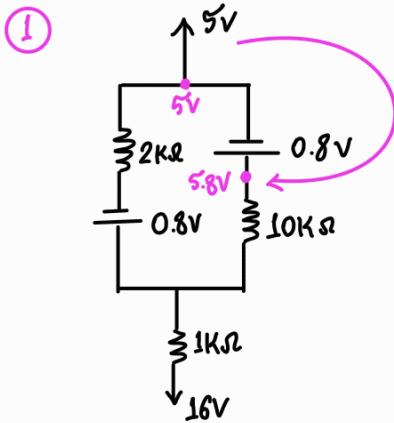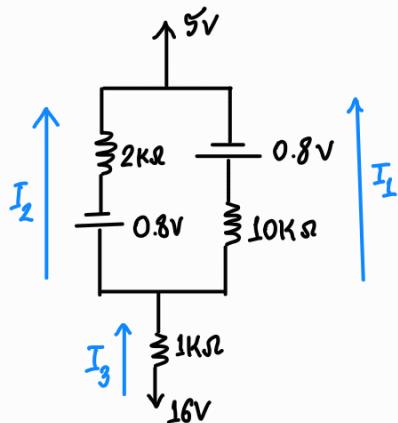
# Find  $I_1, I_2, I_3$  and all the node voltages



Transferring node voltages

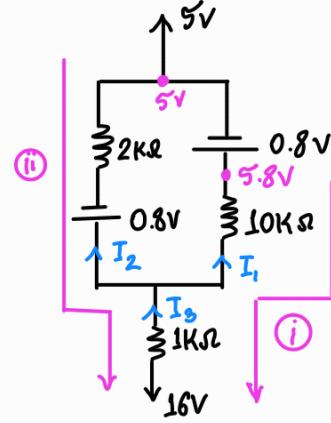

Using nodal analysis —

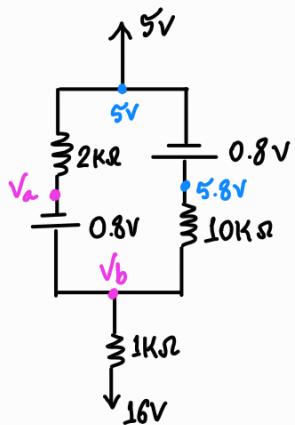

KCL @ SN a,b —

$$\frac{V_a - 5}{2} + \frac{V_b - 5.8}{10} + \frac{V_b - 16}{1} = 0$$

$$\Rightarrow V_a (2^{-1}) + V_b (10^{-1} + 1^{-1}) = 2.5 + 0.58 + 16$$

Voltage relation equation @ SN a,b —

$$-V_a + V_b = 0.8$$

Solving the equations —

$$V_a = 11.375V$$

$$V_b = 12.175V$$

$$I_2 = \frac{11.375 - 5}{2} = 3.1875 \text{ mA}$$

$$I_1 = \frac{12.175 - 5.8}{10} = 0.6375 \text{ mA}$$

$$I_3 = \frac{16 - 12.175}{1} = 3.825 \text{ mA}$$

KVL in line ① —

$$-10I_1 - I_3 = 5.8 - 16$$

KVL in line ② —

$$-2I_2 - 0.8 - I_3 = 5 - 16$$

Using KCL —


$$I_3 = I_1 + I_2$$

Solving the equations we get —


$$I_1 = 0.6375 \text{ mA}$$

$$I_2 = 3.1875 \text{ mA}$$

$$I_3 = 3.825 \text{ mA}$$

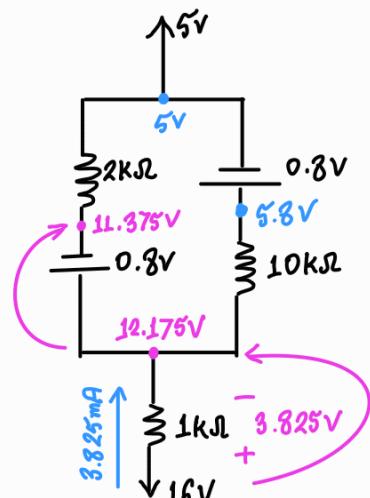

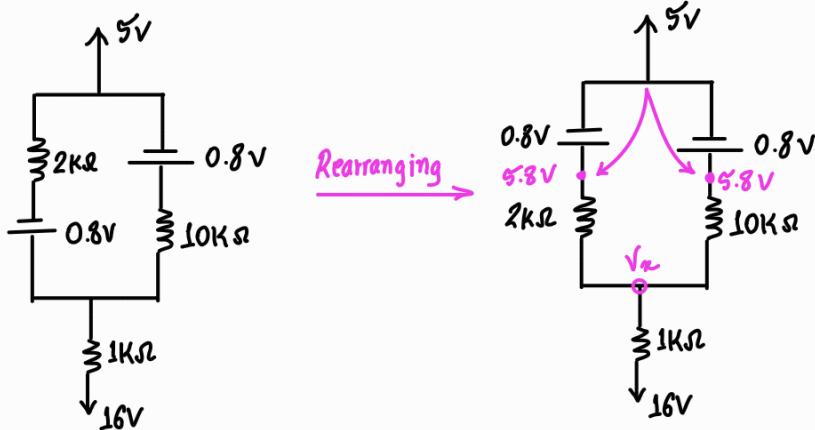You can make the nodal analysis even shorter —



KCL @ node 2 —



$$\frac{V_2 - 5.8}{2} + \frac{V_2 - 5.8}{10} + \frac{V_2 - 16}{1} = 0$$

$$\therefore V_2 = 12.175$$

Then just find  $I_1, I_2$  &  $I_3$  as usual.

Takeaway — There are multiple ways to solve the same problem.

#Find  $I_1, I_2$  &  $V_o$

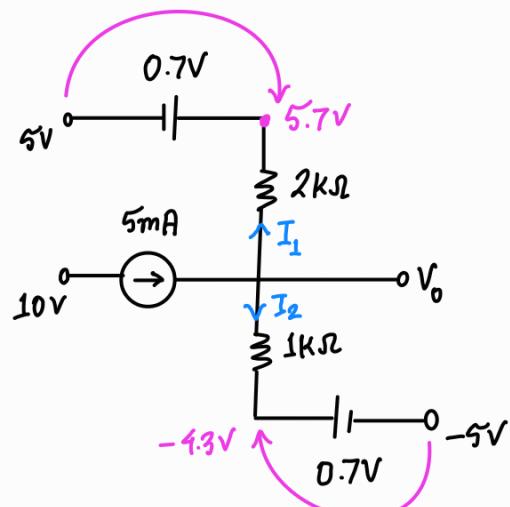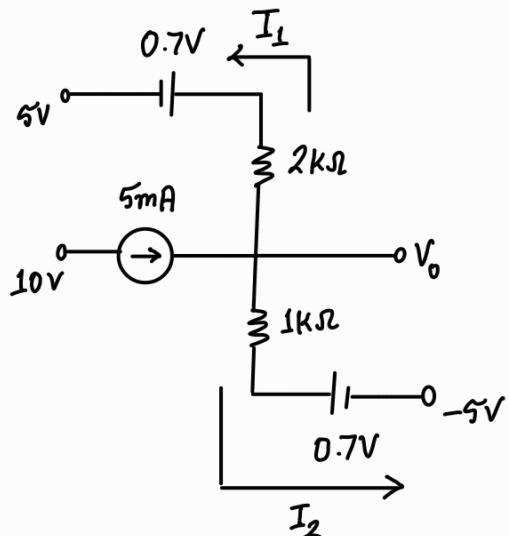

Using KCL @ the output node —

$$5 = I_1 + I_2 \rightarrow 5 = \frac{V_o - 5.7}{2} + \frac{V_o - (-4.3)}{1}$$

$$\therefore V_o = 2.367 \text{ V}$$

$$\therefore I_1 = \frac{2.367 - 5.7}{2} = -1.6665 \text{ mA}$$

$$I_2 = \frac{2.367 - (-4.3)}{1} = 6.667 \text{ mA}$$