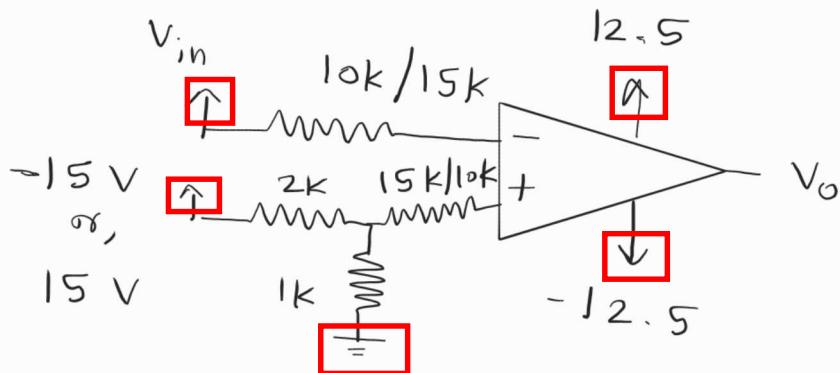


Q1
(a)



There are total 5 modifications needed (marked in the solve) to convert the loop diagram to line diagram. each contains 0.5 marks.

0.5*5 = 2.5 marks

(b) $i_+ = i_- = 0$



0.5 mark for each value

0.5*2 = 1 mark


(c) Op amp inputs zero current, can be treated independently:

$$V_x = \frac{1}{1+2} \times (15 \text{ or } -15)$$

$= -5 \text{ V}$ Set-1, 5 V Set-2

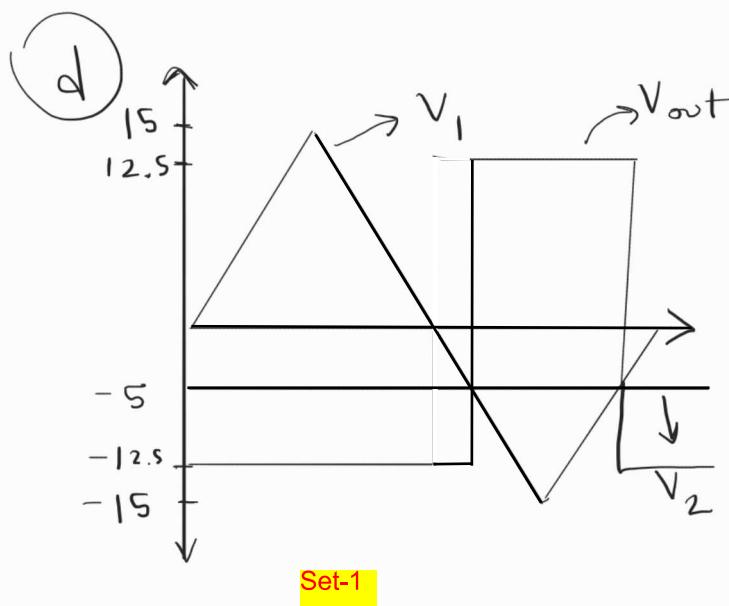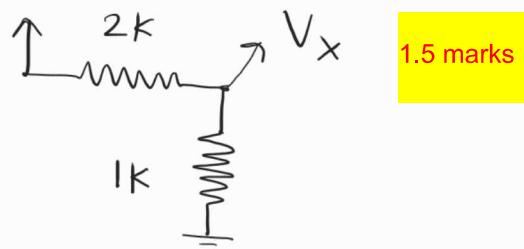

Set-1

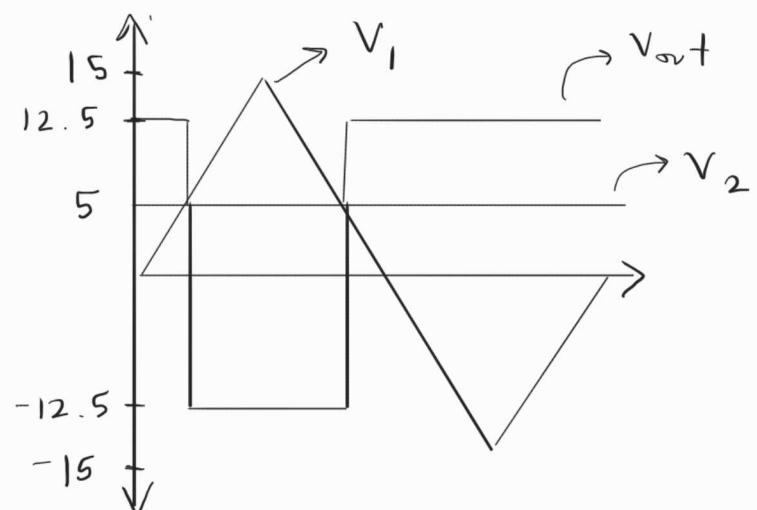


Set-2

2.5 Marks

Q2
Set a

a

P₁, P₂ ON

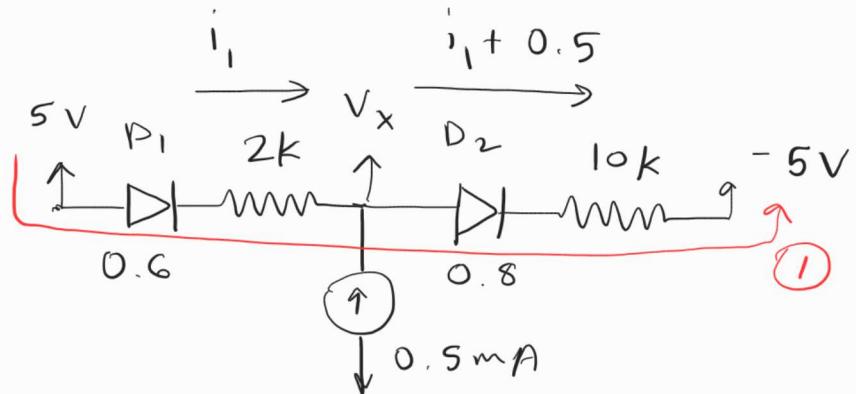

$$\text{Line } ①, 12i_1 + 1.4^+ = 5 + 5$$

$$\Rightarrow 12i_1 = \frac{3.6}{12} = 0.3 \text{ mA}$$

$$V_x = 5 - 0.6 - 2 \times 0.3 = 3.8 \text{ V}$$

$$i_{D_1} = 0.3 \text{ mA}, \quad i_{D_2} = 0.8 \text{ mA}$$

Sect b -

D₁, D₂ ON

Line ①,

$$12 \begin{smallmatrix} 1 \\ 2 \end{smallmatrix} + 1.4 + 5 = 5 + 5$$

$$\Rightarrow i_2 = \frac{3.6}{12} = 0.3 \text{ mA}$$


$$i_{D_1} = 0.8 \text{ mA}, \quad i_{D_2} = 0.3 \text{ mA}$$

W

Correct KVL, KCL eqn - 1 mark
I_D1 - 1 mark
I_D2 - 1 mark
Verification - 1

total 4 marks

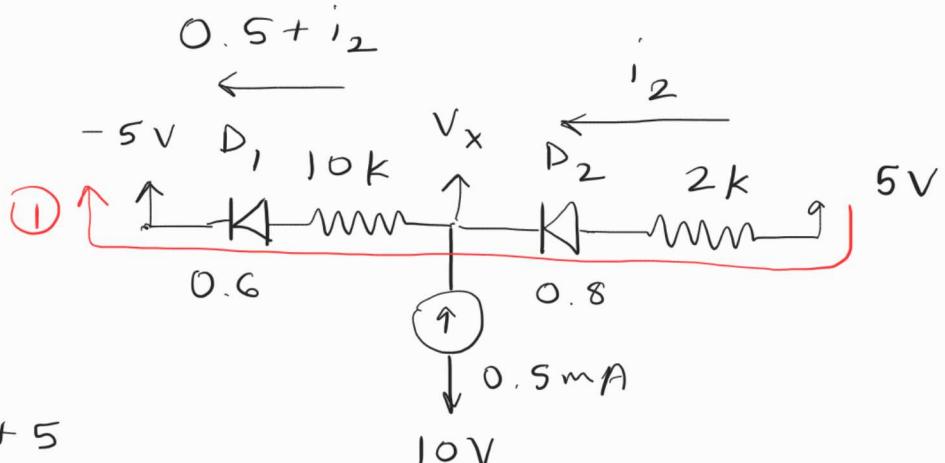
if the initial assumption is wrong
but the procedure is ok, give 2
marks




✓✓

① b) Set A :

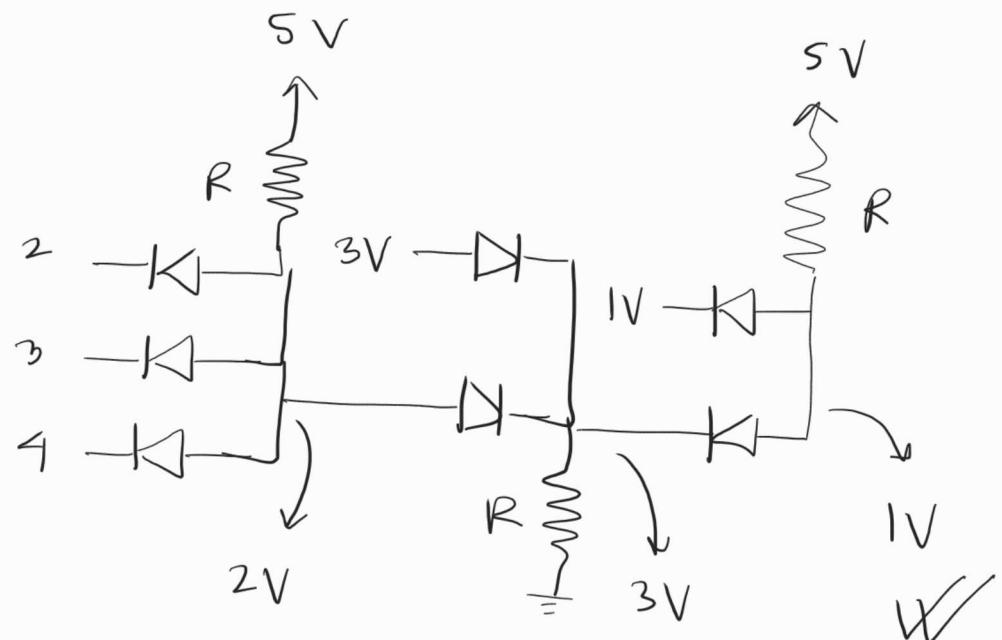
X - 0.5 mark
Y - 0.5 mark
F - 0.5 mark
total - 1.5 marks



Set B :

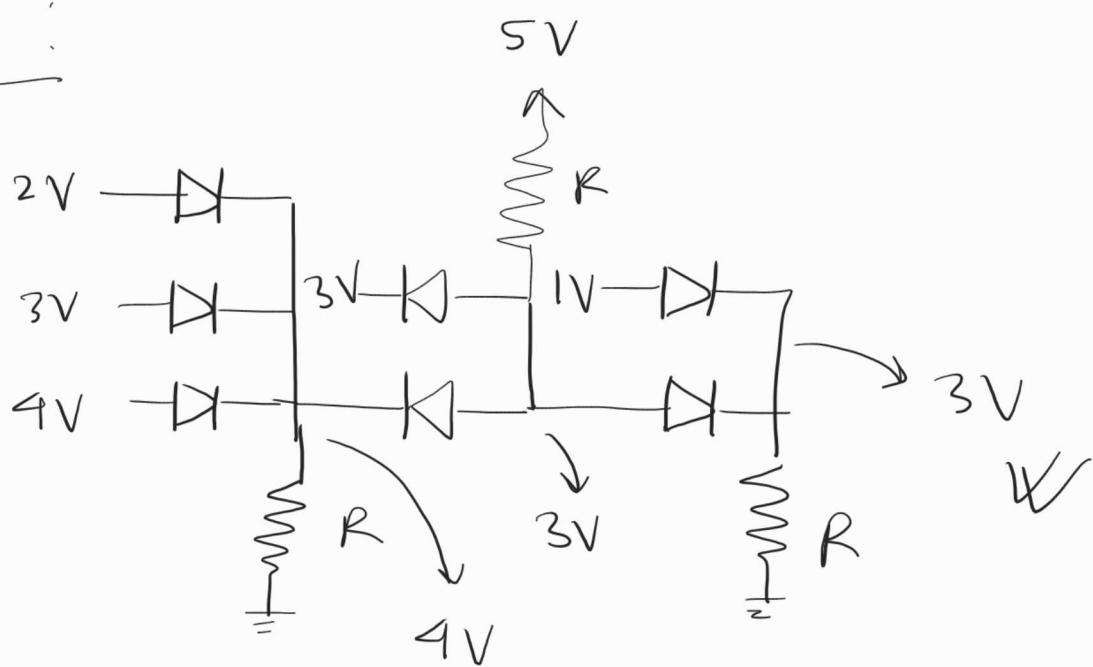


c)

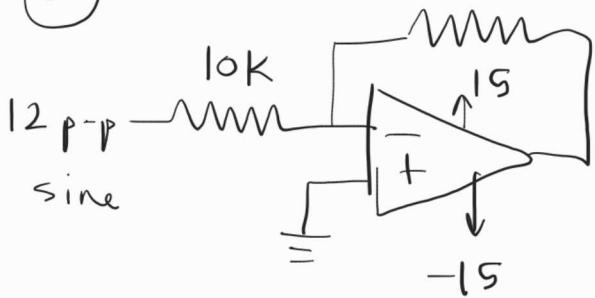


correct eqn - 1 mark
correct graph - 1 mark

total - 2 marks

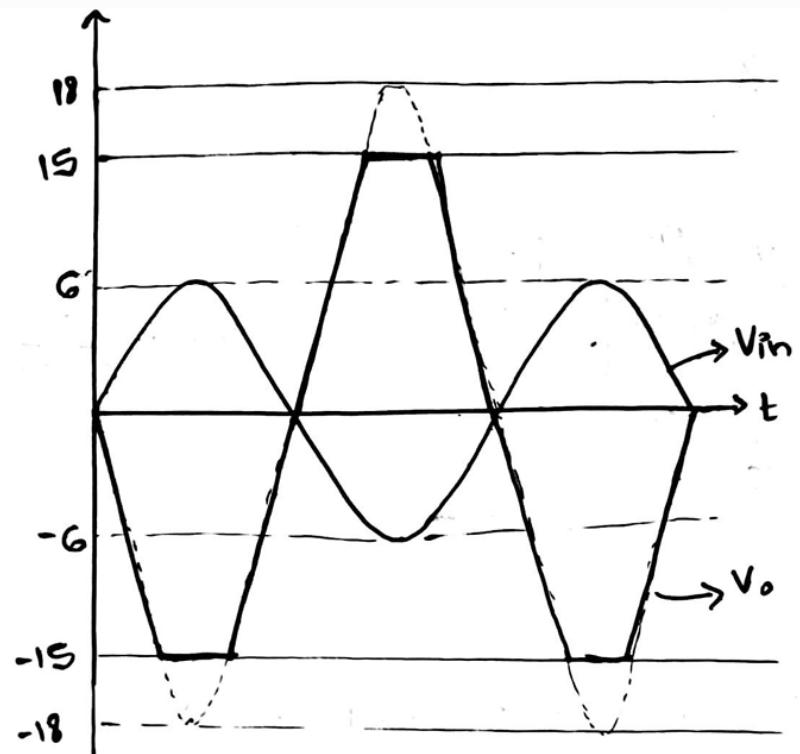
if the graph is not labeled correctly - deduct 0.5 mark



Q3

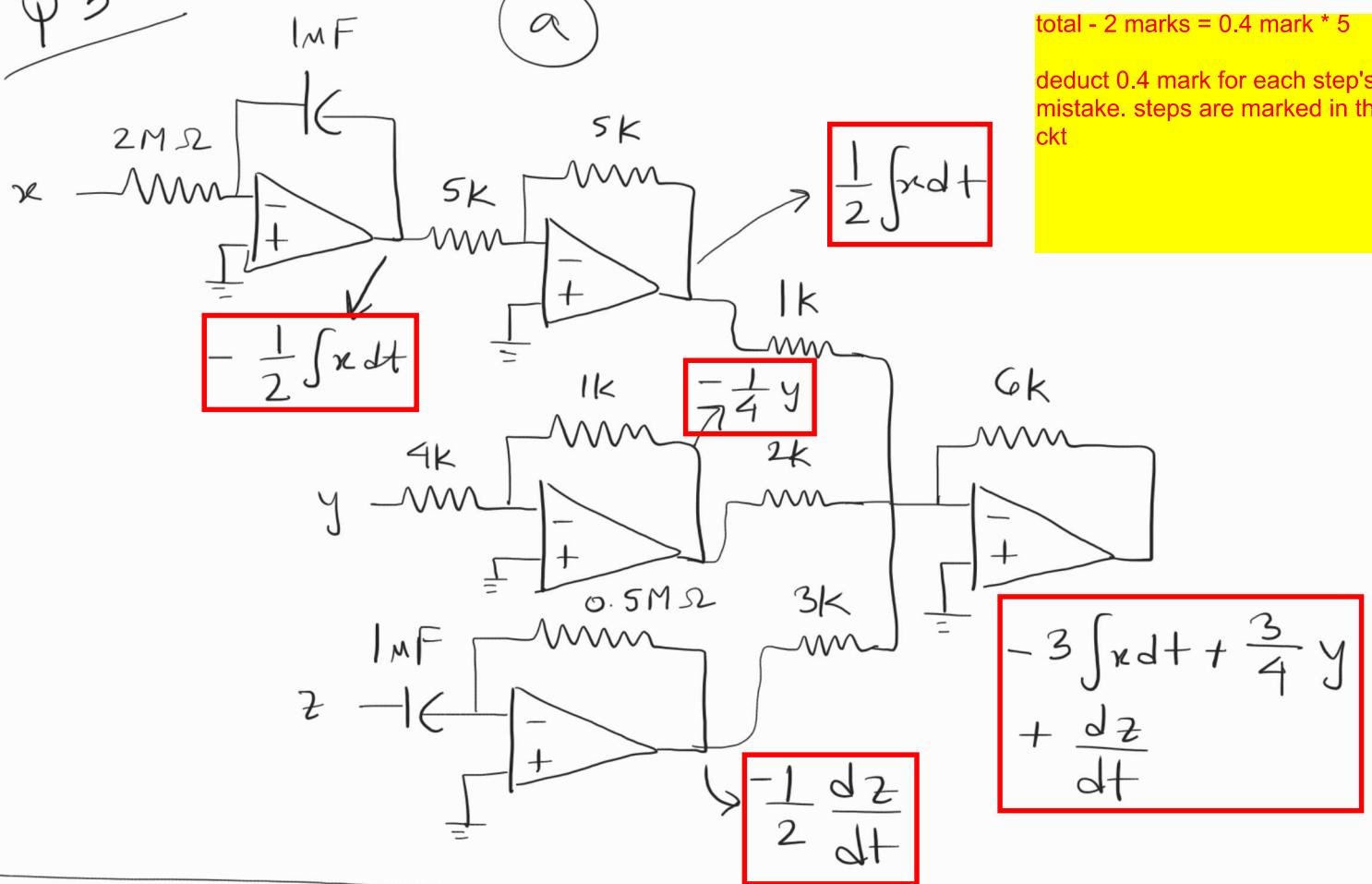

(b)

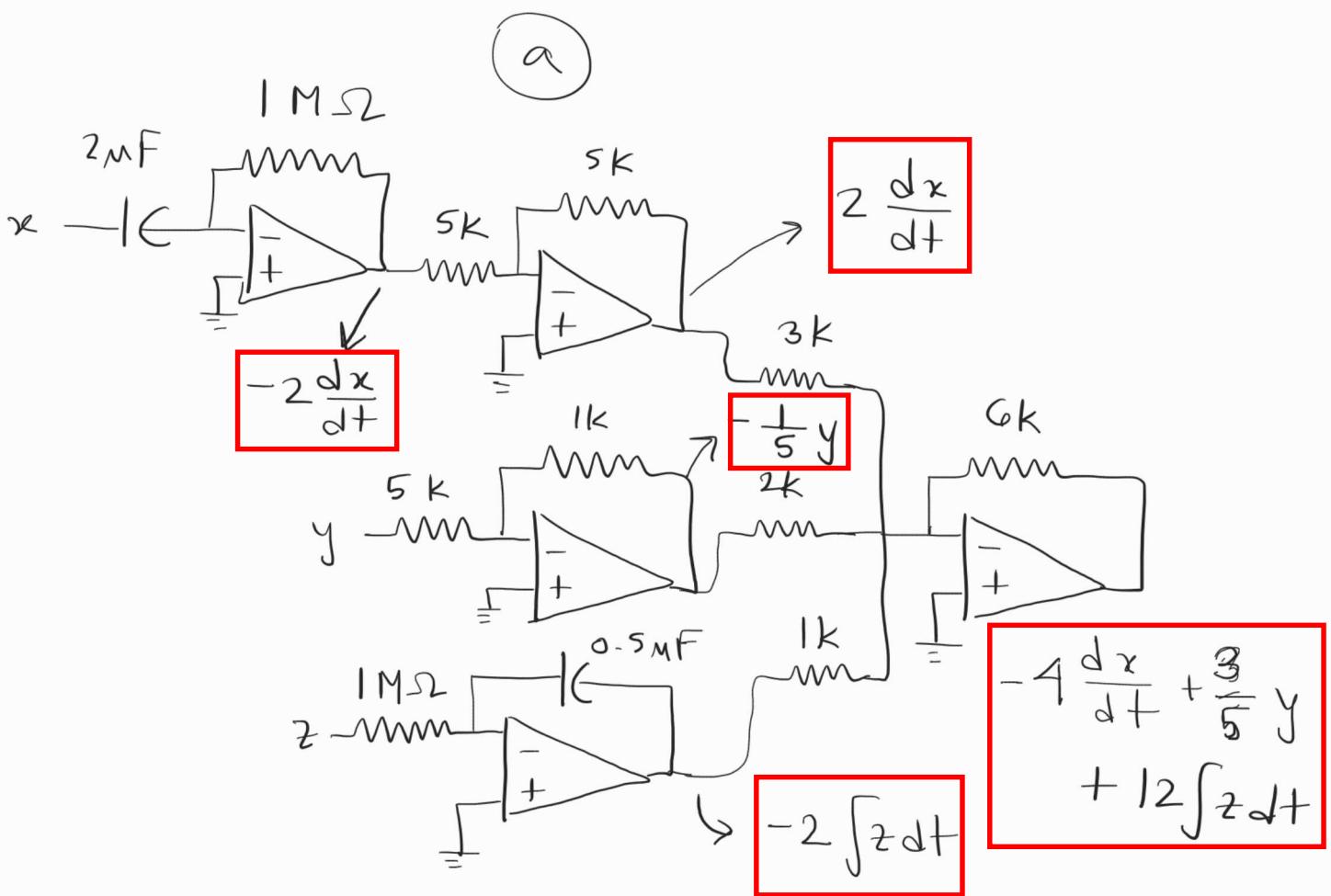

(b)

If D_1, D_2 ON:

$$V_o = -4V,$$

impossible for D_2 ON.Then, D_1 ON, D_2 OFF:

$$\textcircled{1}, 12i_1 + 0.7 = 3 + 4$$

$$\Rightarrow i_1 = \frac{6.3}{12} = 0.525 \text{ mA} > 0 \quad \checkmark \quad D_1 \text{ ON}$$

$$V_x = 3 - 12 \times i_1 = -3.3V$$

I_D1 - 1 mark, I_D2 - 1 mark, V_O - 1 mark
Verification - 1 mark

total 4 marks, if the initial assumption is wrong but the procedure is ok, give 2 marks

$$V_{D_2} = -3.3 - (-3) = -0.3 < 0.7 \quad \checkmark \quad D_2 \text{ OFF}$$

If D_1, D_2 ON:

$$V_o = -4V,$$

impossible for D_2 ON.Then, D_1 ON, D_2 OFF:



$$\textcircled{1}, 6i_1 + 0.7 = 3 + 4$$

$$\Rightarrow i_1 = \frac{6.3}{6} = 1.05 \text{ mA} > 0 \quad \checkmark \quad D_1 \text{ ON}$$


$$V_x = 3 - 6 \times i_1 = -3.3V$$

$$V_{D_2} = -3.3 - (-3) = -0.3 < 0.7 \quad \checkmark \quad D_2 \text{ OFF}$$

(A)

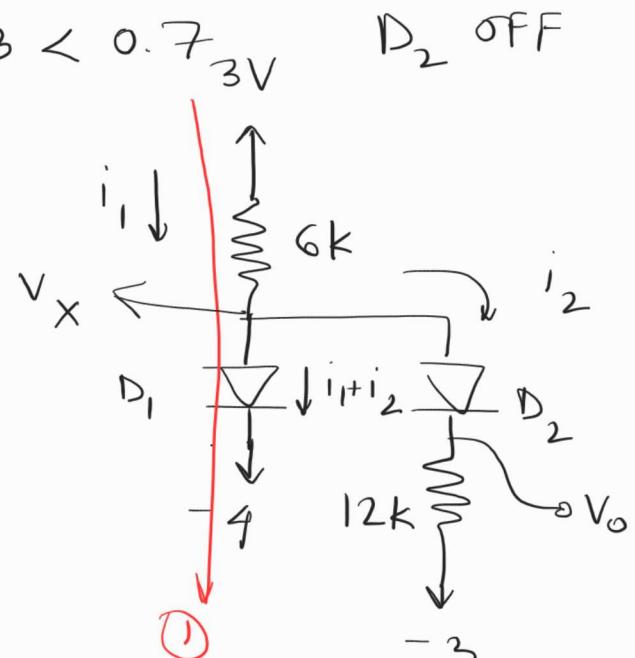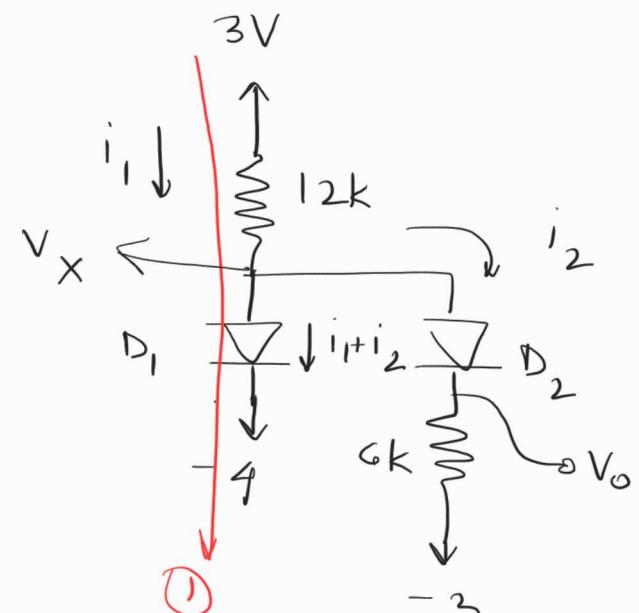

(c)

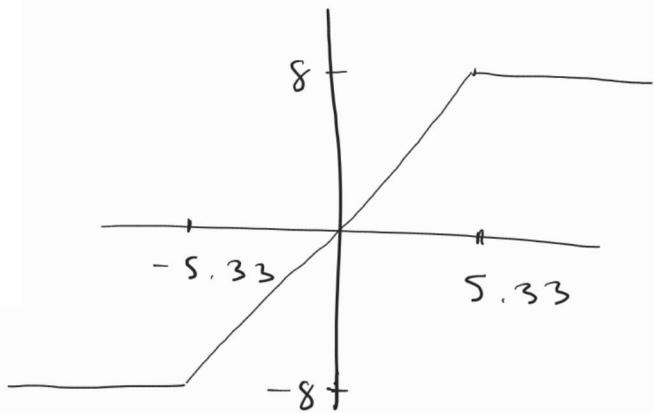

$$V_o = 1.5 V_{in}$$

$$V_o = 8 \therefore V_{in} = 5.33V$$

$$V_o = 8 \mid V_{in} = 5.33V$$

Correct graph - 1 mark
Correct label - 0.5 mark
total - 1.5 marks

Q-4

Set-01

1 mark
no partial

(a) $V_o = A(V_+ - V_-) = AV_d$


(b) Linear amplifier is an amplifier whose output is proportional to its input.

===== Alternative definition =====
A linear amplifier is a device that follows this equation--
Output = $k \times$ Input
here, k is a constant

Reason for saturation \rightarrow power supply to the amplifier.

definition - 1 mark
reason - 1 mark
total - 2 marks

(c)

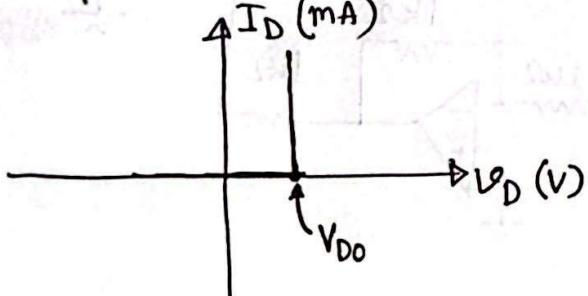

correct graph - 1 mark
proper label - 1 mark
total - 2 marks


4.

(a) Same as set-01

=====Rubric=====

(b) Same as set-01

(c)

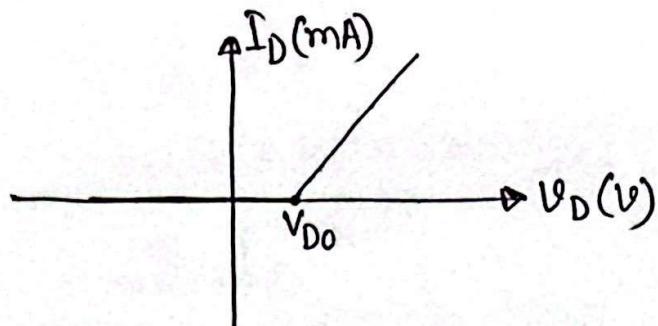

Set-01

5(a) $V_{in} = 10 \cos(t)$

$V_o = 5 \sin(t)$ [By inspection]

gain = $5/10 = 0.5$

Differentiating $\cos(t)$ gives $-\sin(t)$;

Differentiator gain, $R_f C_1 = 0.5$

$$C_1 = \frac{1}{2R_f} \rightarrow \text{Let } R_f = 0.5 \quad \left. \begin{array}{l} \text{set complementary} \\ \text{units} \end{array} \right\} \\ \therefore C_1 = 1 \quad \left. \begin{array}{l} (M\Omega \times \mu F, k\Omega \times mF) \end{array} \right\}$$

(Double check -

$$V_o = -0.5 M\Omega \times 1 \mu F \times \frac{d}{dt} 10 \cos(t) \\ = -\frac{10}{2} (-\sin(t)) \\ = +5 \sin(t)$$

identifying differentiation - 1 mark
ckt implementation - 2 marks

total - 3 marks

(b) Same as 'set-02' 5(b)

6. (a) Non-inverting amplifier-

$$|\text{Slope}| = \left| \frac{\Delta V_{out}}{\Delta V_{in}} \right| = \left| \frac{10}{5} \right| = 2$$


identifying ckt - 1 mark
ckt implementation - 1 mark

total - 2 marks

$$\text{Slope} = 2 = \left(1 + \frac{R_f}{R_i} \right) = \text{gain}$$

$$\therefore \frac{R_f}{R_i} = 1$$

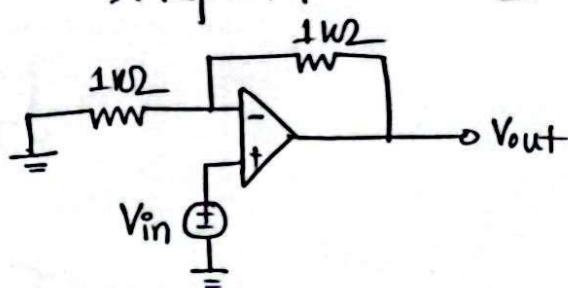
$$\therefore R_f = R_i = 1 k\Omega \quad [\text{let's assume}]$$




$$\begin{aligned}
 (b) \quad f &= 3 \frac{d}{dt} (x+y) - 5 \int z dt \\
 &= 3 \frac{d}{dt} x + 3 \frac{d}{dt} y - 5 \int z dt
 \end{aligned}$$

Total - 3 marks

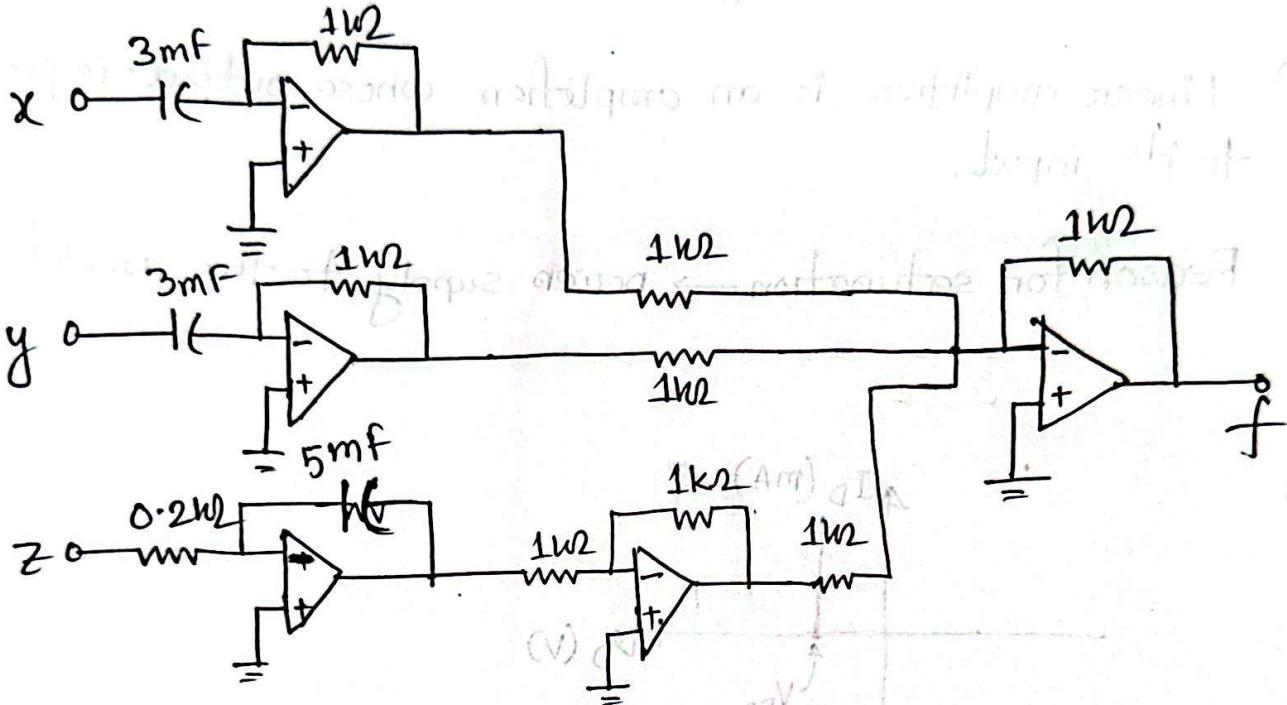give partials according to your judgement



7. (a)

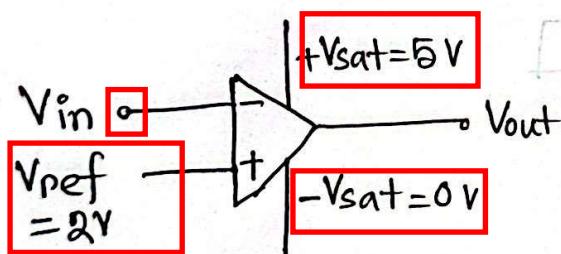

1 mark for each terminal

4 * 1 mark = 4 marks

(b) Not possible.

1 mark
no partial


Set B

b.

(a) Given.

$$V_{\text{input}} = 5 \sin(t)$$

$$V_{\text{output}} = 10 \cos(t)$$

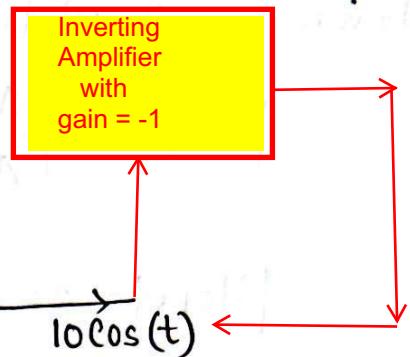


$$= 2 \times 5 \frac{d}{dt} \sin(t)$$

$$= RC \times \frac{d}{dt} [5 \sin(t)]$$

$$\therefore RC = 2$$

Let's assume, $R = 1 \text{ k}\Omega$; $C = 2 \text{ mF}$

Circuit:

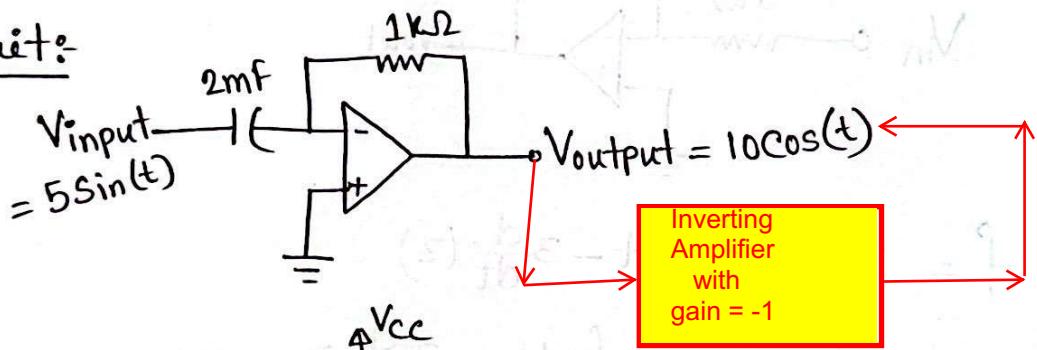


(b)

(i)

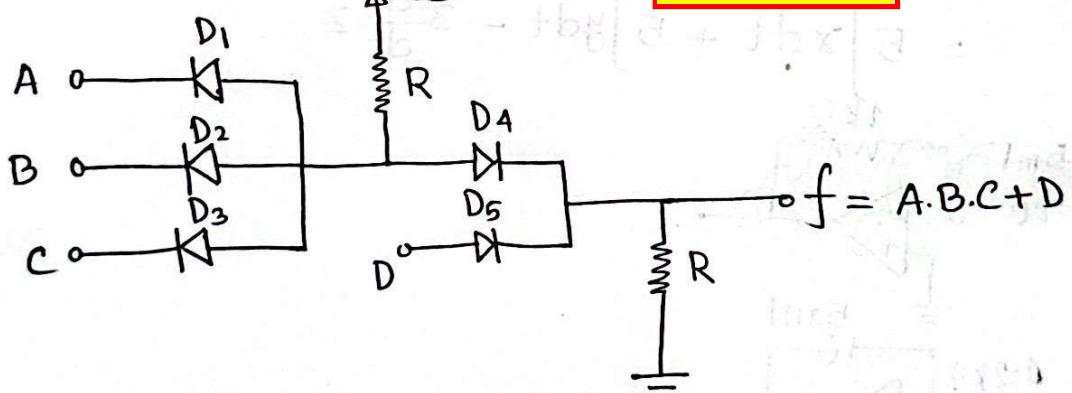
(i) - 1 mark
(ii) - 1 mark

Total - 2 marks

give partials
according to your
judgement



(iii)

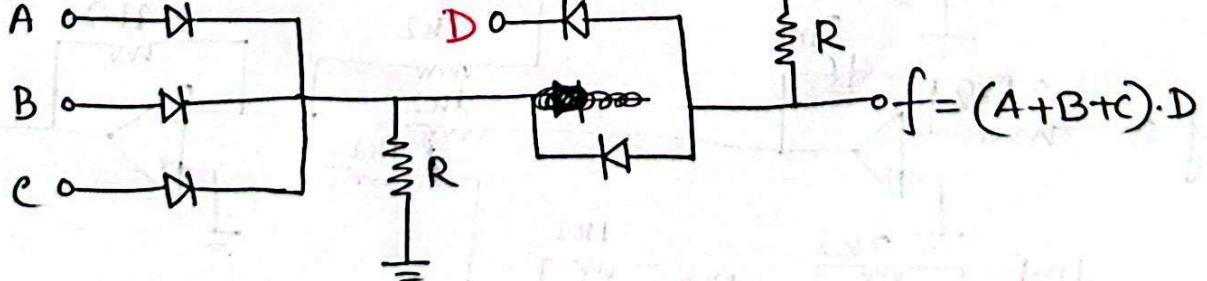

6.

(a) Inverting Amplifier-

$$|\text{Slope}| = \left| \frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} \right| = \left| \frac{10}{5} \right| = 2$$


$$|\text{Slope}| = 2 = \frac{R_f}{R_i} = \text{gain}$$

$$\therefore R_f = 2R_i$$

=====Rubric=====


Let's assume, $R_i = 1\text{ k}\Omega$

$$\therefore R_f = 2 \text{ k}\Omega$$

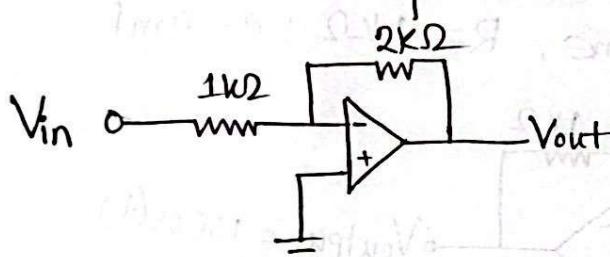


$$(b) \quad f = 5 \int (x+y) dt - 3 \frac{d}{dt} (z)$$
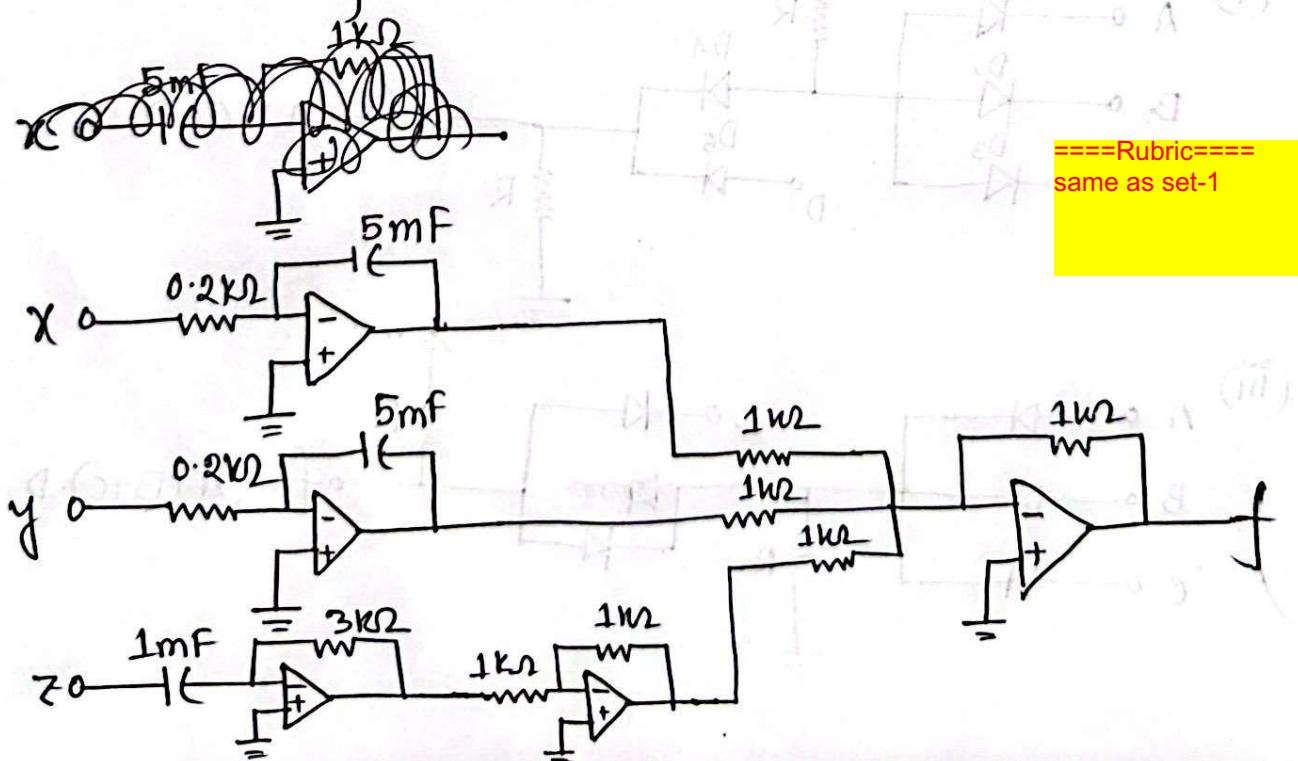
$$= 5 \int x dt + 5 \int y dt - 3 \frac{d}{dt} z$$



7.

(a)

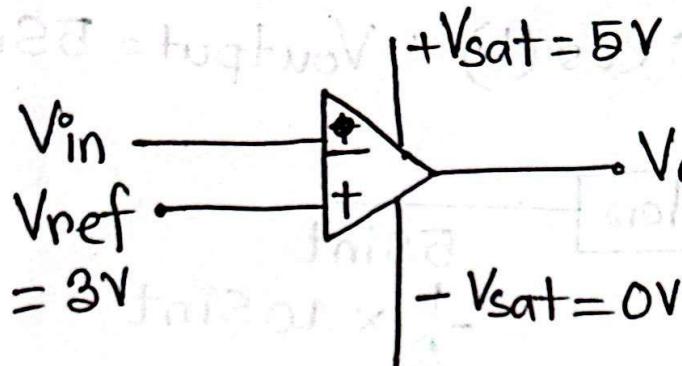

(b) Not possible.

====Rubric====
same as set-1