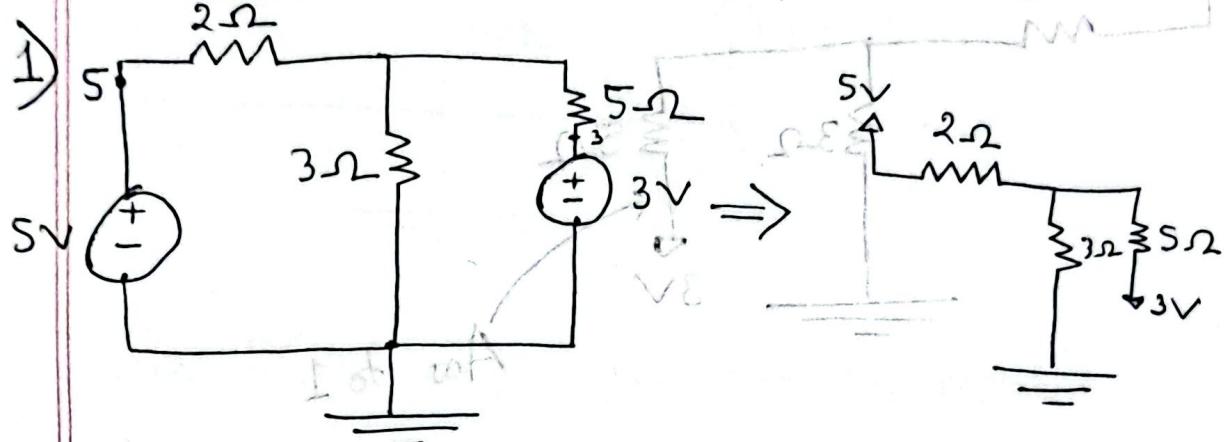


Lecture-1CSE-250 reviewLine representation

- 1) Decide a ground such that floating voltage sources are minimized (Maximum voltage source will have a ground)



Non-floating



floating

11) Replace voltage sources with known node voltages

5V

2Ω

$10V$



2Ω

3Ω

5Ω

3V

Ans to 1

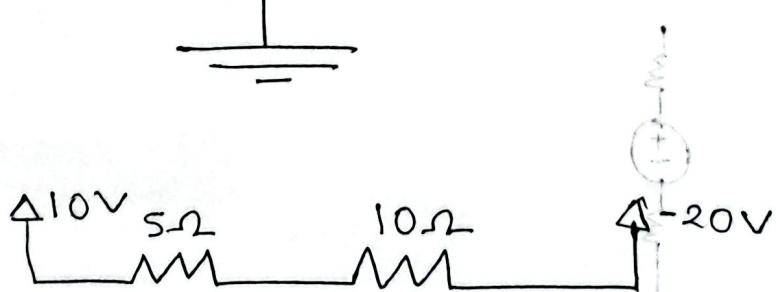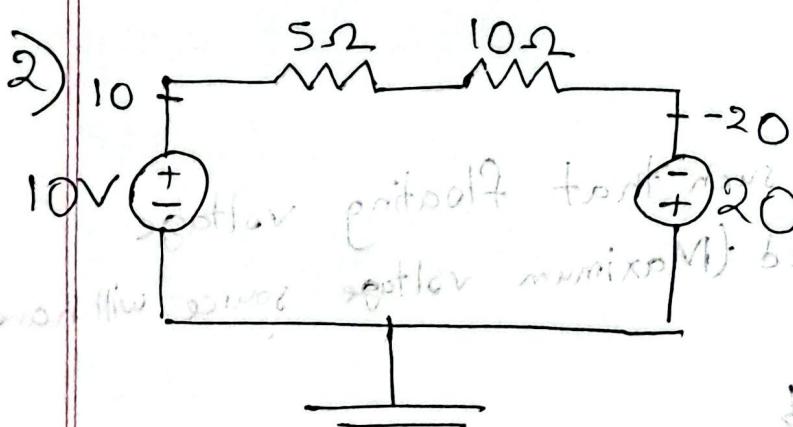

10V 5Ω

10Ω

10Ω

10Ω


-20V

10V 5Ω

10Ω


10Ω

-20V

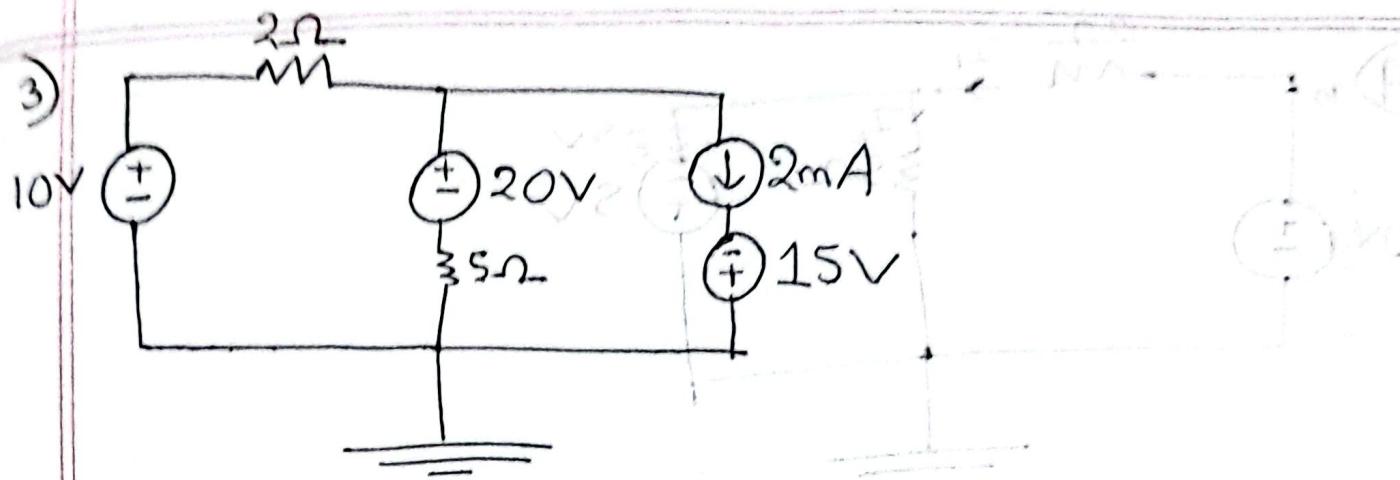



The 20V and 5Ω can be replaced with

Hence the line representation will be,

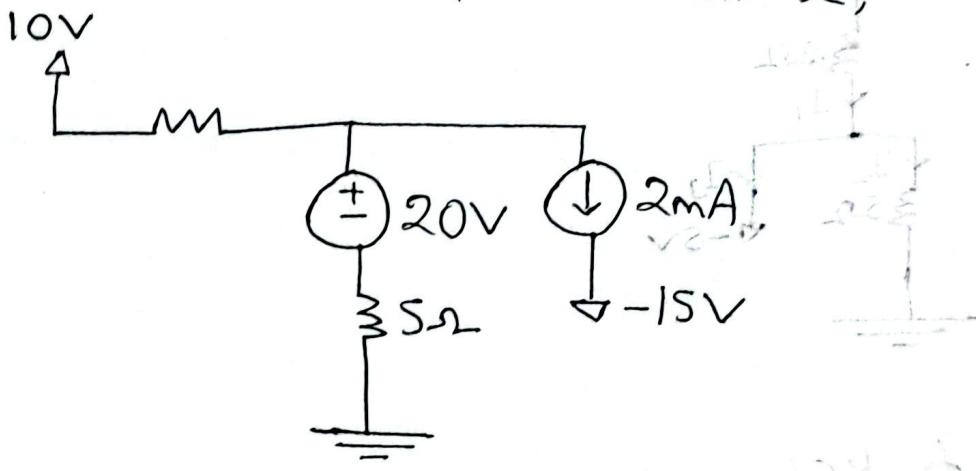


or

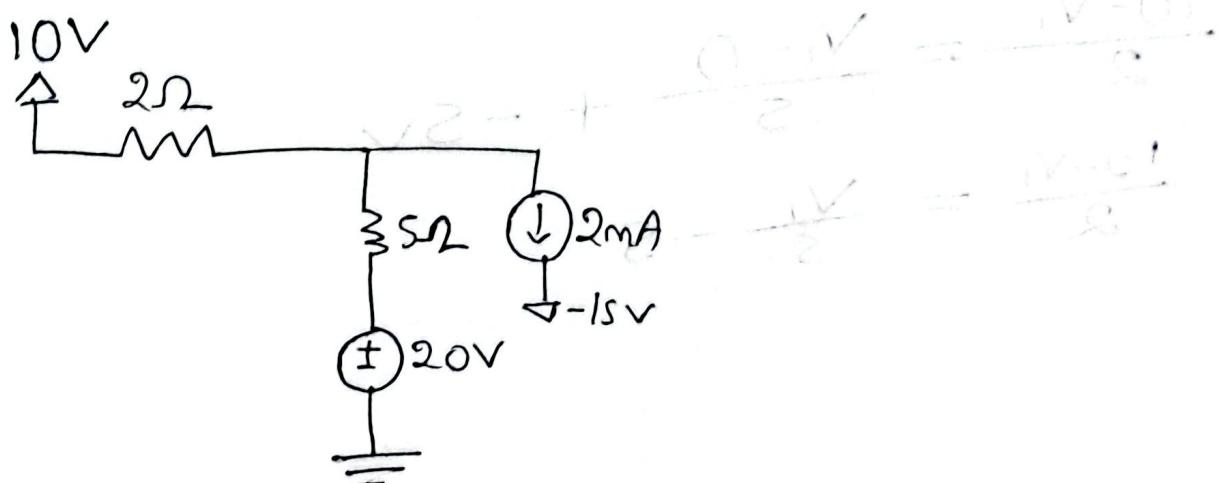

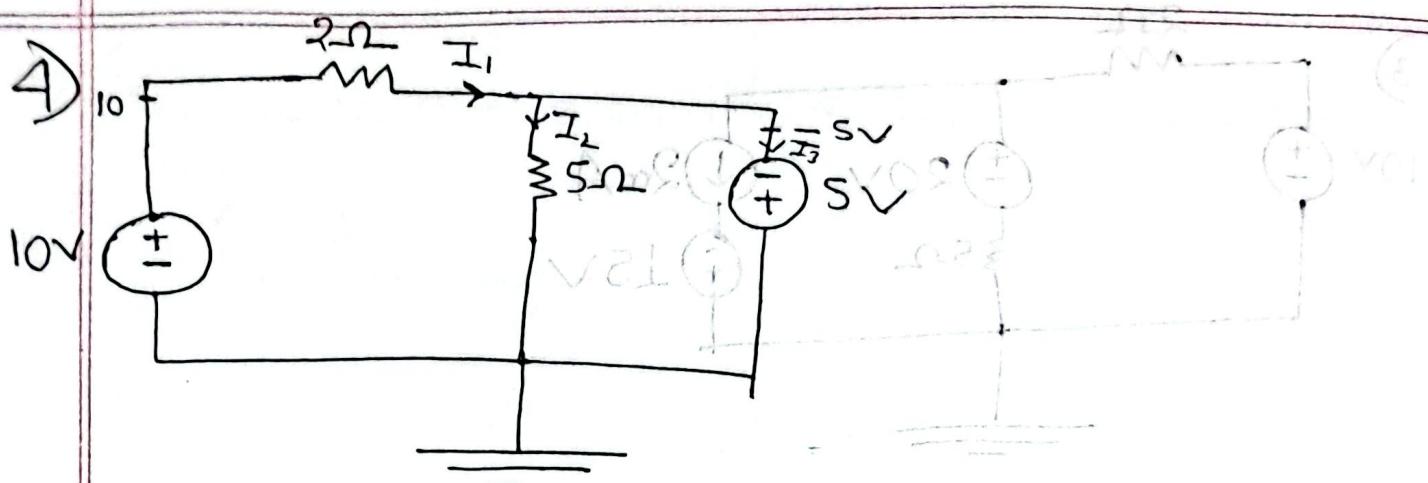

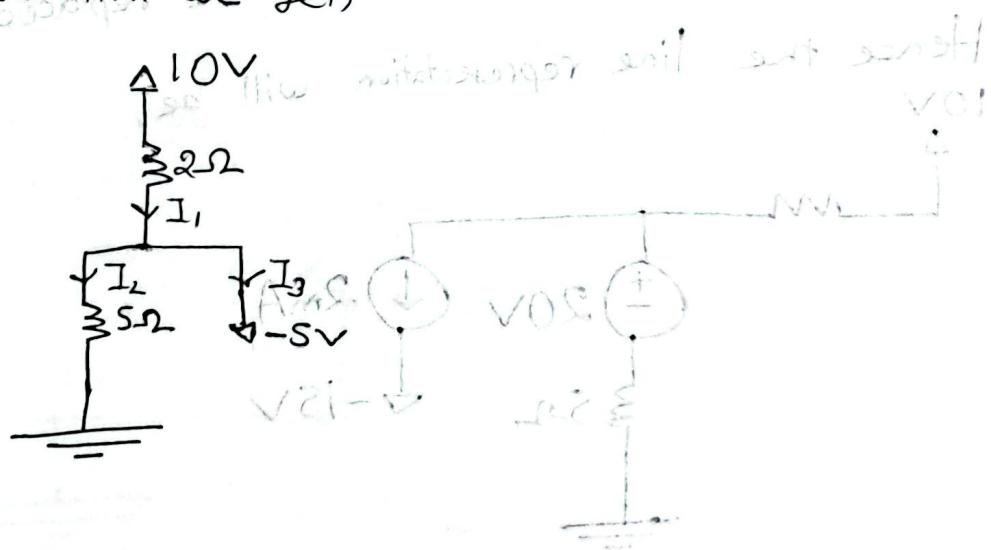Line representation we get $\frac{dx}{dt} = \frac{1}{2} \sin \theta$ all




According to KCL,

$$I_1 = I_2 + I_3$$

$$\therefore \frac{10 - V_1}{2} = \frac{V_1 - 0}{5} + -5V_1$$

$$\frac{10-v_1}{2} = \frac{v_1}{5} - 5$$

KVL in Line representation

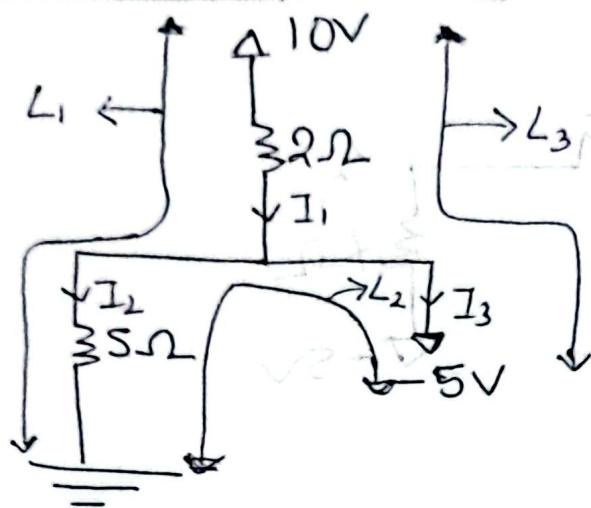

electrical network



- We will do KVL in terms of Line. There are 3 different voltages, hence there can be 3 equations
- A line will have a starting and ending voltage

Box Starting voltage - End voltage = All of the components in between

$$10 - 0 = 2I_1 + 5I_2 \quad (L_1)$$

$$10 = 2I_1 + 5I_2 \quad (1)$$

$$0 - (-5) = -5I_2 \quad (L_2)$$

$$5 = -5I_2$$

$$I_2 = -1A$$



$$10 - (-5) = 2I_1 \quad (L_3)$$

$$15 = 2I_1$$

$$I_1 = 7.5A$$

$$0 = \frac{2}{3} + \frac{15}{5} - \left(\frac{1}{2} + \frac{1}{2}\right) \quad \text{Ans}$$

Nodal Analysis

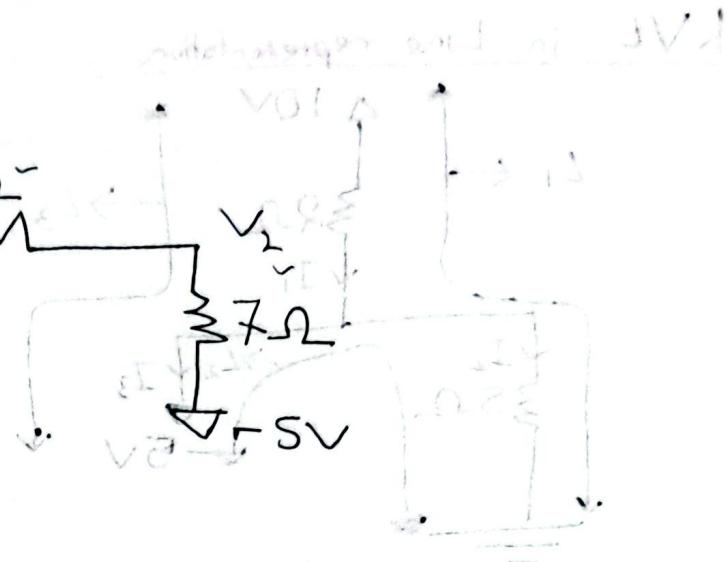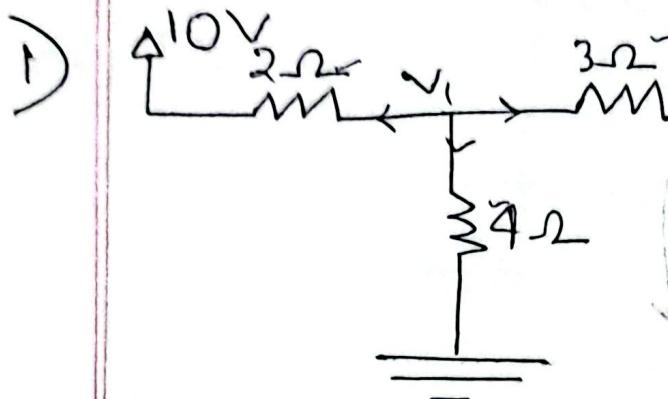

Applying Nodal at V_1 we get

$$\frac{V_1 - 10}{2} + \frac{V_1 - V_2}{3} + \frac{V_1 - 0}{4} = 0 \text{ A}$$

$$V_1 \left(\frac{1}{2} + \frac{1}{3} + \frac{1}{4} \right) - \frac{10}{2} - \frac{V_2}{3} = 0$$

$$V_1 \left(\frac{1}{2} + \frac{1}{3} + \frac{1}{4} \right) - 5 - \frac{V_2}{3} = 0$$

$$V_1 \left(\frac{1}{2} + \frac{1}{3} + \frac{1}{4} \right) - 5 = 0$$

$$\frac{V_1 - V_2}{3} + \frac{V_1 + 5}{7} = 0$$


$$V_2 \left(\frac{1}{3} + \frac{1}{7} \right) - \frac{V_1}{3} + \frac{5}{7} = 0$$

$$V_2 \left(\frac{1}{3} + \frac{1}{7} \right) - \frac{V_1}{3} + \frac{5}{7} = 0$$

$$V_2 = 2$$

$$V_1 = 5$$

2)

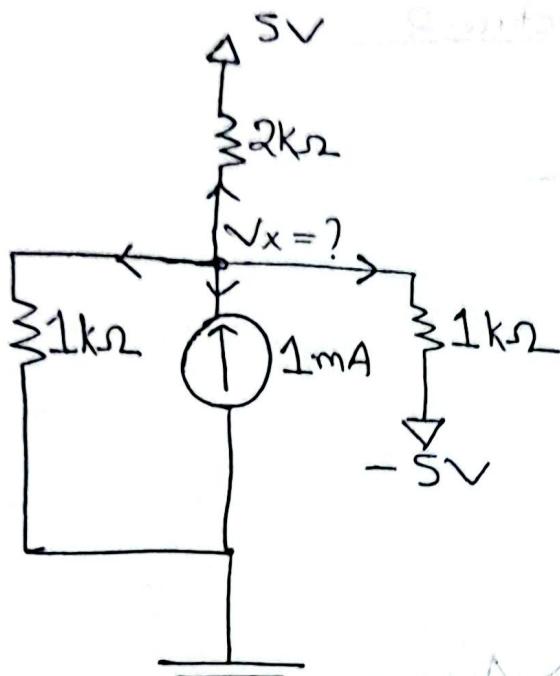

position sign set ~~mit einem \leftarrow anfangen - schreibe~~

$$\frac{V_x - 0}{1} + \frac{V_x + 5}{1} \xrightarrow{\text{mit einem } \leftarrow \text{ anfangen und erst}} + \frac{V_x - 5}{2} - 1 = 0$$

$$V_x + V_x + 5 - 1 = \frac{5 - V_x}{2}$$


$$2V_x + 4 = \frac{5 - V_x}{2} \xrightarrow{\text{mit einem } \leftarrow \text{ anfangen und erst}}$$

$$\cancel{V_x + 2} = \cancel{5 - V_x} \quad 4V_x + 8 = 5 - V_x$$

$$2V_x = -3$$

$$V_x = -1.5$$

$$V_x = -0.6$$

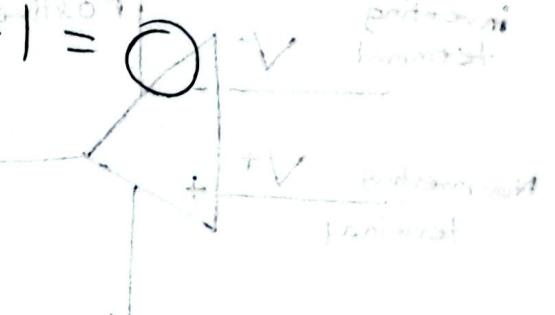


lecture-2Syllabus for Mid-term

- 1) Op-Amp
- 2) Diode
- 3) MOSFET
- 4) BJT

Op-Amp

Operation-Amplifier \Rightarrow Amplifier the input voltage

Perform Mathematical operation

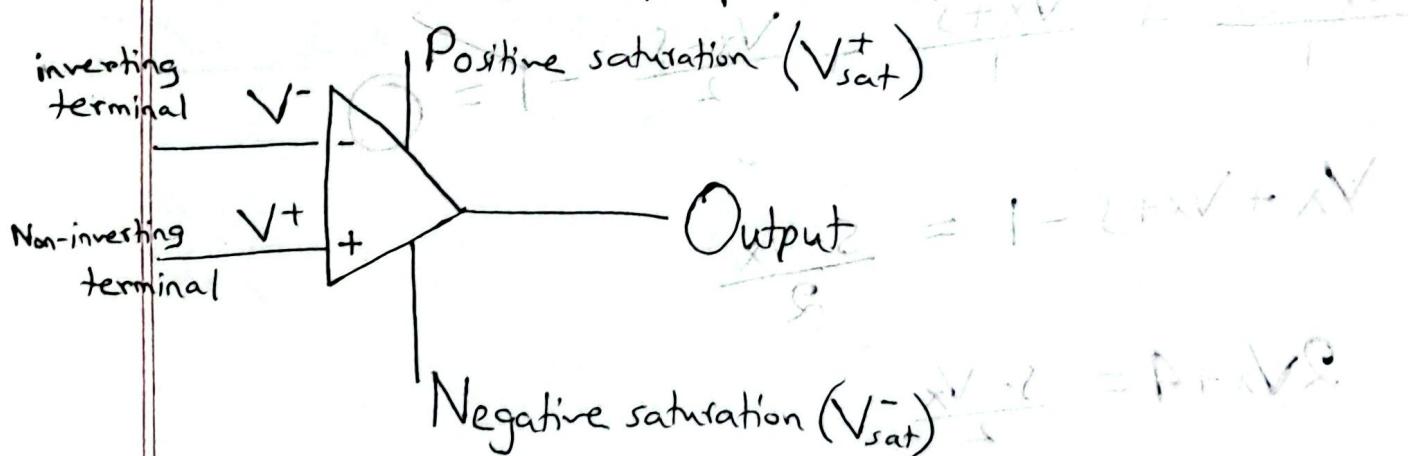

Op-Amp is a difference amplifier

$$V_d = V^+ - V^- \quad (\text{Non-inverting} - \text{Inverting})$$

$$V_o = A V_d$$

Gain

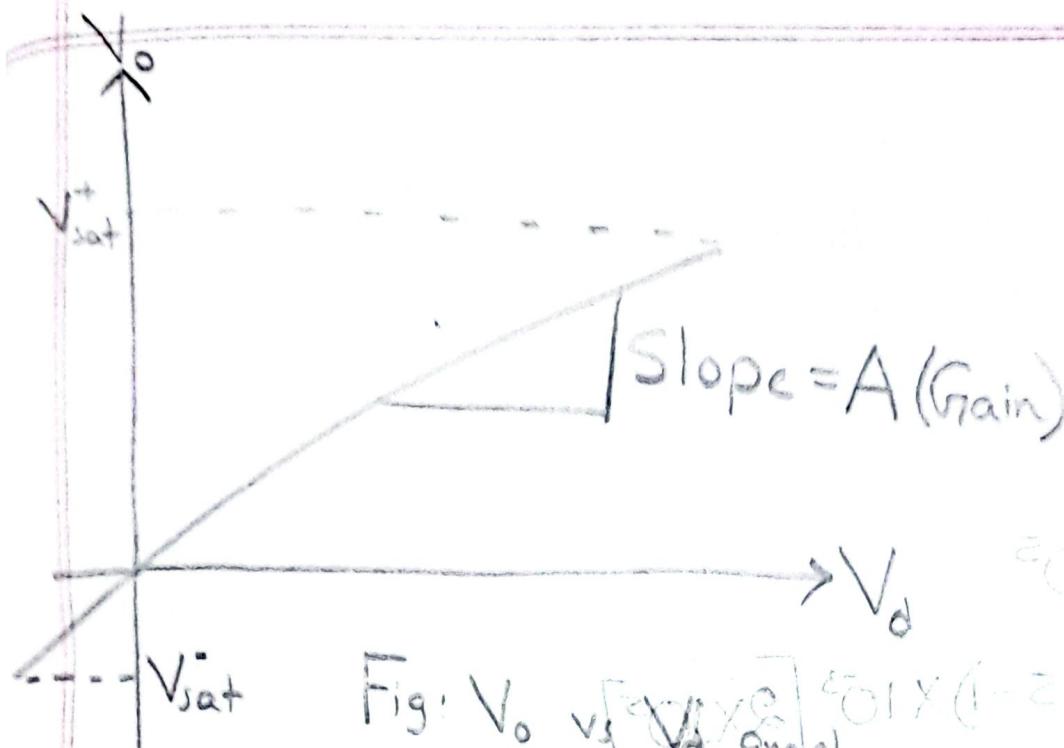




Fig: $V_o \propto V_i$ (Graph) $\therefore V_o = A V_i$


1) Given,

$$V_{sat}^+ = 10V$$

$$V_{sat}^- = -10V$$

$$A = 3$$

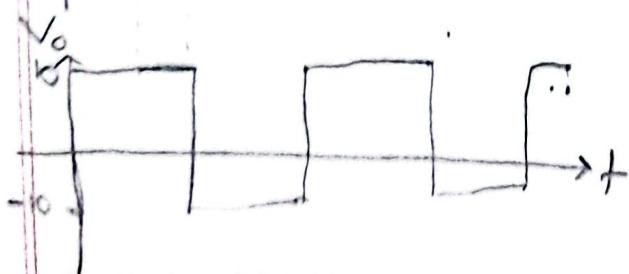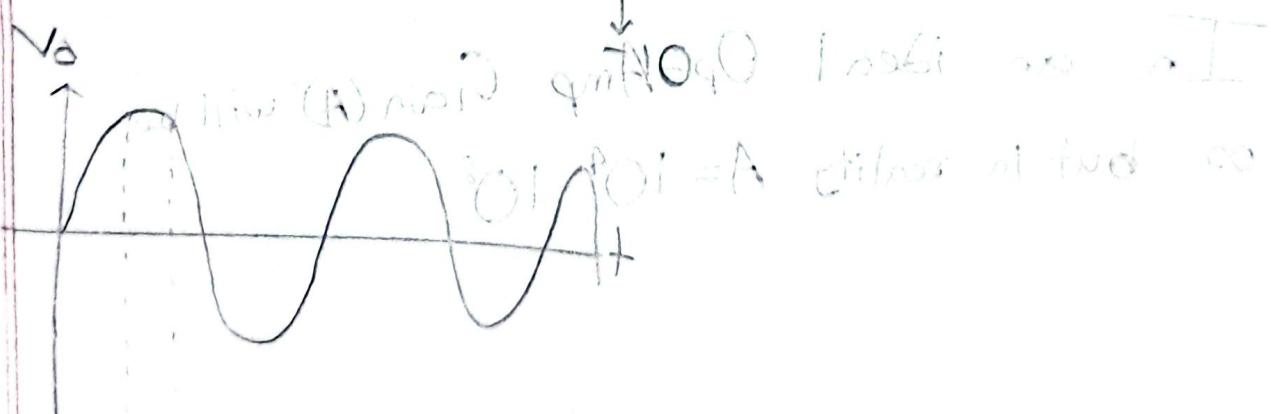

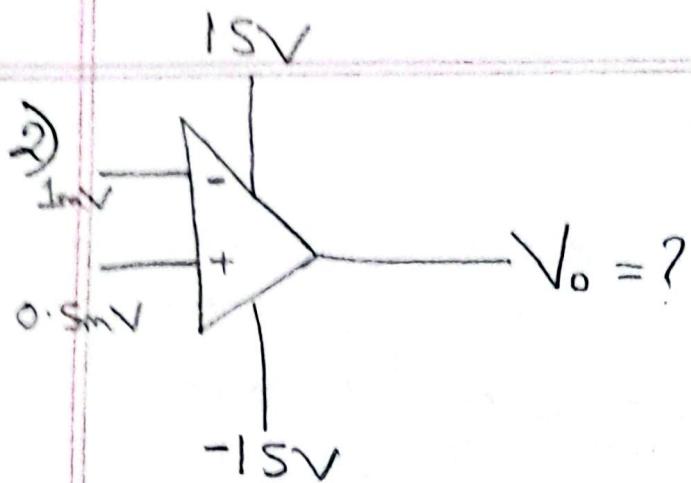

$$A = 2 \times 10^5$$

$$V_o = (0.5 - 1) \times 10^3 [2 \times 10^5]$$

$$= (-0.5 \times 10^3) (2 \times 10^5)$$

$$= -100$$

Since $-100V$ is less than $V_{sat}(-15V)$, V_o will be $\approx V_{sat} = -15V$

In an ideal Op-Amp Gain (A) will be ∞ but in reality $A = 10^4 - 10^8$

Comparator



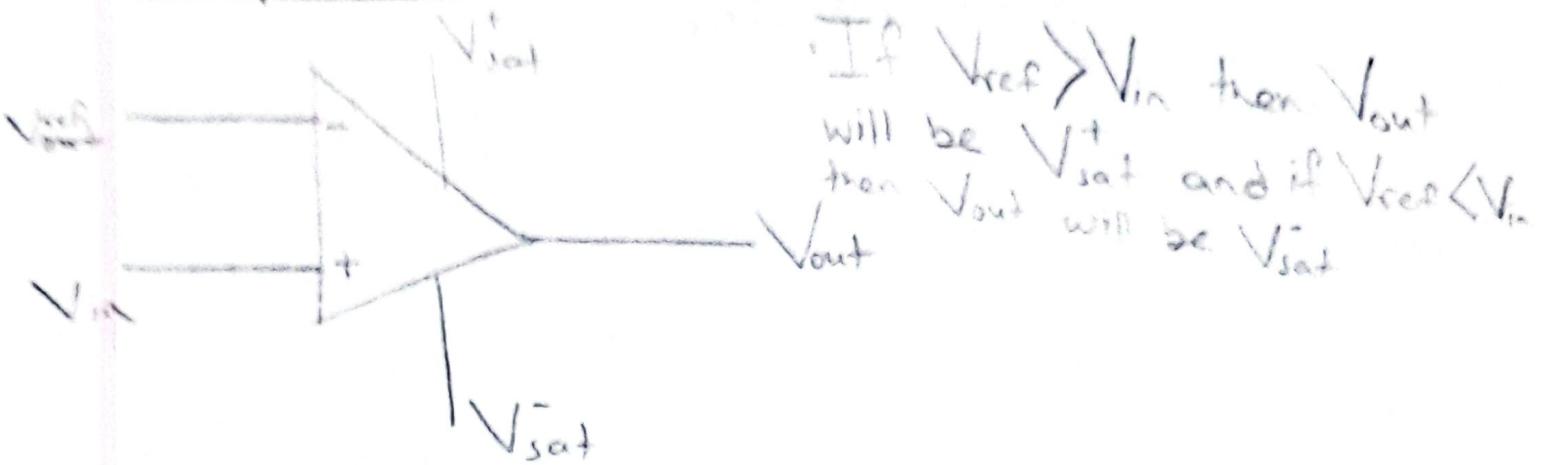



Fig: Non-inverting Comparator

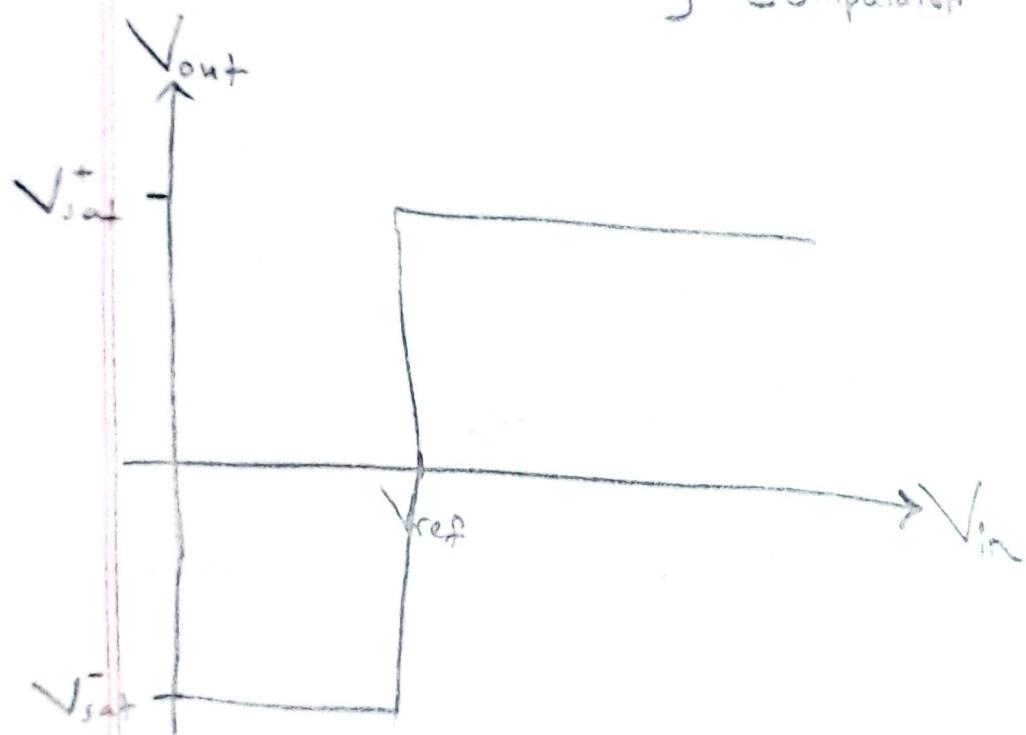


Inverting Comparator

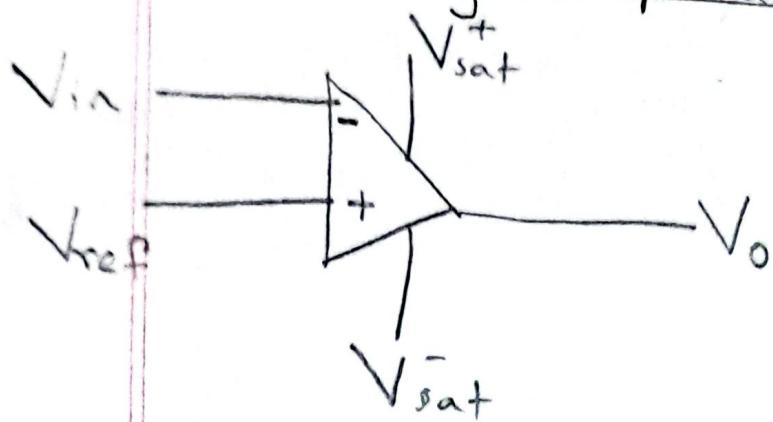

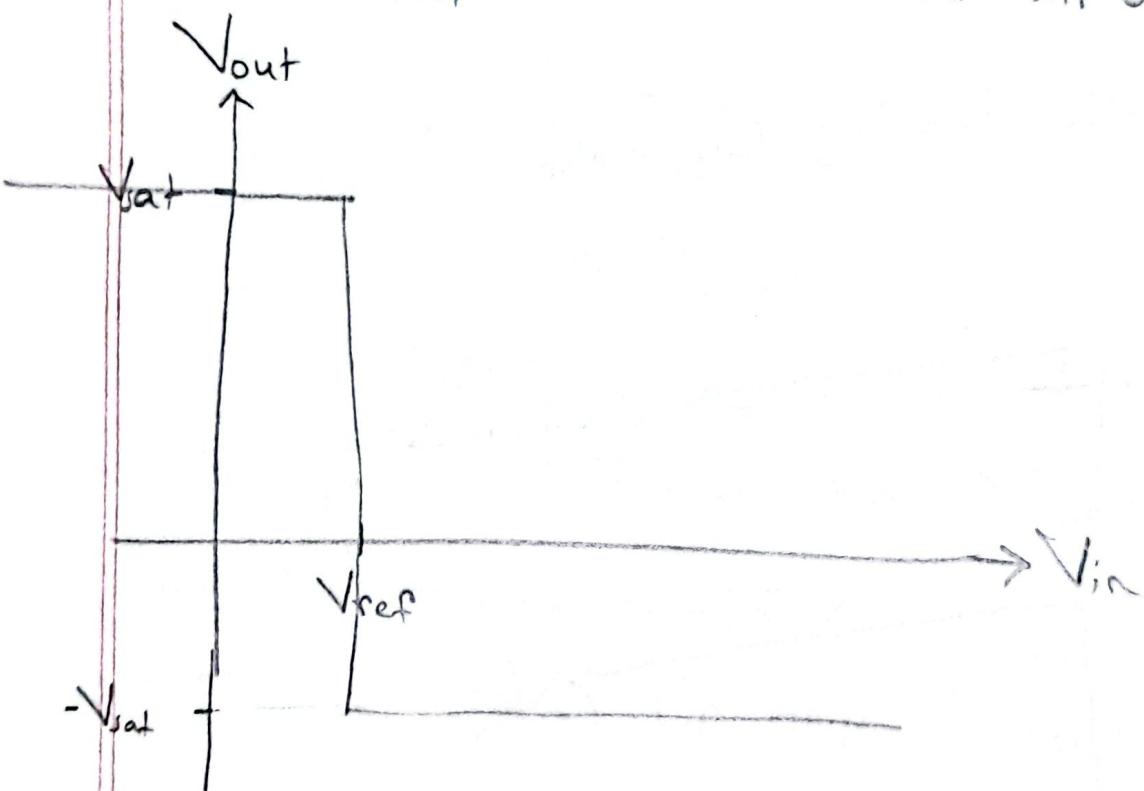If $V_{in} > V_{ref}$ then
 V_{out} will be V_{sat}^+ and
if $V_{in} < V_{ref}$ then
 V_{out} will be V_{sat}^-




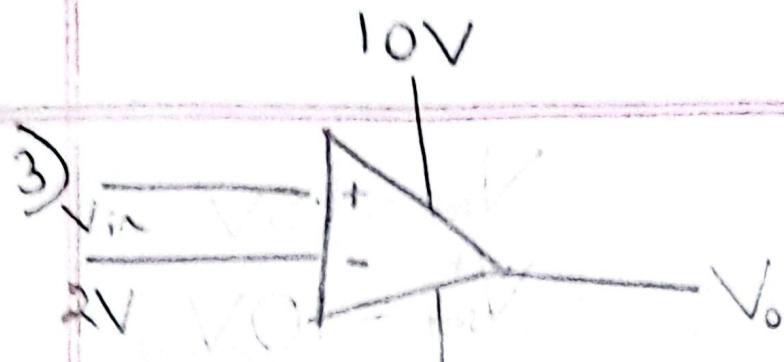


$$V_{out} = -10V$$

V_{out} ~~from~~

10

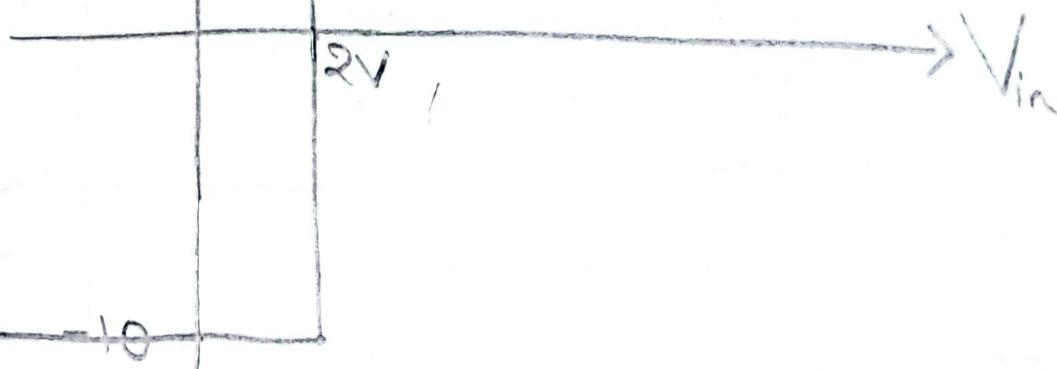

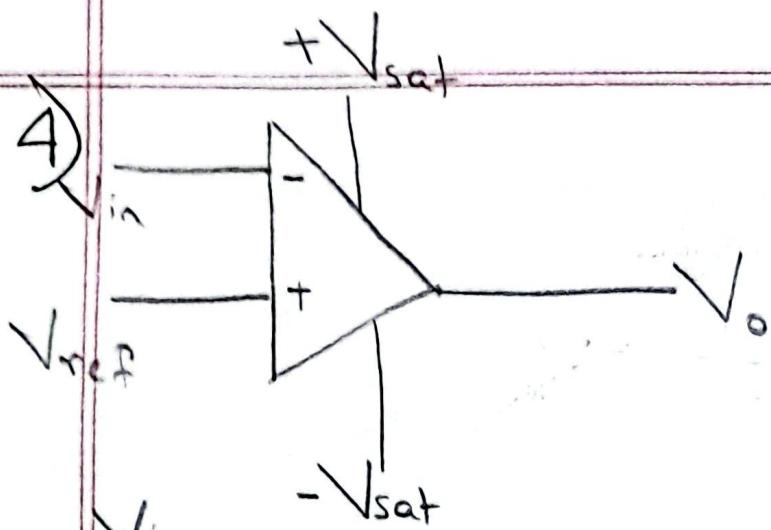


$$V_{ref} = 1.5V$$

$$+V_{sat} = 10V$$

$$-V_{sat} = -10V$$


$$V_{in} = 3\sin\omega t$$

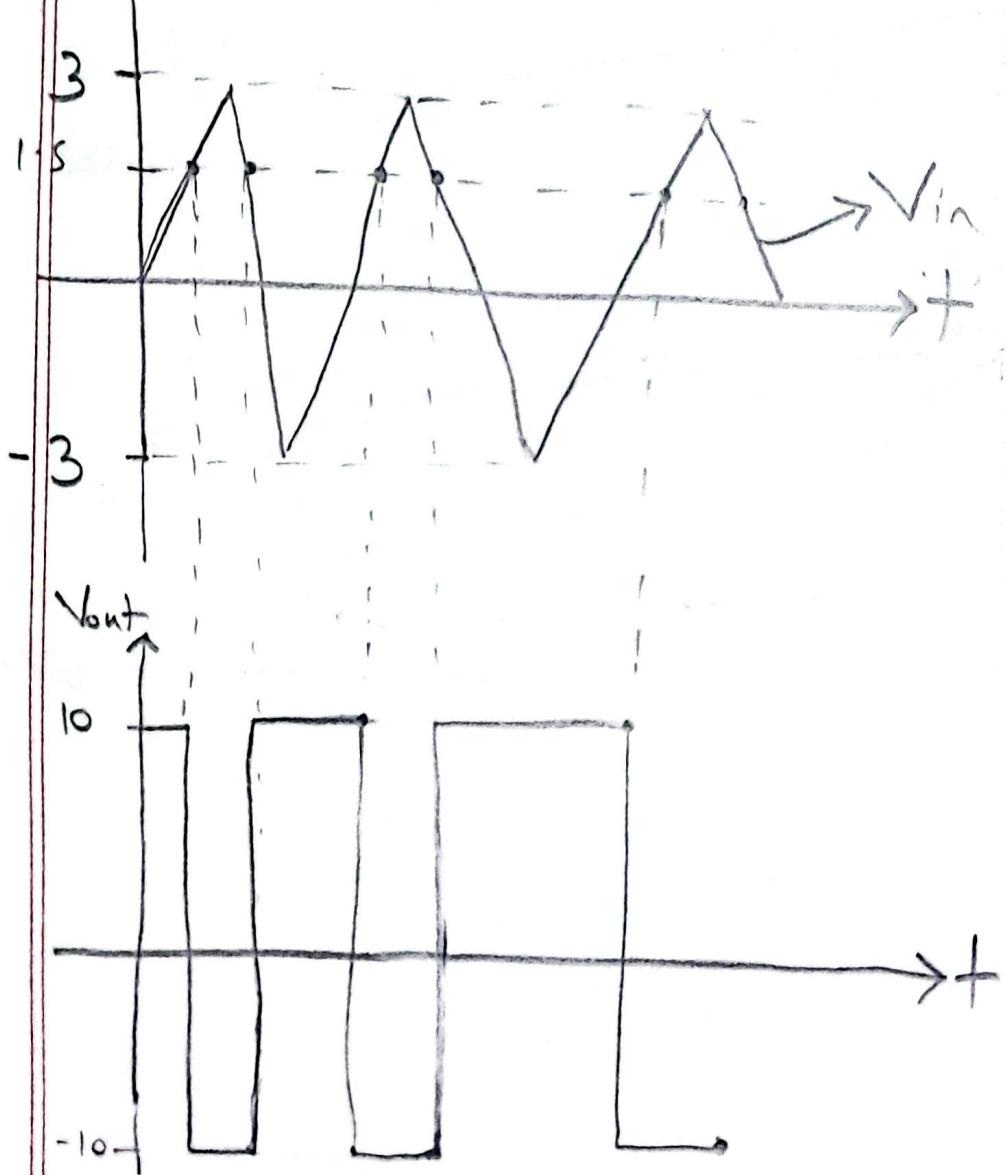

5) V_{out}

CEP-820

Plot graph

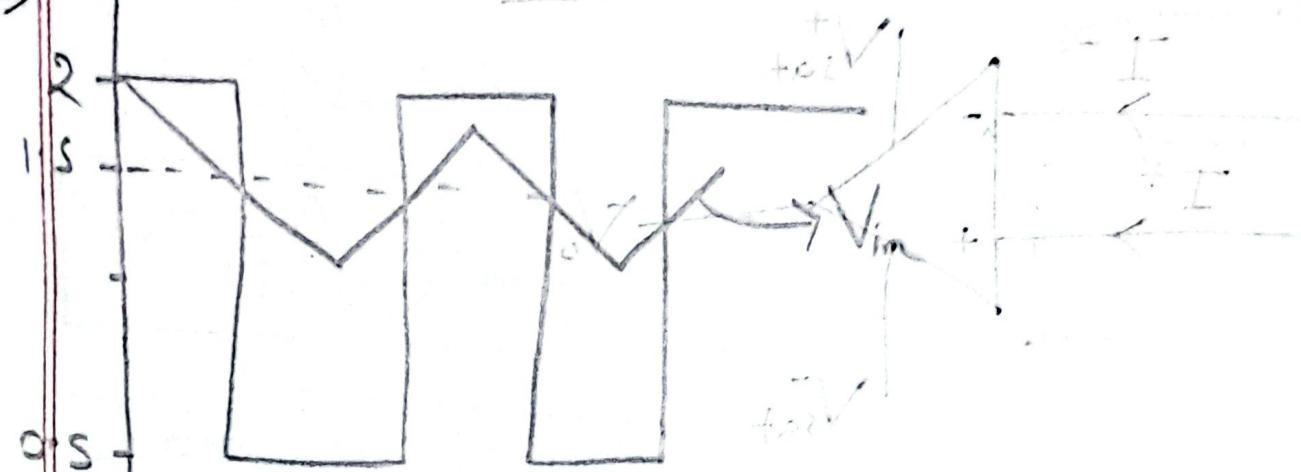


$$(100\text{fT}) \times 10 = A$$

$$(100\text{fT}) \times 10 = 1000$$

$$(100\text{fT}) 0 = 0$$

rearranged and solved


$$100\text{fT} = 1000$$

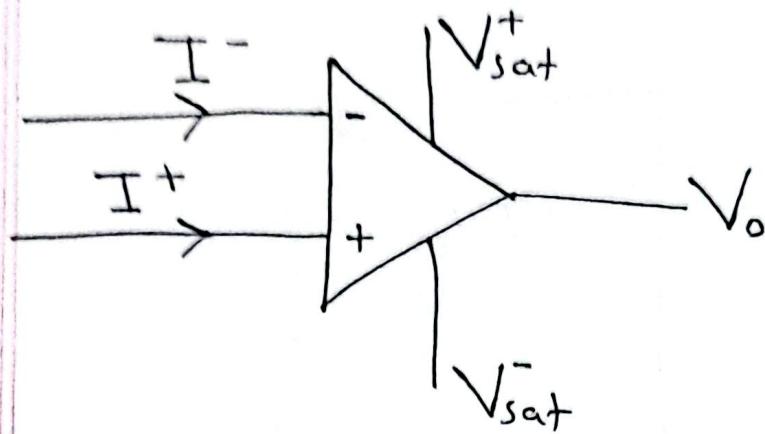Lecture-3

$$A = \infty \text{ (Ideal)}$$

$$R_{in} = \infty \text{ (Ideal)}$$

$$R_{out} = 0 \text{ (Ideal)}$$

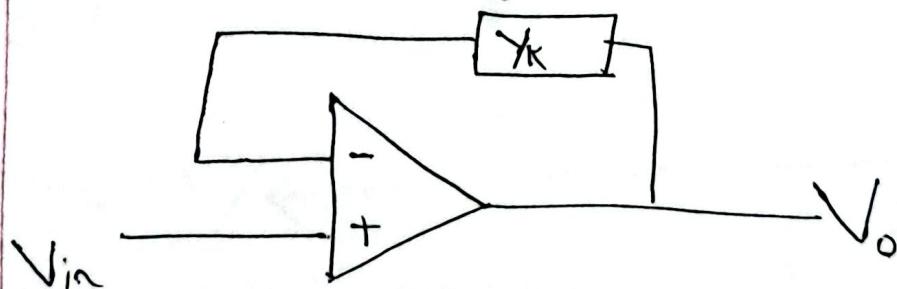Closed loop Configuration

$$V^+ = V_{in}$$

$$V^- = V_o/K$$

$$V_d = V^+ - V^-$$

$$V_d = V_{in} - \frac{V_o}{K}$$

$$\therefore V_o = AV_d$$

$$V_o = A \left(V_{in} - \frac{V_o}{K} \right)$$

$$V_o = \left(\frac{A}{1 + \frac{A}{K}} \right) V_{in}$$


$$\text{Ideal: } V_o = KV_{in}$$

$$V_{sat}^- < V_o < V_{sat}^+$$

$$V_o = V$$

$$I_o = I^+ = 0 \text{ (For closed loop)}$$

$$V^+ = V^- \text{ (closed loop)}$$

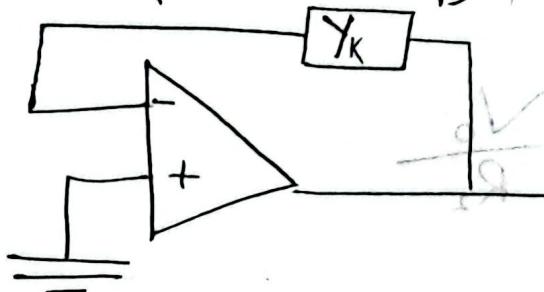


$$V = \frac{V_o}{1 + \frac{V_o}{K}} = \frac{V_o}{1 + \frac{V_o}{KV}} = \frac{V_o}{1 + \frac{V_o}{V}} = V$$

Since V^+ is OV, V^- will also be OV. ($V^+ = V^-$)

Mathematical Operation

Inverting Amplifier

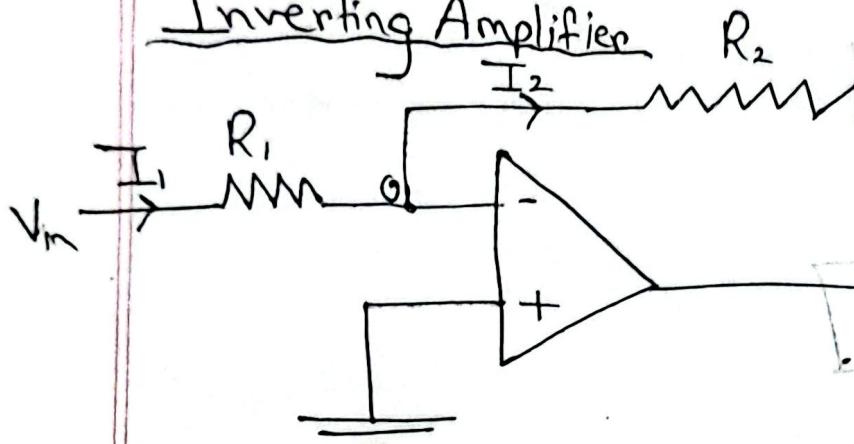

$$\frac{V_o}{V} A = \frac{V_o}{V} \cdot 1$$

$$(V_o - V) A = V_o$$

$$V_o \left(\frac{A}{A+1} \right) = V_o$$

$$\frac{V_o}{V} A = V_o \cdot \frac{1}{A+1}$$

$$\frac{V_o}{V} = \frac{1}{A+1}$$

$$V_o = V \cdot \frac{1}{A+1}$$

$$V^- = 0V$$

Since $V^+ = 0V$,

$$I_1 = \frac{V_{in} - 0}{R_1} = \frac{V_{in}}{R_1}$$

$$I_2 = \frac{V_o - 0}{R_2} = \frac{V_o}{R_2}$$

$$V_o = \left(-\frac{R_2}{R_1} \right) V_{in}$$

$(V_o - V) A = V_o \cdot \frac{1}{A+1} - V_o = V_o \cdot \frac{1}{A+1}$

1) If $V_o = y$ and V_{in} assuming positive sign

2) Form a circuit to form the equation $y = 4x$

Ans: Assuming $V_o = y$ and $V_{in} = x$

$$y = \left(-\frac{R_2}{R_1}\right)x$$

$$\therefore \frac{-R_2}{R_1} = 4$$

$$-R_2 = 4R_1$$

$$R_2 = -4R_1$$

$$\frac{V_o - 0}{R_1} = I$$

$$\frac{V_o - 0}{R_2} = I$$

Since resistance cannot be negative, V_o cannot be 0

\therefore Assuming $V_o = y$ and $V_{in} = -4x$

$$y = -\left(\frac{R_2}{R_1}\right)(-4x)$$

$$\therefore \frac{R_2}{R_1} = 4$$


$$R_2 = 4R_1$$

\therefore If $R_2 = 1\Omega$ and $R_1 = \frac{1}{4}\Omega$ the circuit can be formed.

$$P = \frac{V^2}{R}$$

$$4E = 4V$$

Non-inverting amplifier

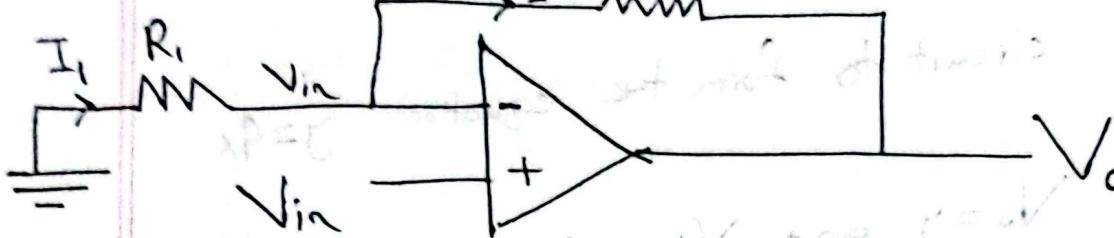

$$I_1 = \frac{V_o - V_{in}}{R_1}$$

$$I_2 = \frac{V_{in} - V_o}{R_2}$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

2) Form a non-inverting amplifier with equation $y = 4x$

Ans: Assuming $y = V_{out}$ and $x = V_{in}$

$$y = \left(1 + \frac{R_2}{R_1}\right) x$$

$\therefore R_1$ can be $1k\Omega$ and R_2


$$1 + \frac{R_2}{R_1} = 4$$

can be $3k\Omega$

$$\frac{R_2}{R_1} = 3$$

$$R_2 = 3R_1$$

Inverting Adder

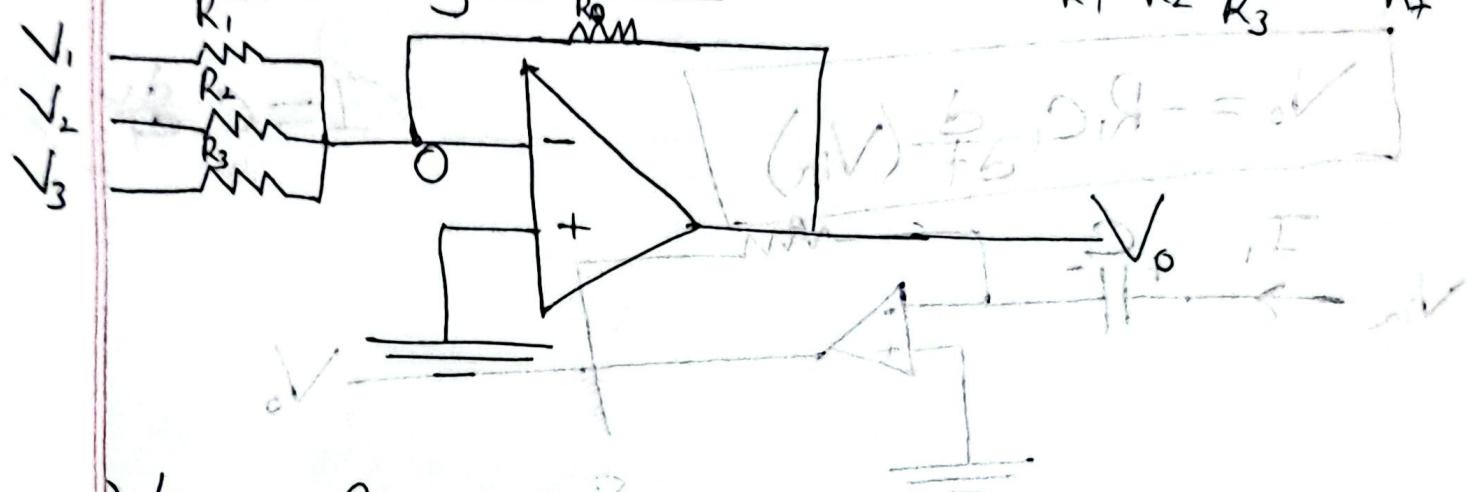

$$V_0 = -\frac{R_o}{R_1} V_1 - \frac{R_o}{R_2} V_2 - \frac{R_o}{R_3} V_3$$

$$V_0 = \frac{1}{R_f} (R_o V_1 + R_o V_2 + R_o V_3)$$

$$\textcircled{3} \quad J = -2x + 3y - 4z$$

$$= -(2x - 3y + 4z)$$

$$y = -(2x - 3y + 4z) \quad (2x - 3y + 4z) = (V) \frac{b}{f_0}$$

$$2 = \frac{R_o}{R_1}$$

$$2R_1 = R_o$$

$$2R_o - 2R_1 = 0 - (1)$$

$$\frac{R_o}{R_2} = -3$$

$$R_o = -3R_2$$

$$R_o + 3R_2 = 0 - (1)$$

$$\frac{R_o}{R_3} = 4 \quad [0] =$$

$$R_o - 4R_3 = 0 - (1)$$


$$(2x - 3y + 4z) = V$$

$$f_{min}(V) =$$

Differentiator


$$V_o = -R_1 C_1 \frac{d}{dt} (V_{in})$$

$$I = C \frac{dV}{dt}$$

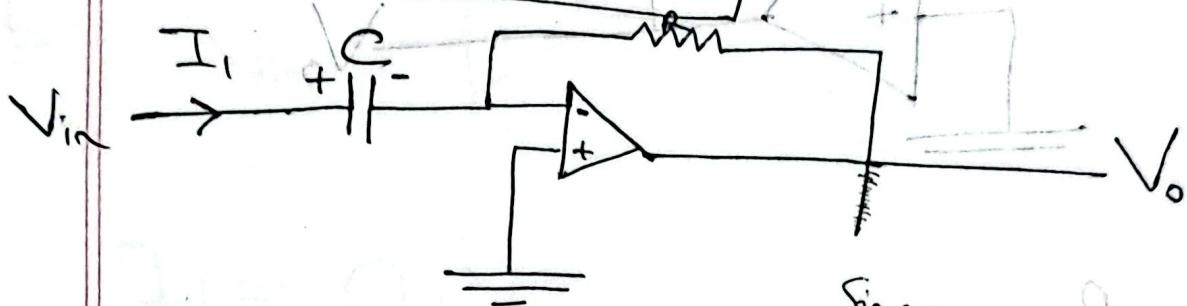

Integrator

$$V_{in} = 10 \cos 2t$$

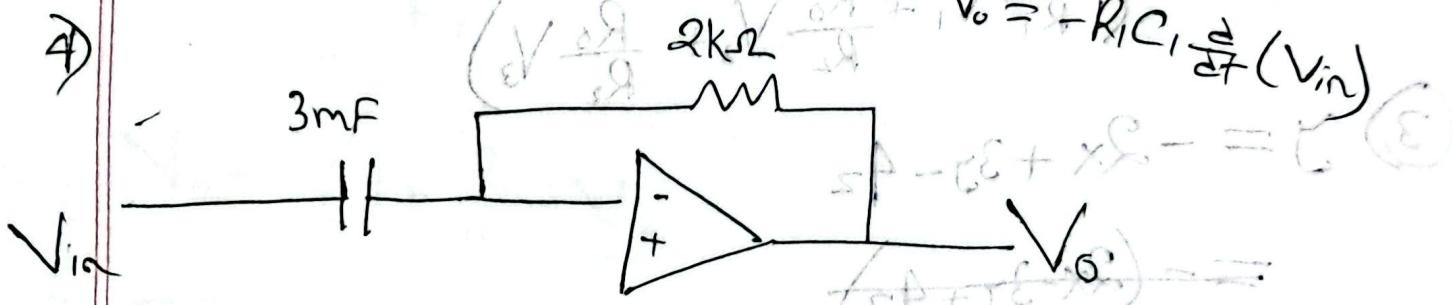

$$\frac{d}{dt} (V_i) = \frac{d}{dt} (10 \cos 2t)$$

$$= 10 \left[-2 \sin 2t \right]$$


$$= -20 \sin 2t$$

$$\begin{aligned} V_o &= - (2 \times 10^6 \times 3 \times 10^{-3} \times -20 \sin 2t) \\ &= 120 \sin 2t \end{aligned}$$

$$E = \frac{2}{3} \times 10^6$$

$$900 = 9$$

$$(1) \rightarrow 0 = 300 + 9$$

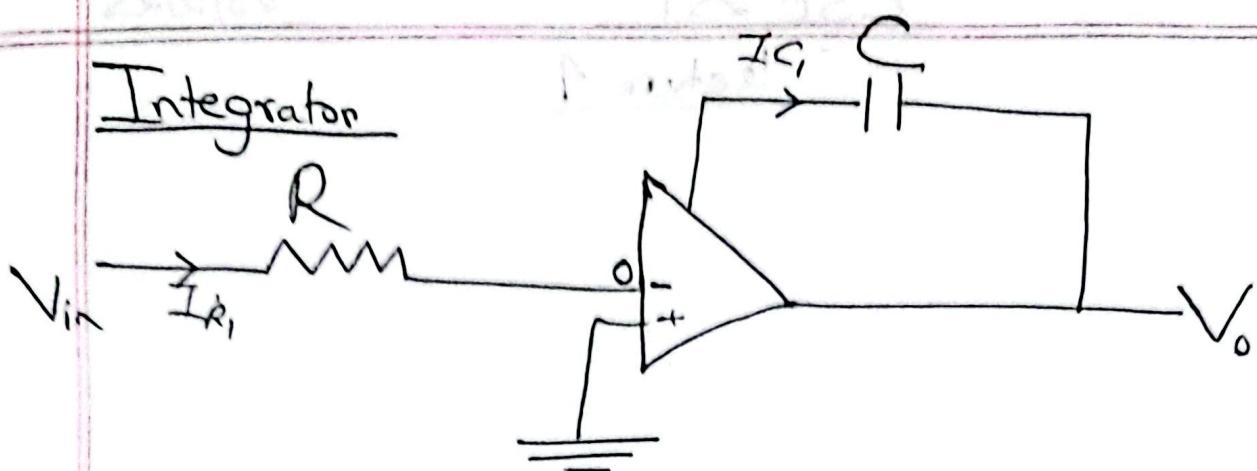

$$V_0 = \frac{-1}{RC} \int V_{in} dt$$

∴

Since

$$IR_1 = \cancel{I_C} + IC_1$$

$$\frac{V_{in} - 0}{R_1} = C \frac{d}{dt} (V_0) (0 - V_0)$$

$$\frac{V_{in}}{R_1} = C_1 \left(\frac{1}{dt} V_0 \right) C_1 \left(\frac{1}{dt} (0 - V_0) \right)$$

$$\frac{V_{in}}{R_1 C_1} = \frac{1}{dt} (-V_0)$$

$$\therefore -V_0 = \int \frac{V_{in}}{R_1 C_1} dt$$

$$V_0 = \frac{-1}{R_1 C_1} \int V_{in} dt$$



lecture-5

$$I = f(V)$$

$$I = C \left(\frac{dV}{dt} \right)$$

$$V = f(I)$$
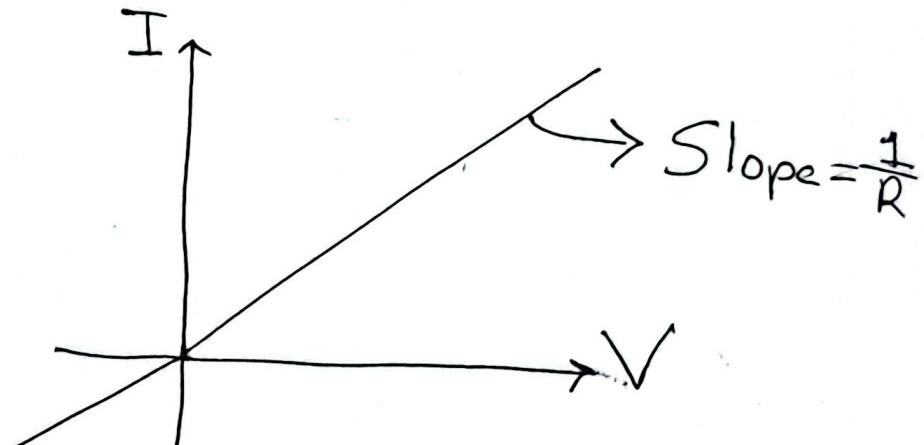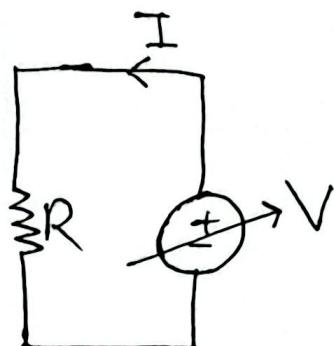
$$\text{Inductor} = V = L \frac{dI}{dt}$$





$$I = V/R$$

$$y = mx + c$$



$$I = \left(\frac{1}{R} \right) V + 0$$



$$\therefore m = \frac{1}{R} \text{ and } R = \frac{1}{m}$$

Current Source



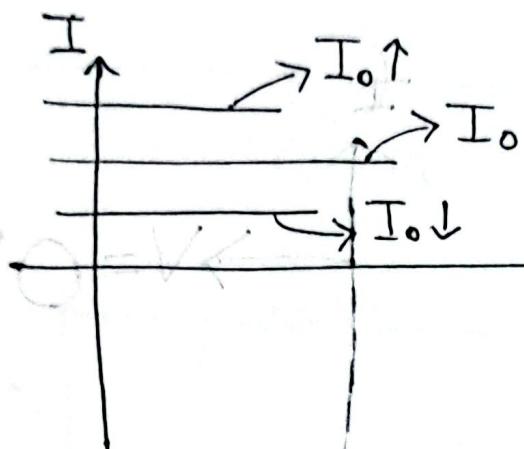
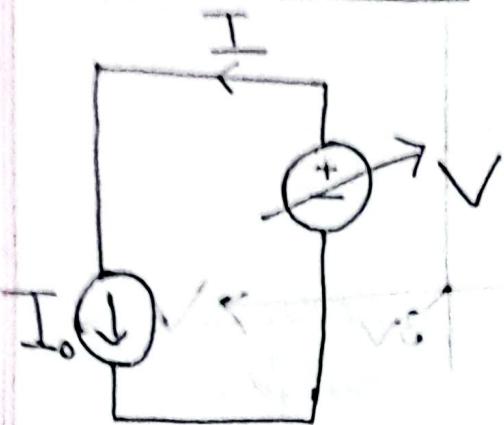


Voltage Source

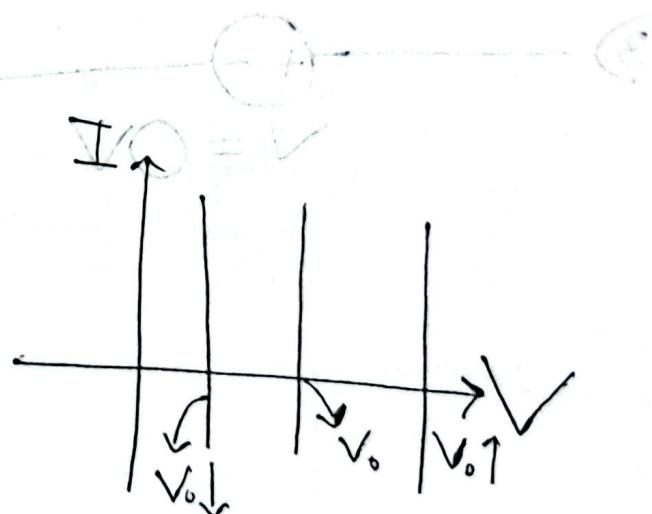
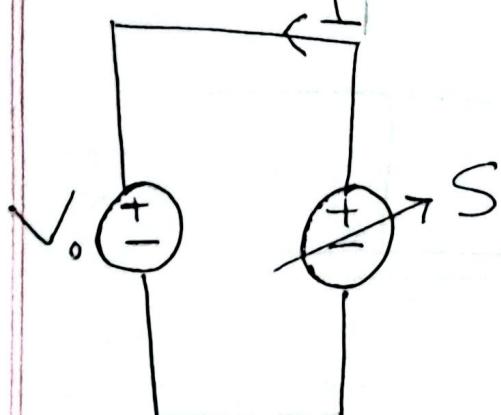


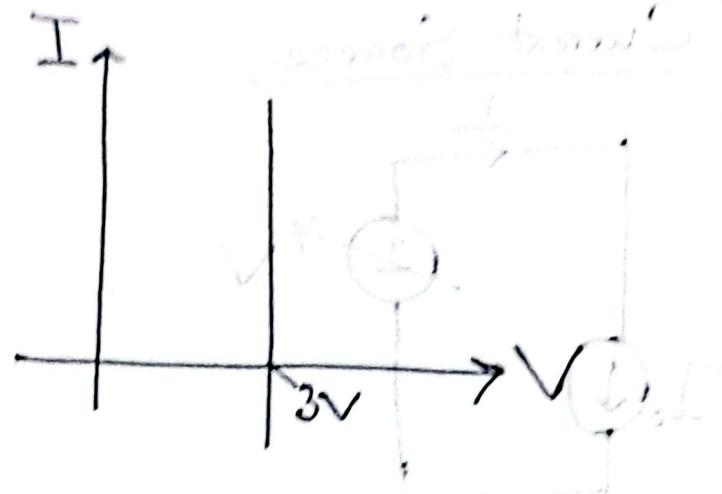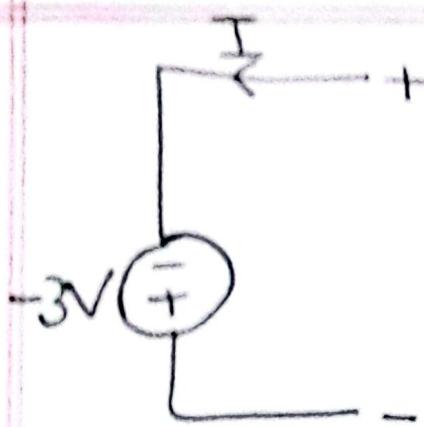




Short Circuit

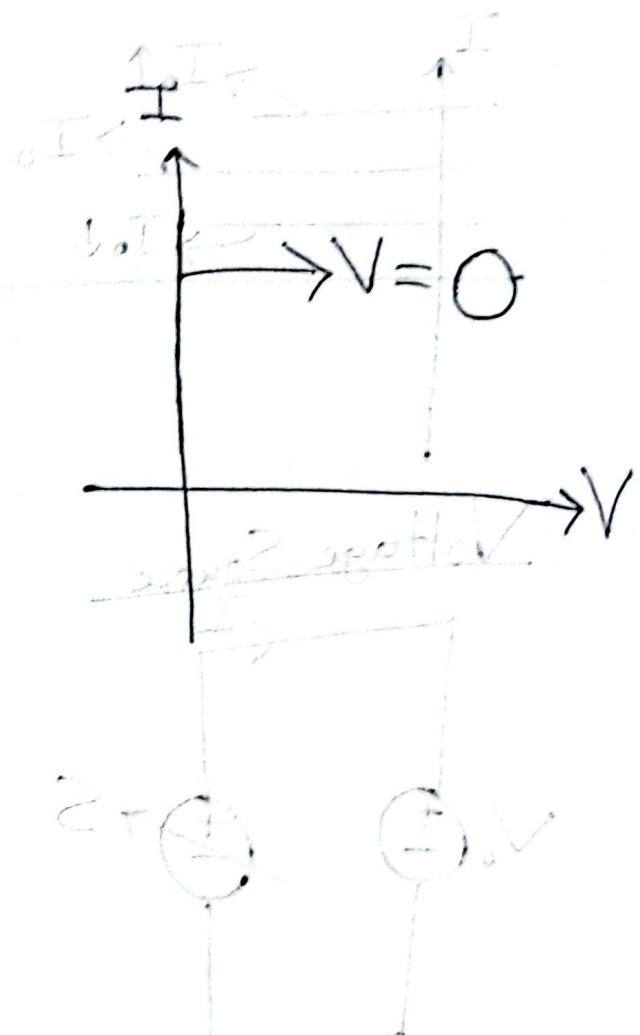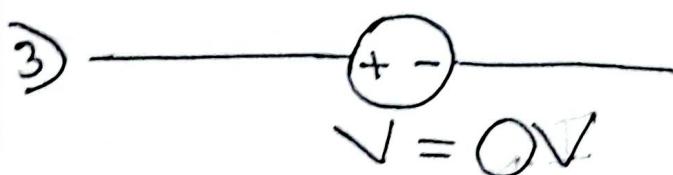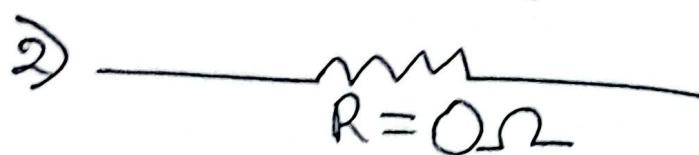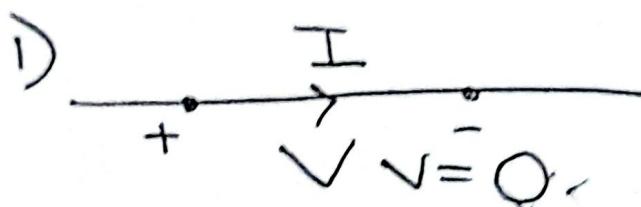

Open Circuit

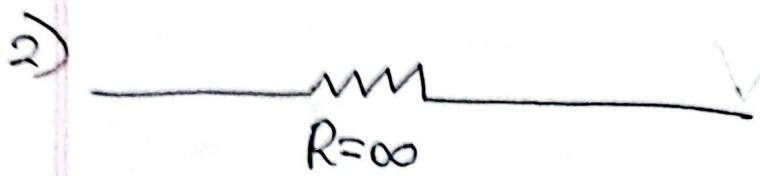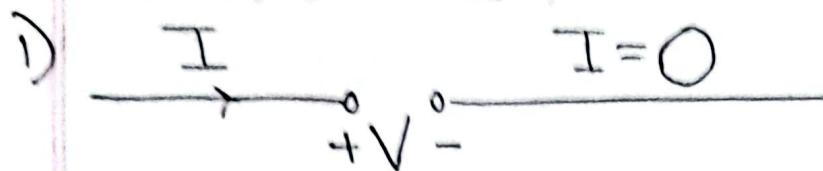


graph and example of A Ω

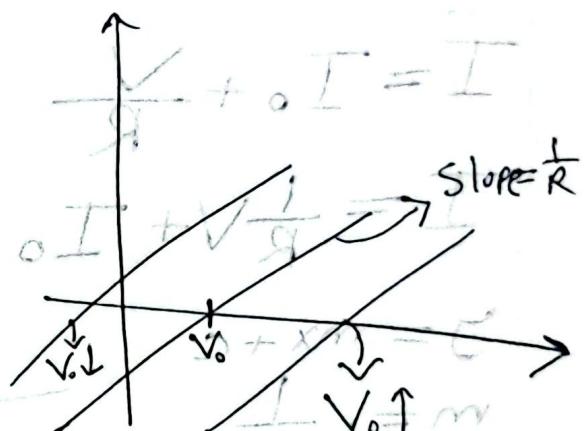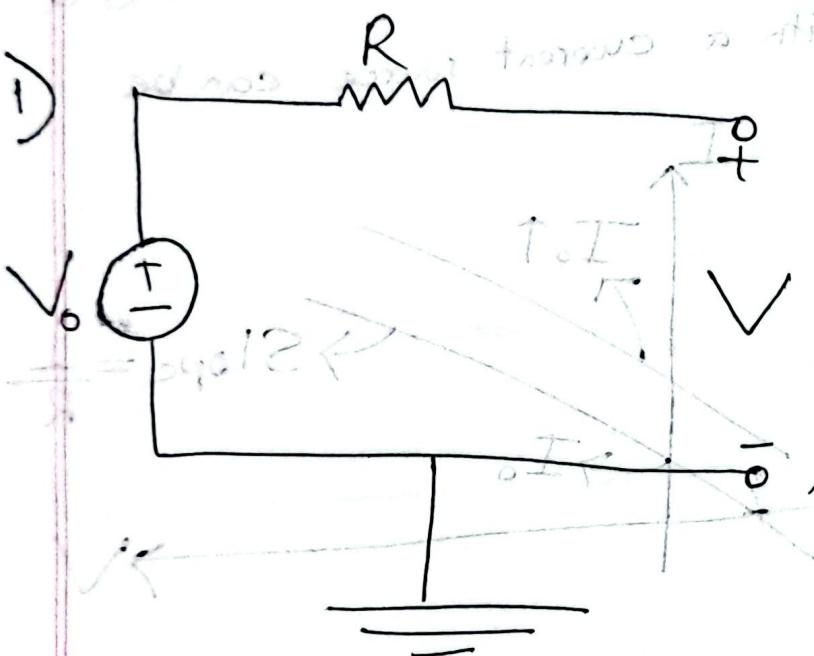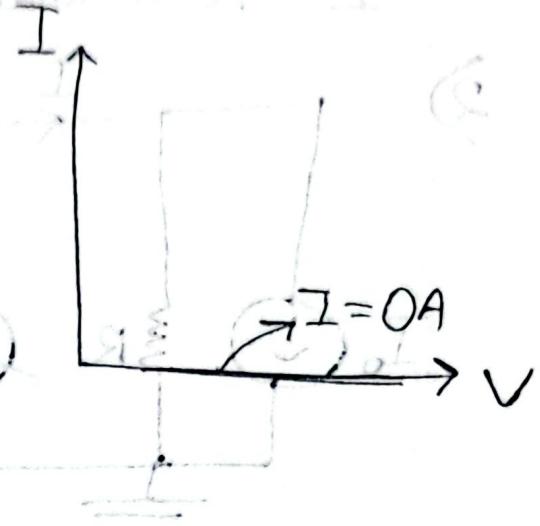

$$I = \frac{V - V_0}{R}$$


$$I = \frac{1}{R}V - \frac{V_0}{R}$$

$$C = -\frac{V_0}{R}$$

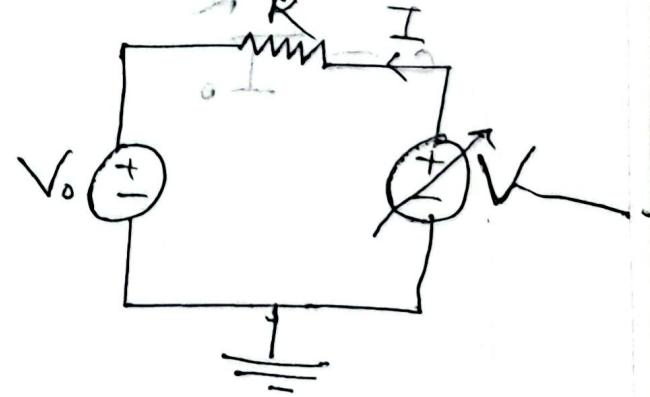

- If R is changed then slope decreases.

2)

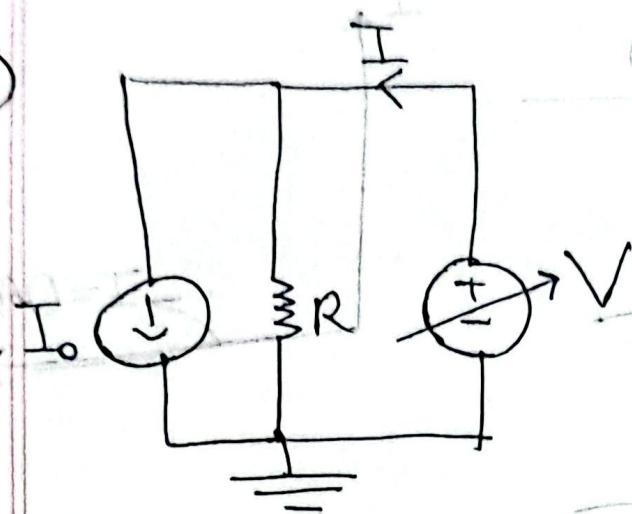

$$Q = I$$

$$-V = V$$

$$Q = R$$

- A resistor parallel with a voltage source and a resistor in series with a current source can be removed.


$$I = I_0 + \frac{V}{R}$$

$$I = \frac{1}{R}V + I_0$$

$$y = mx + c$$

$$m = \frac{1}{R}$$


$$c = I_0$$

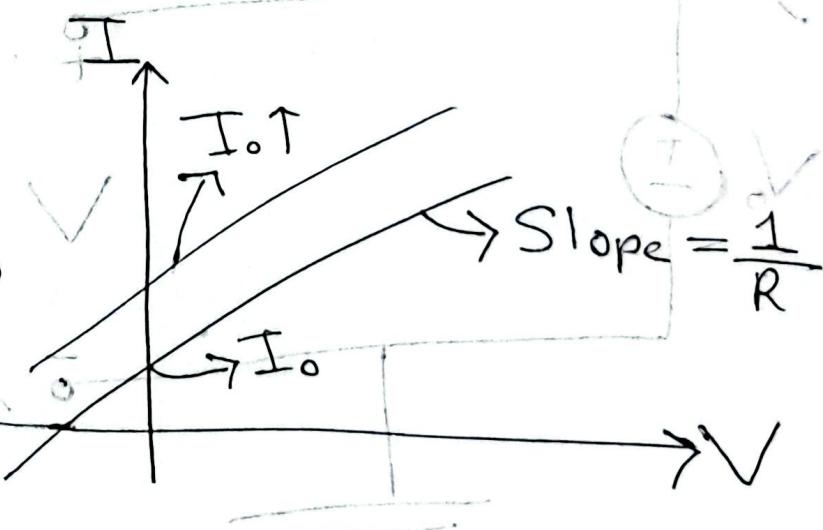


$$\frac{V - V}{R} = I$$



$$\frac{V - V}{R} = I$$

$$\frac{V - V}{R} = c$$

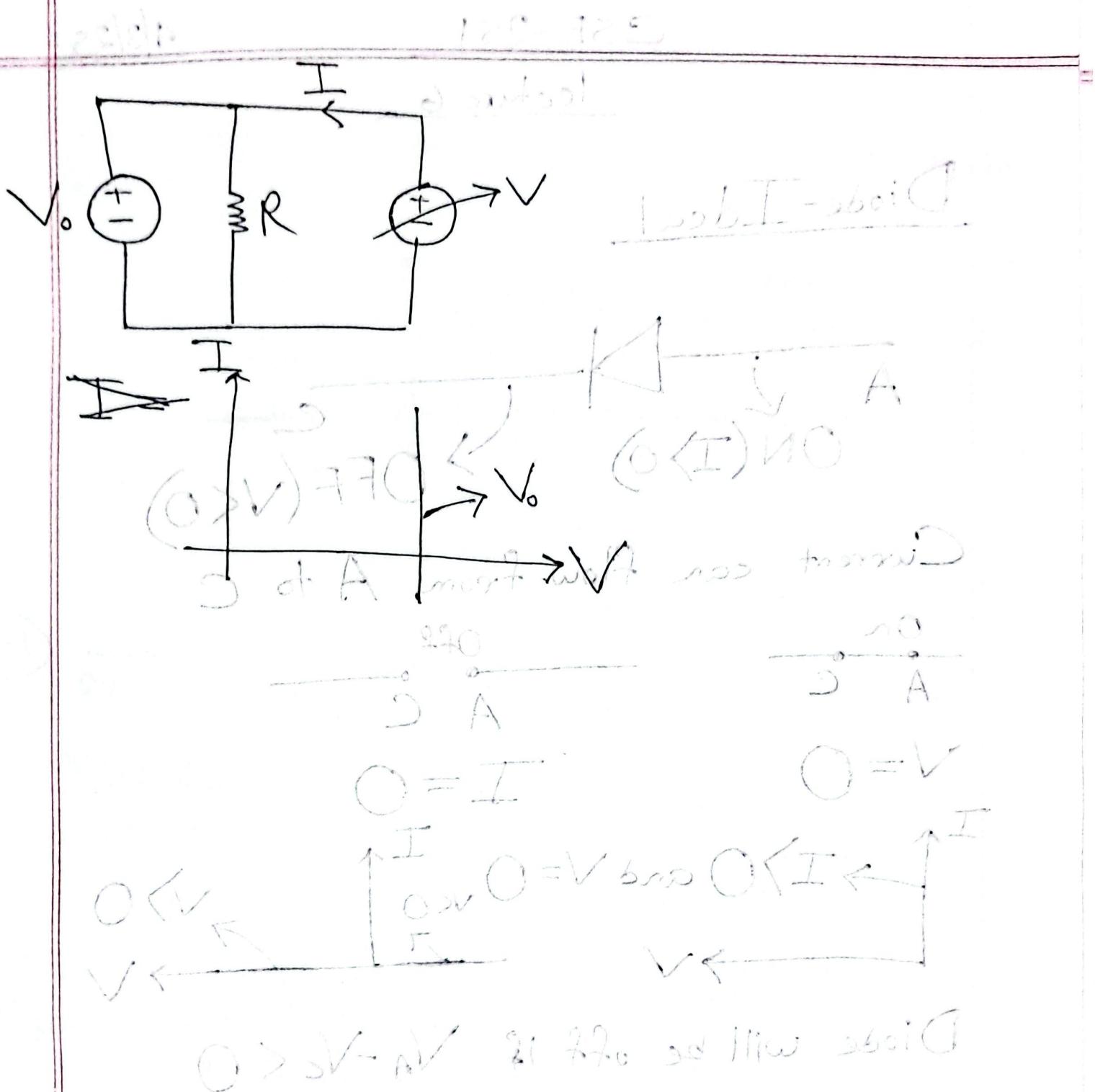


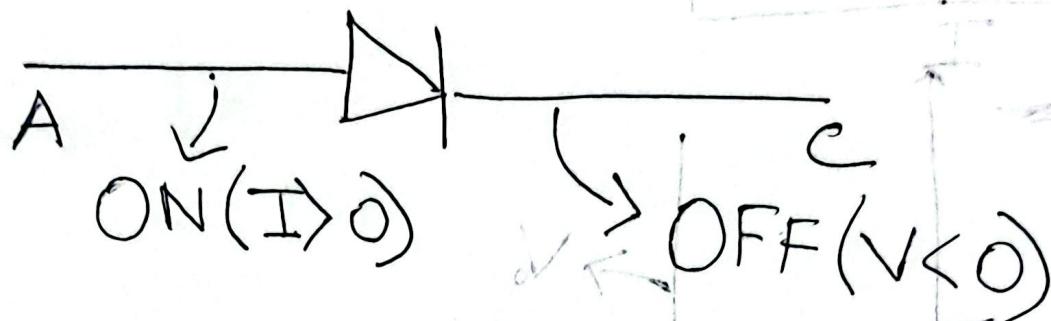
lecture-6Diode-Ideal

Current can flow from A to C

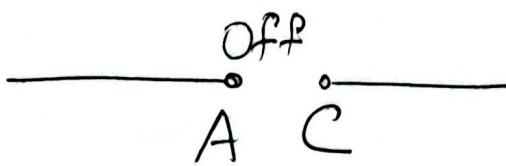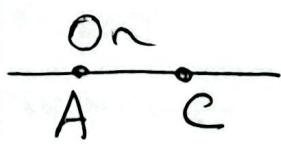



$$V = 0$$

$$I = 0$$

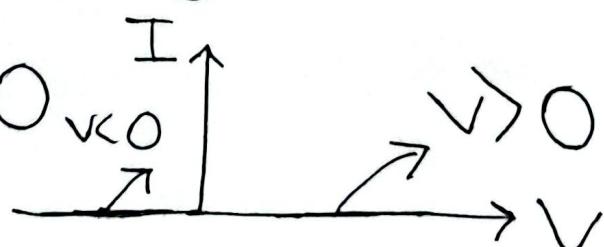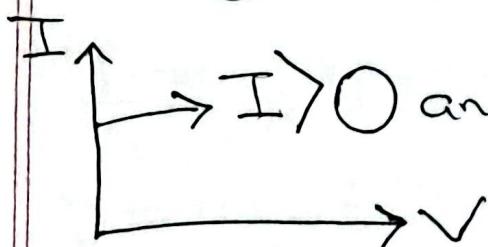

Diode will be off if $V_A - V_C < 0$

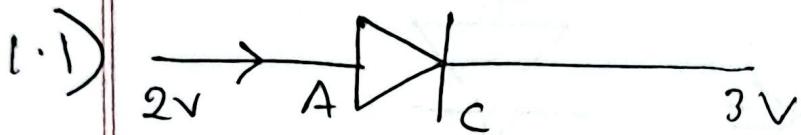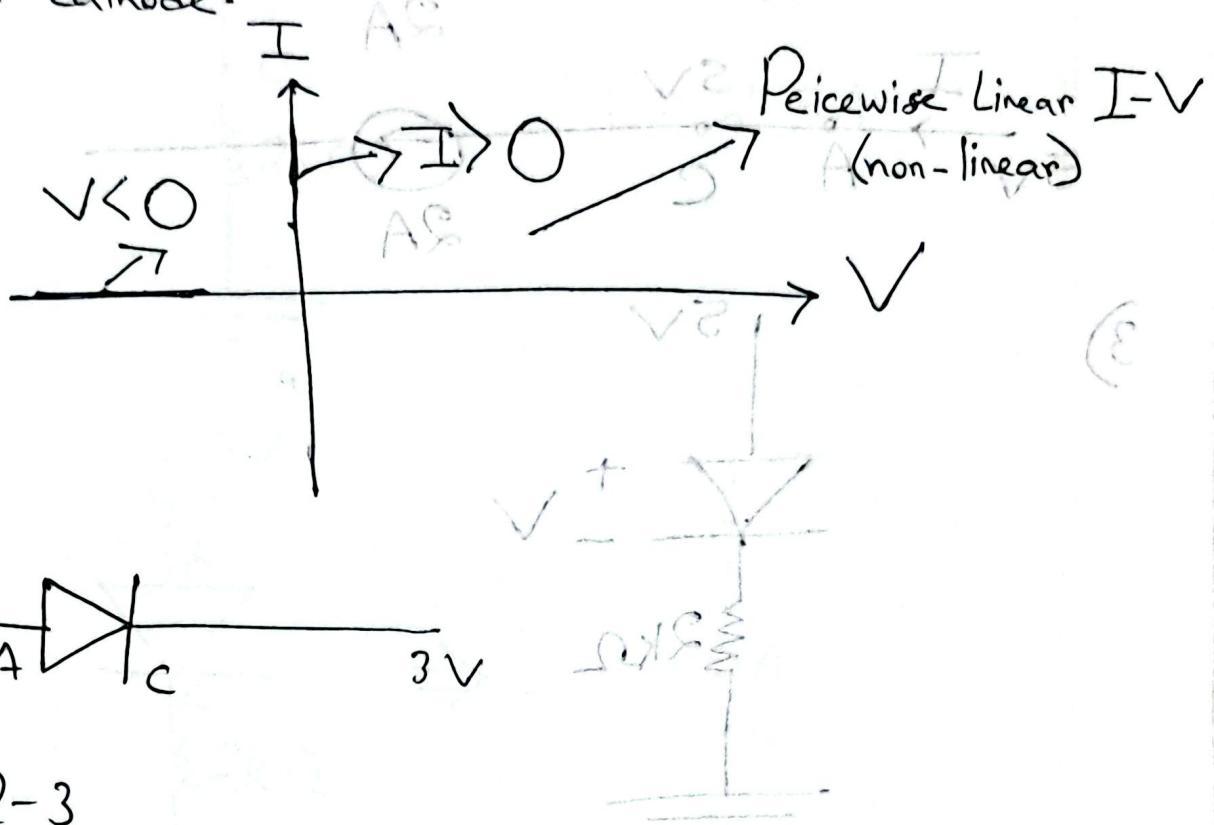• Stoppage sign jeidike ; sheidike cathode are opposite side a cathode.



$$V = 2 - 3 \\ = -1 < 0$$




\therefore Diode is off and $I = 0A$



$$V = V_A - V_C \\ = 3 - 2 \\ = 1V > 0$$

$$V2 =$$

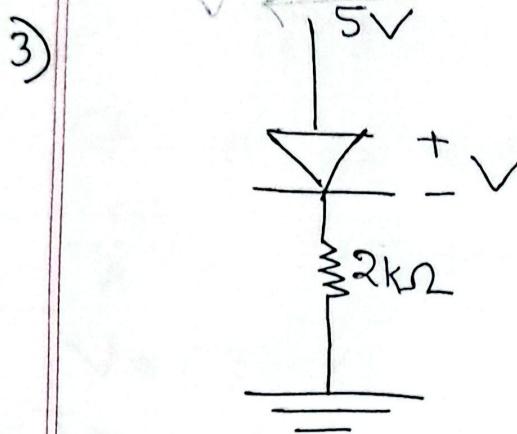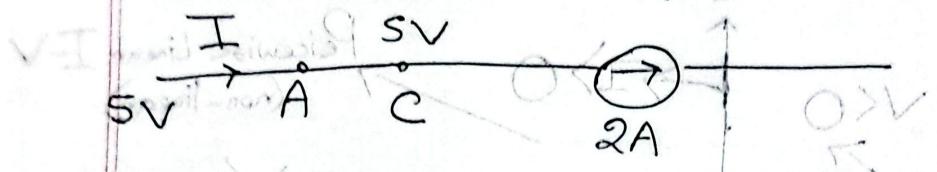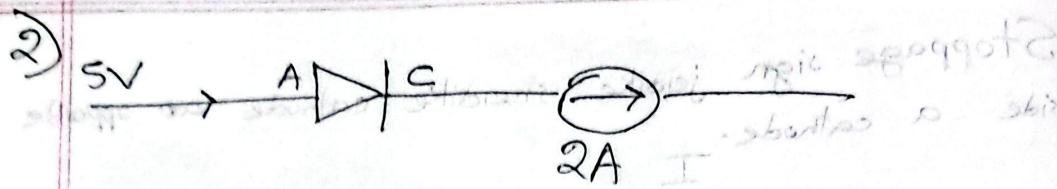• Since there is no resistor I cannot be calculated hence circuit is invalid.




Voltage of anode is 5V and voltage of cathode is 0V. Hence.

$$\begin{aligned} V &= 5 - 0 \\ &= 5V \end{aligned}$$

Since the diode is ON,

$$\begin{aligned} V - A &= V \\ 5 - 5 &= 0 \\ 0 &= 0 \end{aligned}$$


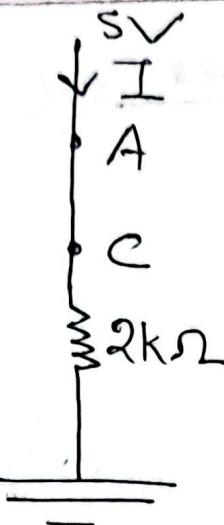
$$\begin{aligned} V &= V_A - 1 \\ &= -3 \\ &= -3 \end{aligned}$$



$$I = \frac{5}{2} \text{ mA}$$

$$I = 2.5 \text{ mA}$$

Ans

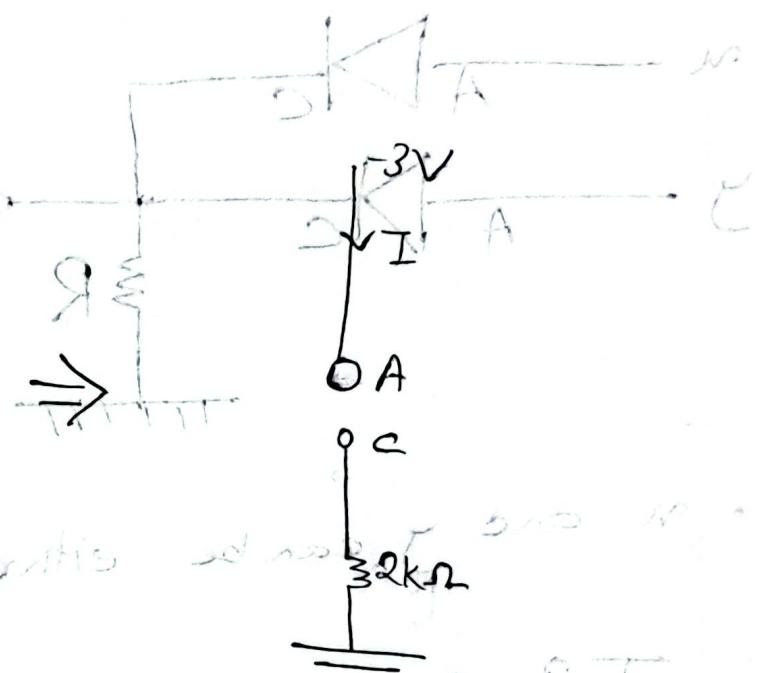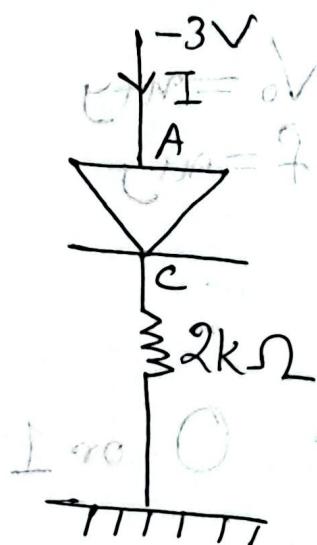

$$V = V_A - V_C$$

$$= -3 - 0 \text{ volt}$$

$$= -3$$

Since Diode is off, $I = 0 \text{ A}$


Q	1	2	3
1	0	0	0
2	2	0	2
3	2	2	0
4	2	2	2

Logic Gate with Diodes

AND OR = NOT

$$\text{and} \quad \text{OR} = \overline{\text{I}}$$

OR

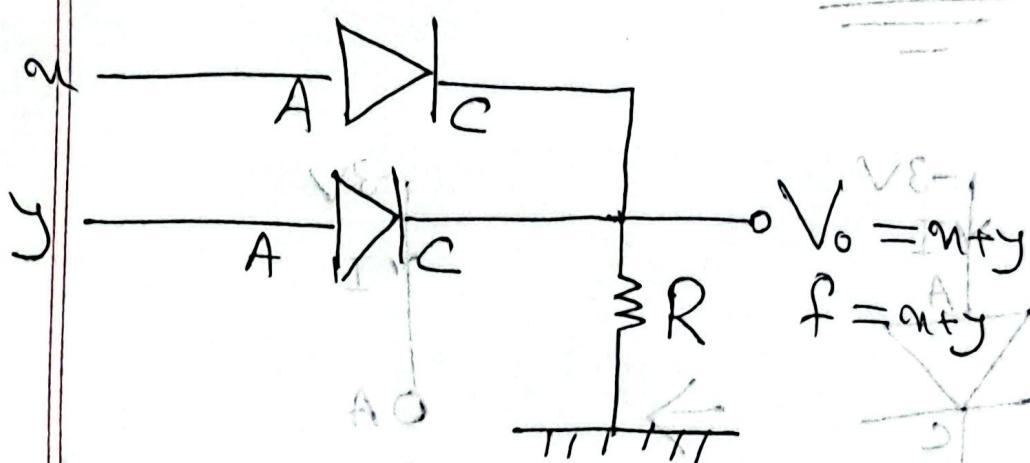

- a and y can be either 0 or 1

- If 5V then on else 0V then off


- If a is off or y is 0V then the diode will be off else on.

a	y	V_o
0	0	0
5	0	5
0	5	5
5	5	5

- If $f = \max(x, y, z)$ then the answer will be 1A.

$\max(x, y, z)$


5)

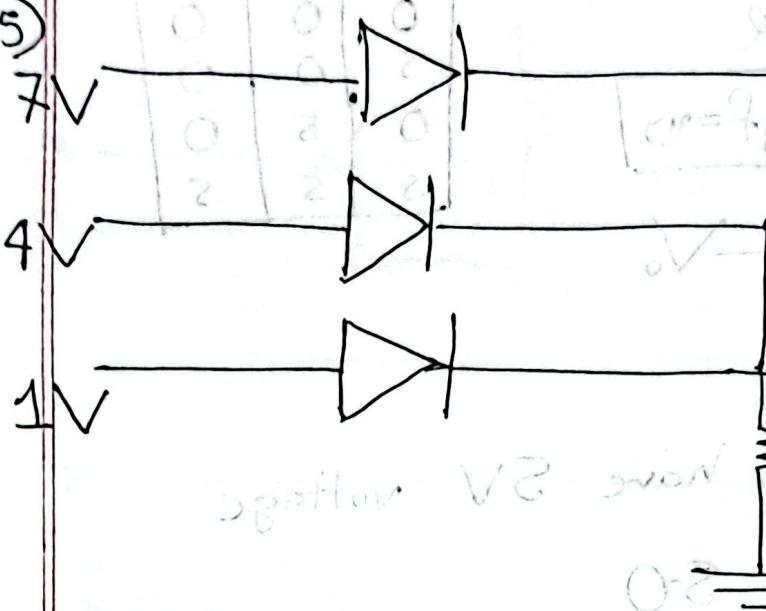

bottom V_2 and R is the load A .
 $0V$ is the common ground.

- x, y, z (as said) $0 \leq x =$
 x, y, z can not be on at the same time. Only the
 diode with the maximum voltage will remain on. (7V for this
 case). (as said) $0 =$

AND Gate

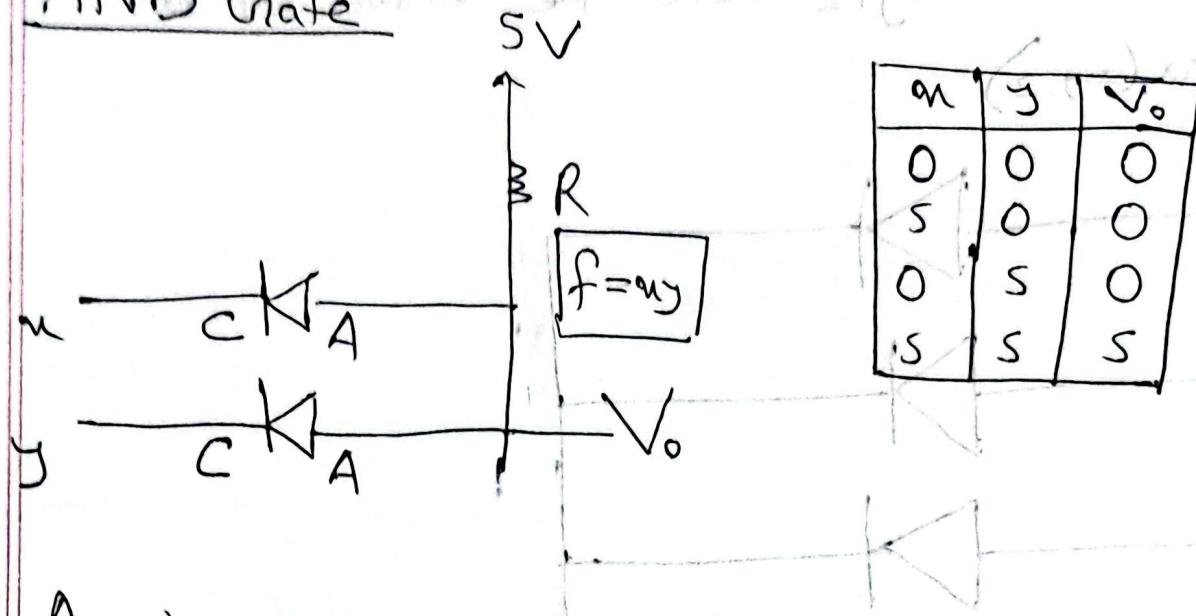


- Anode will always have $5V$ voltage
- When u is 0 , $V = 5-0$
 $= 5 > 0$ (Diode on)

When u is 5 , $V = 5-5$
 $= 0$ (Diode off)

6) Design the circuit:

$$f = (x_j) + j + z \quad 5V$$


using logic


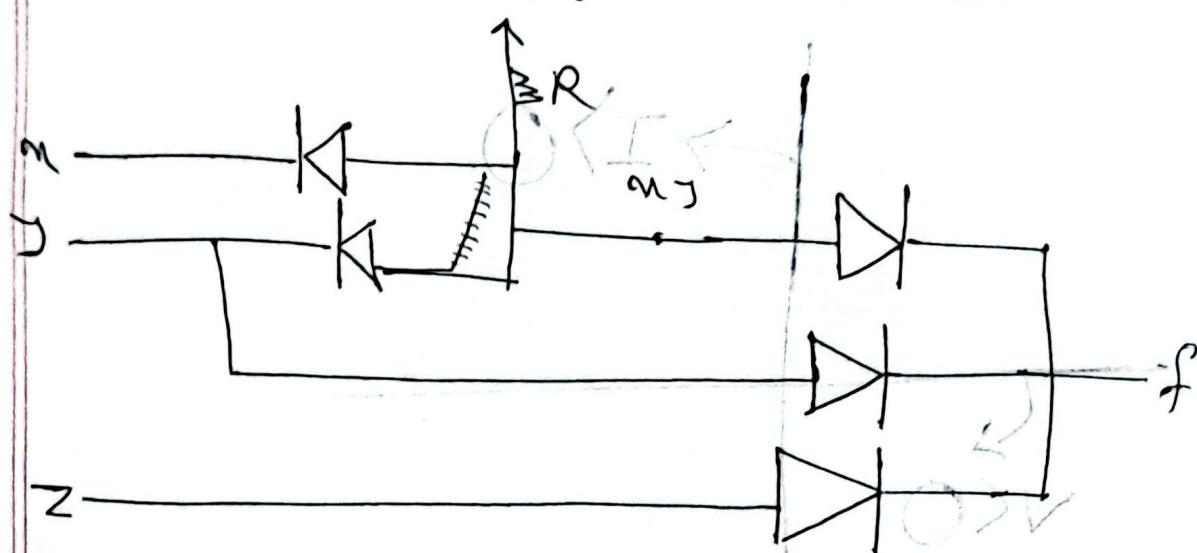


$$f = y(a+1) + z$$

$$f = \bar{a}j + a\bar{j} + z$$


using logic

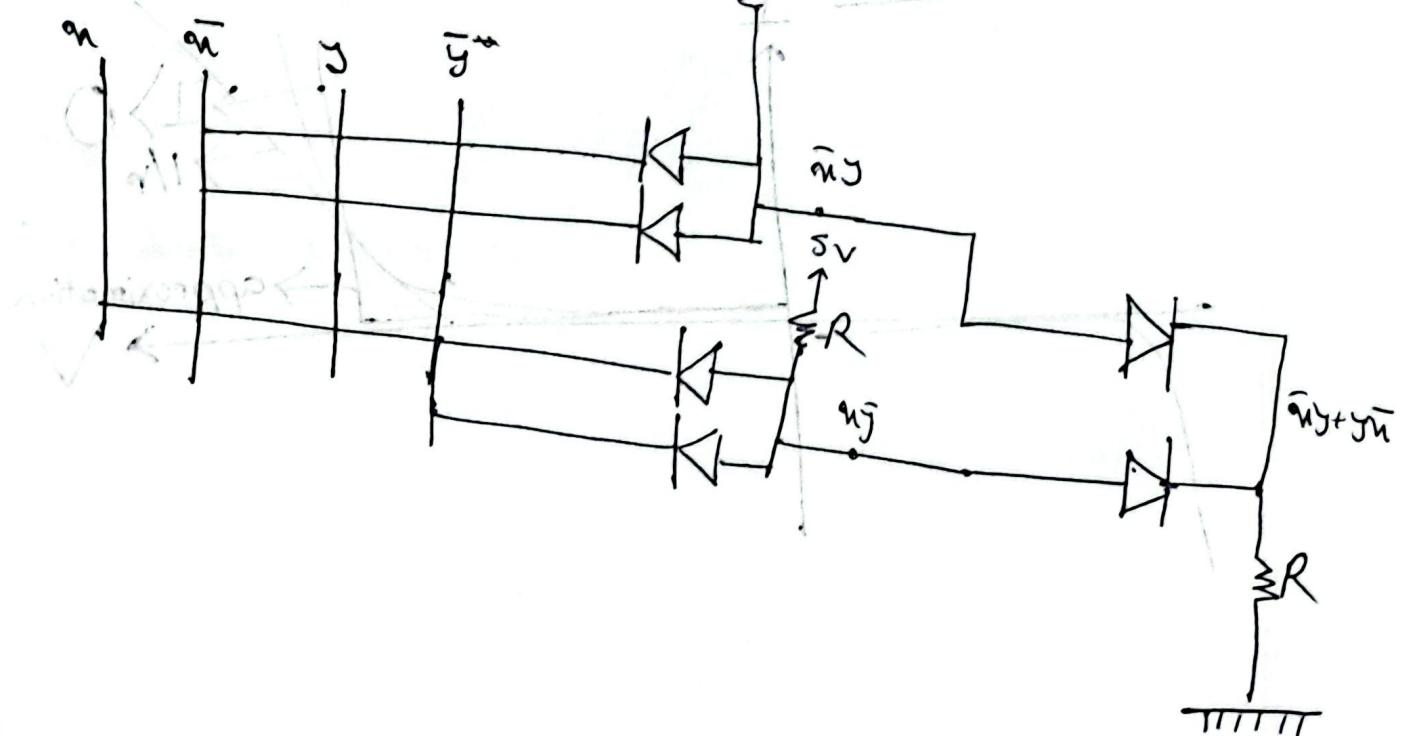

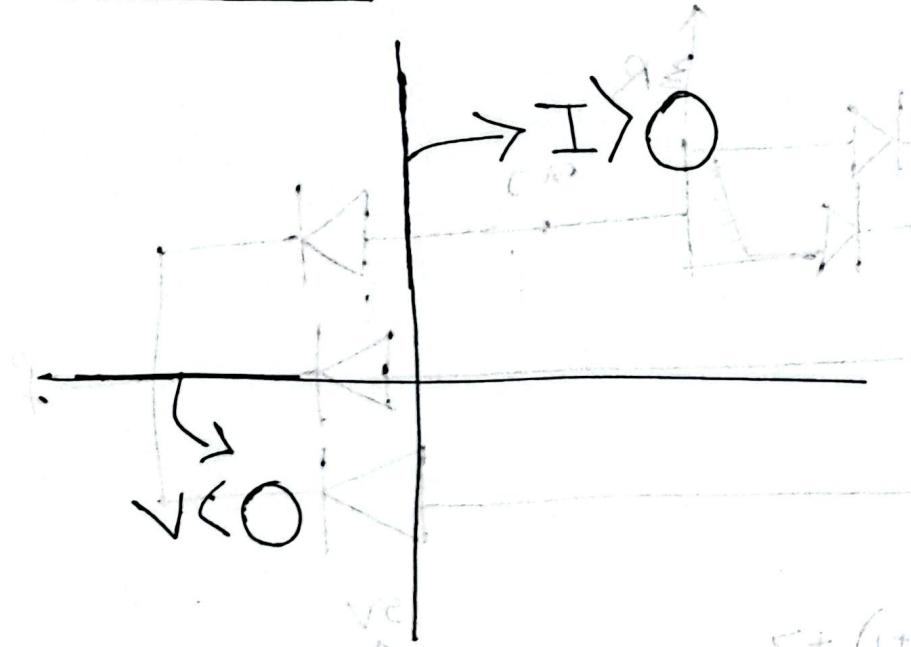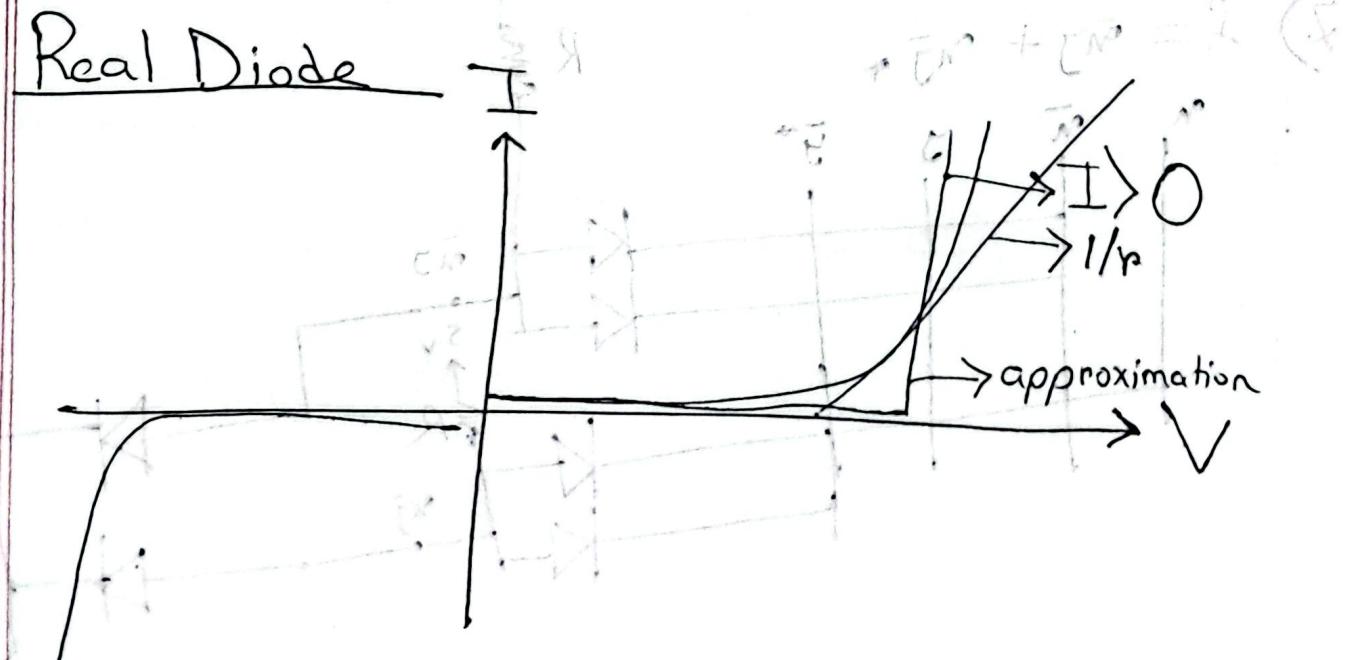Lecture-7Ideal DiodeReal Diode

Approximation of Real Diode

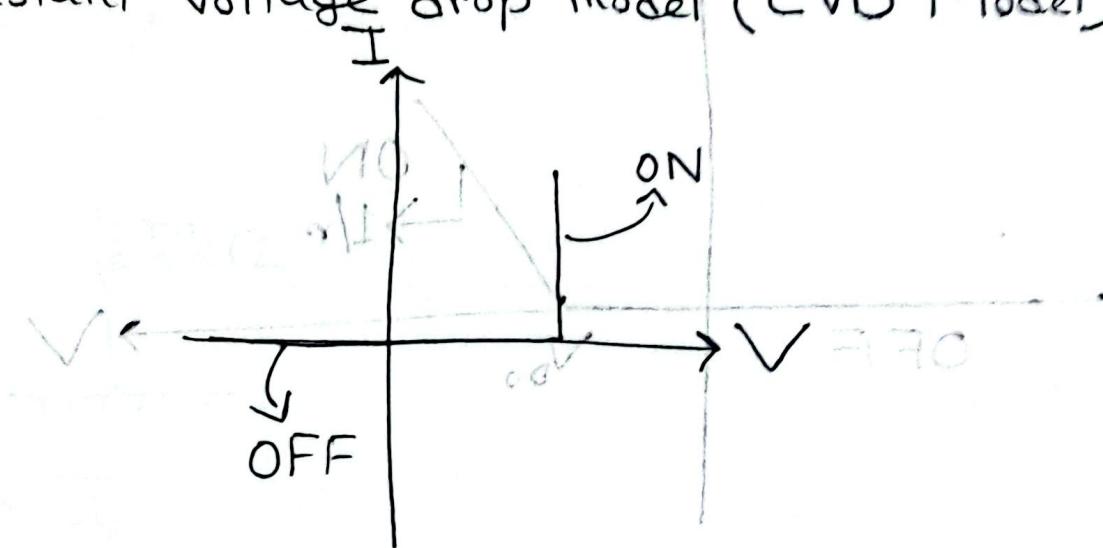i) Constant voltage drop model (CVD Model)



If diode is on, diode can be replaced by V_{D0}



$$V_{D0} = 0.7 \text{ (Si)} \text{ or } 0.2 \text{ (Ge)}$$


If diode is ON then,

$$I > 0$$

If diode is off then,


$$V < V_{D0}$$

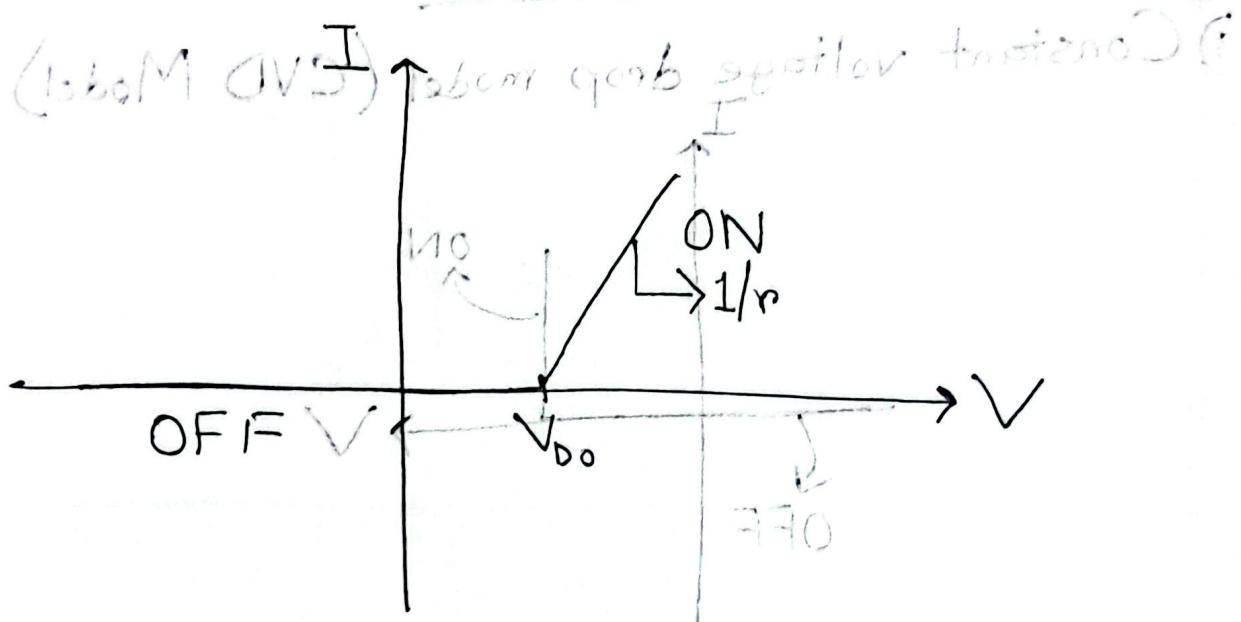ii) Constant voltage drop + resistance (CVD+rm model)



If ON,

$V > V_{D0}$ and $I > 0$

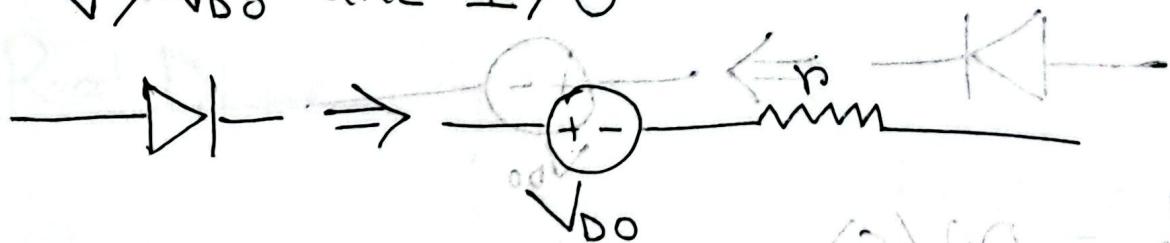

If OFF,

$$(iD)_{<0} \approx (iC)_{<0} = 0V$$

$V < V_{D0}$



and NO in shunt $\frac{1}{r}$

OK



and $\frac{1}{r}$ is shunt $\frac{1}{r}$

$$0V > V$$

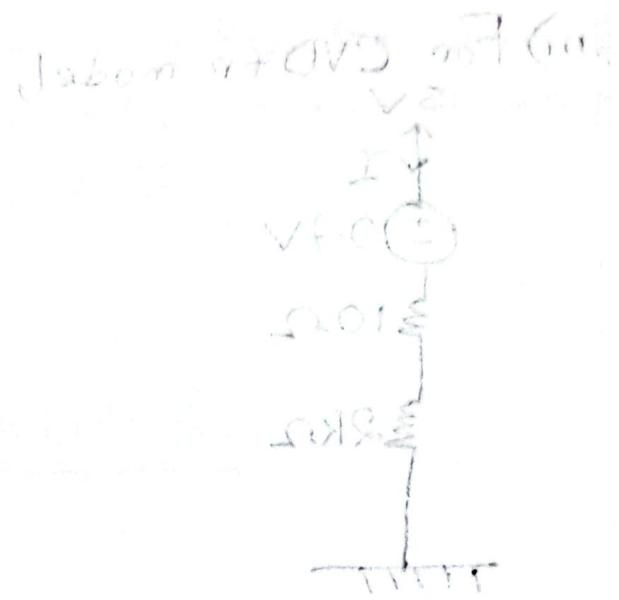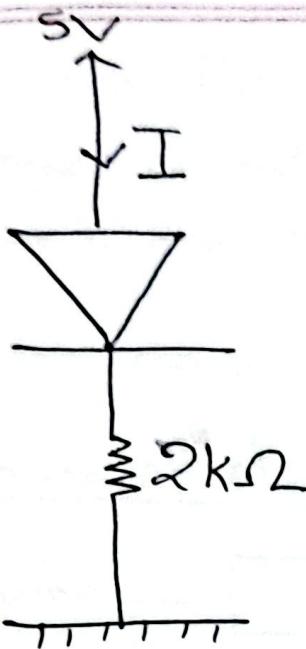

Find I,

$$\frac{V(0-0-0)}{2k\Omega} = I$$



i) For an ideal diode model

ii) For CVD model with $V_{D0} = 0.7V$

iii) For CVD+tr model with $V_{D0} = 0.7V$ and $r = 10\Omega$


iv) For ideal

$$V_D = 5 - 0$$

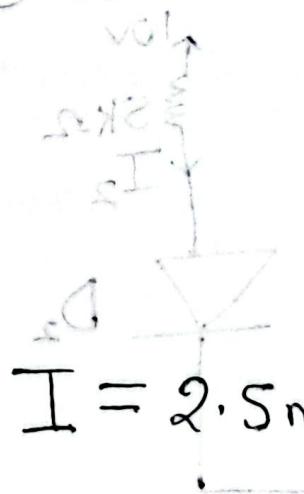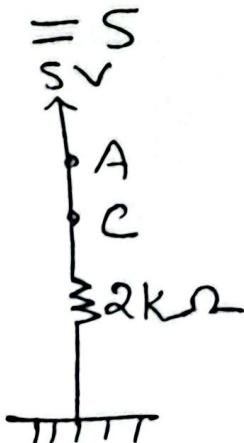

$$I = 2.5mA$$


ii) For CVD model

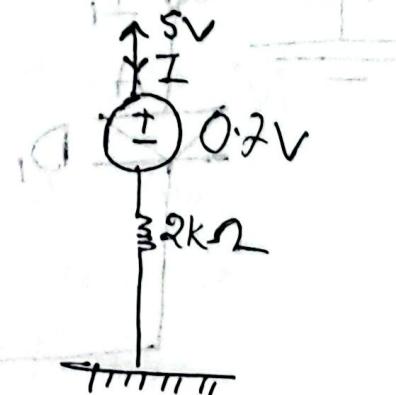

$$I = \frac{5 - 0.7}{2}$$

$$= 2.15mA$$

ii) For CVD+r model,

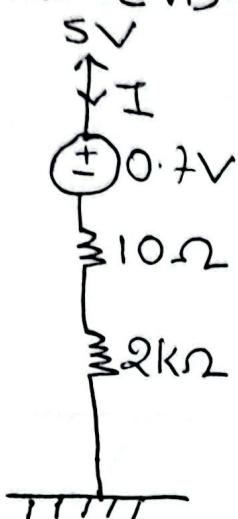



$$I = \frac{(5 - 0.7 - 0)V}{2100\Omega}$$

$$I = 5.37 \text{ mA}$$

$$I = 2.19 \text{ mA}$$

If r is not specified, then use CVD Model.

Q2)

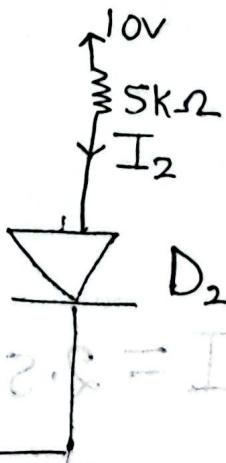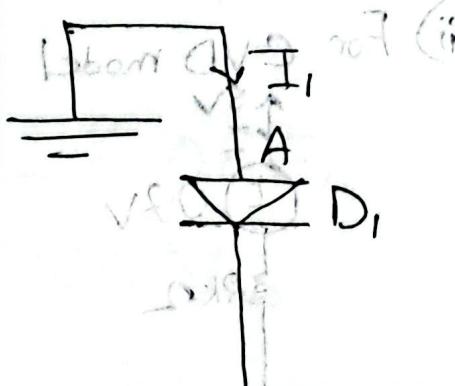


$$A_1 \cdot 2^{\frac{I}{I_0}} = I$$


$$\frac{10 - 2}{2} = 1$$

$$A_1 \cdot 2^{\frac{I}{I_0}} = -5$$

- For both D_1 and D_2 we don't know the value of voltage of cathode and due to this we cannot determine whether a diode is ~~on or~~ ON or OFF
- For this reason we will use,

Method of Assumed State (MAS)


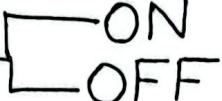
I) Assume 

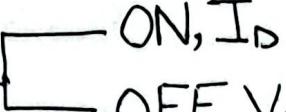II) Calculation 

III) Verify 

Assumption-1: Assume D_1 and D_2 are both open

Using CVD Model,

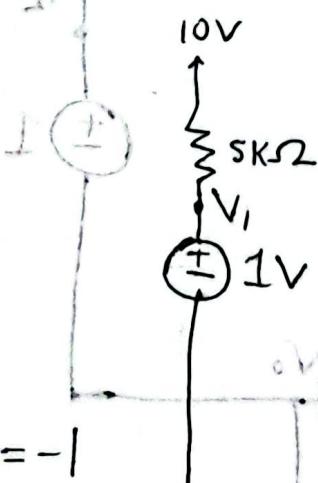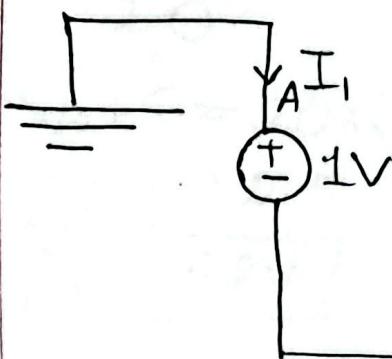

$$I = 0 - V_0$$

$$I = -V_0$$

$$V_0 = -1V$$

∴ For D_1

$$i_3 = -1 - (-1) \over 20$$

$$i_3 = 0.2mA$$

$$V_1 - (-1) = 1$$

$$V_1 + 1 = 1$$

$$V_1 = 0V$$

$$i_2 = \frac{10 - 0}{5} = 2 \text{ mA}$$

$$i_2 = 2 \text{ mA}$$

Applying KCL at V_o ,

$$i_1 + i_2 = i_3$$


$$i_1 + 2 = 0.2$$

$$i_1 = -1.8 \text{ mA}$$

Since $i_1 < 0$,

D_1 and D_2 both cannot be on,

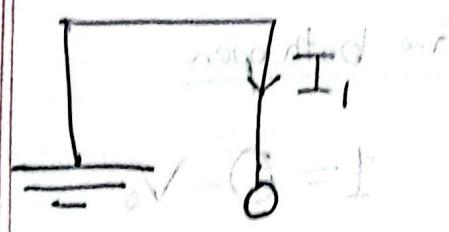Since $i_1 < 0$ we will assume that D_1 is off and D_2 is on



$$V_o = 1$$

$$$$

Since D_1 is off, $i_1 = 0$

$$I_1 = 0V$$

Applying KCL at V_o ,

$$i_1 + i_2 = i_3$$

$$0 + i_2 = i_3$$

$$\therefore i_2 = i_3$$

Apply KVL in the circuit,

$$10 - (-5) = 5i_2 + 1 + 20i_3$$

$$15 = 5i_2 + 1 + 20i_3$$

$$14 = 25i_2$$

$$i_2 = 0.56mA$$

$$i_3 = 0.56mA$$

$$\frac{V_o - (-5)}{20} = 0.56$$

$$V_o + 5 = 20 \times 0.56$$

$$V_o = 11.2 - 5$$

$$V_o = 6.2V$$

CSE-251

14/11/25

Lecture-8

No notes

$VO = I$

$\Delta \rightarrow \text{ISI} \text{ entry A}$

$\beta = \alpha + \beta$

CSE-251

lecture-9

16/11/25

$\beta = \alpha$

No notes

$\Delta \rightarrow \text{ISI} \text{ entry A}$

$\Delta \rightarrow \text{ISI} \rightarrow 162 + 1 + 82 = (2-) - 01$

$\Delta \rightarrow \text{ISI} \rightarrow 162 + 1 + 82 = 21$

$\beta = \beta$

$\Delta \rightarrow \text{ISI} - 1$

$\Delta \rightarrow \text{ISI} - 1$

$\Delta \rightarrow \frac{(2-) - \Delta}{01}$

$\Delta \rightarrow 0 \times 02 = 2 + \Delta$

$2 - 3 \Delta = \Delta$

$\Delta = 0$