

Question 1

Set-01: (a) [1.5 marks]

Why can we use MOSFETs as switches? Explain briefly with necessary graphs.


Set-02: (a) [1.5 marks]

Why can we use BJTs as switches? Explain briefly with necessary graphs.

Answer

Set-01: Cutoff & Triode Mode in MOSFET's I-V graph resembles the OFF & ON state of a Switch's I-V graph. That's why we use MOSFETs as switches.

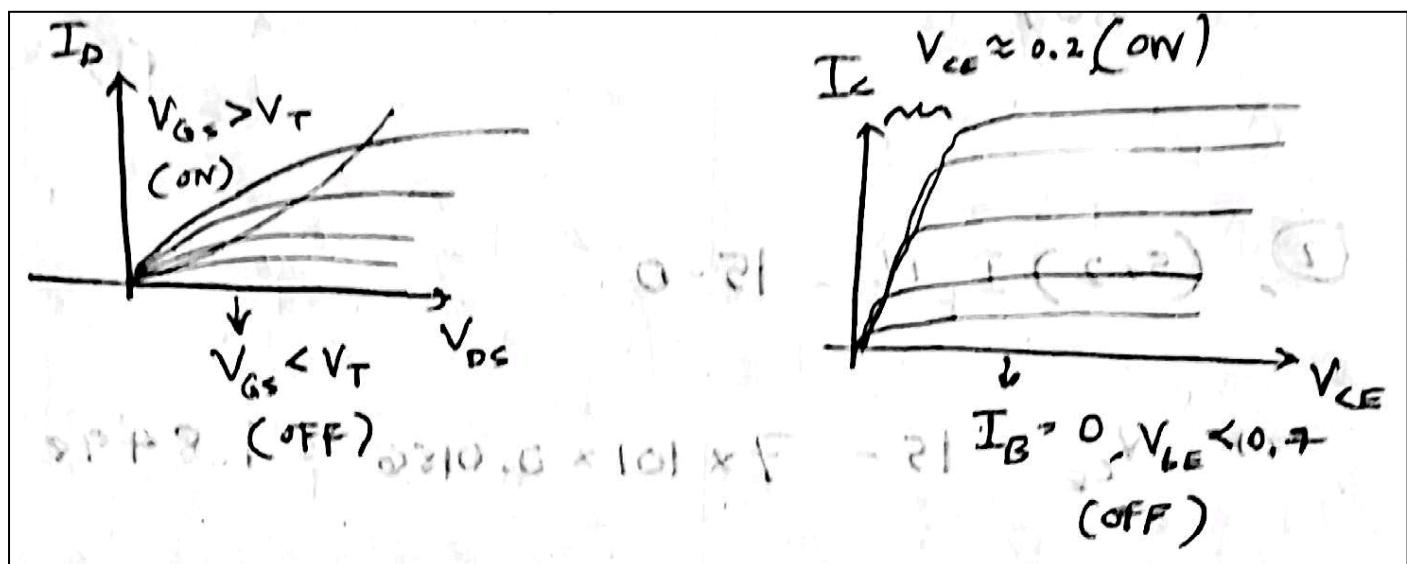Set-02: Cutoff & Saturation Mode in BJT's I-V graph resembles the OFF & ON state of a Switch's I-V graph. That's why we use MOSFETs as switches.




Set-01: (b) [2 marks]

Draw the input and output voltage waveforms of a full-wave rectifier with CVD model when a sinusoidal voltage is applied as input. Label the graph properly. Indicate the states of the diodes during the positive and negative half cycles of the input voltage.

Set-02: (b) [2 marks]

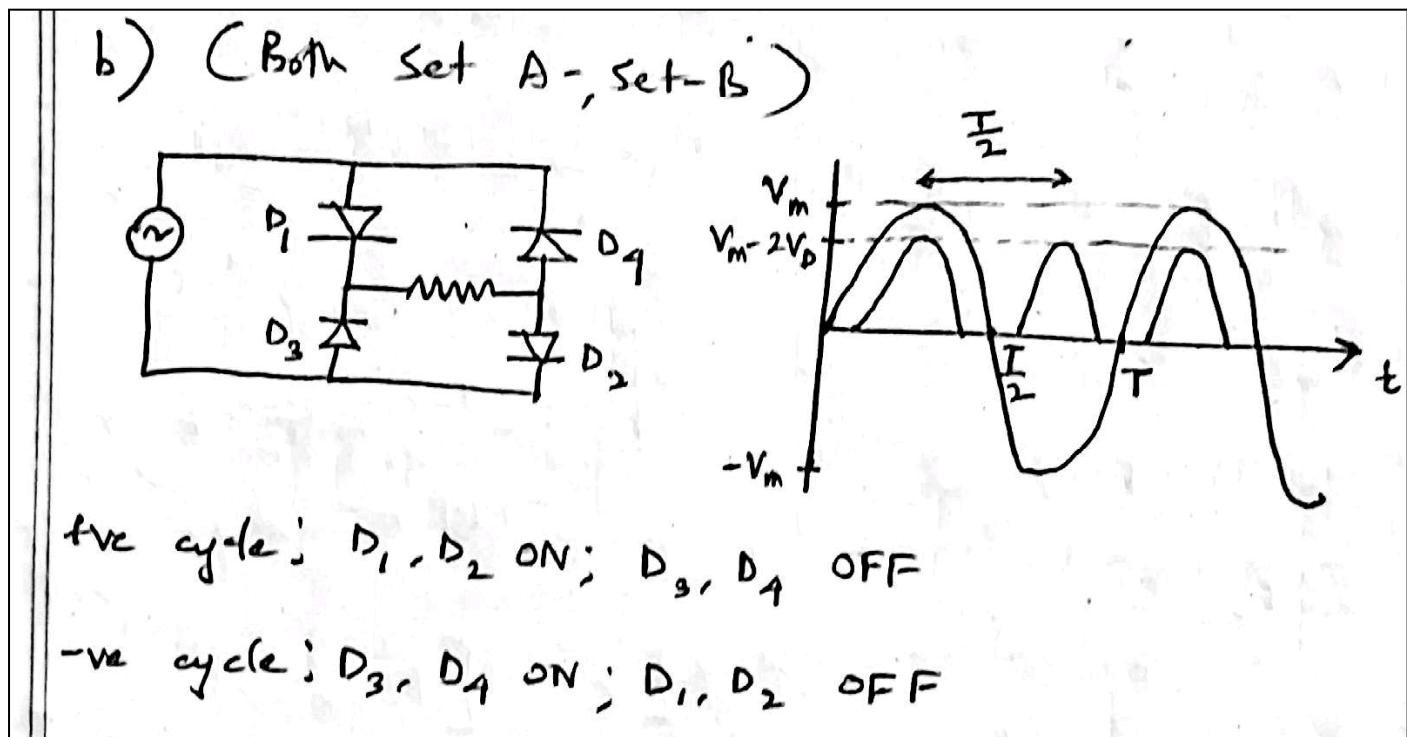Draw the input and output voltage waveforms of a full-wave rectifier with CVD model when a sinusoidal voltage is applied as input. Label the graph properly. Indicate the states of the diodes during the positive and negative half cycles of the input voltage.



Set-01: (c) [1 mark]

"A resistor is connected to the base of a BJT to build logic gates." - Explain the reason briefly.

Set-01: (c) [1 mark]

"A resistor is connected to the base of a BJT to build logic gates." - Explain the reason briefly.

- c) To convert voltage to current, ~~for~~ for cascading of gates.
To limit current of base.
To allow control of base current via R_B

Set-01: (d) [1.5 marks]

Will the output waveform change if you increase the value of the load resistance of a full-wave rectifier with a capacitor? Explain briefly.

Set - A : $R_L \uparrow \Rightarrow V_{\text{ripple}} \downarrow \Rightarrow V_{DC} \uparrow$ [Waveform less ripple]

Set-02: (d) [1.5 marks]

Will the output waveform change if you decrease the value of the load resistance of a full-wave rectifier with a capacitor? Explain briefly.

Set - B : $R_L \downarrow \Rightarrow V_{\text{ripple}} = \frac{V_p}{f R_L C} \uparrow \Rightarrow V_{DC} = (V_p - V_{\text{ripple}}) \downarrow$ Waveform has more ripple

Question 2

(a) [6 marks]

Q2 : Set - A

Assume active :

KVL ①,

$$7I_E - 1 + 50I_B = 15 - 1V$$

$$+ 0.7 + 3I_E$$

$$\Rightarrow 7 \times 101 \times I_B + 50I_B = 14.3$$

$$\Rightarrow I_B = \frac{14.3}{757} = 0.0189 \text{ mA}$$

$$I_C = 1.89 \text{ mA}, I_E = 1.908 \text{ mA}$$

KVL ②, (1+3)I_E + V_{CE} = 15 - 1V

$$\Rightarrow V_{CE} = 14 - 7 \times 1.908 = 0.649 > 0.2$$

\therefore In active mode

Set - B

Assume active :

KVL ①,

$$7 \times 101 \times I_B + 100I_B + 0.7 + 1 = 15 - (-1)$$

$$\Rightarrow I_B = \frac{14.3}{807} = 0.0177 \text{ mA}$$

$$I_C = 1.77 \text{ mA}, I_E = 1.789 \text{ mA}$$

KVL ②, $-V_{CE} = 15 - (-1) - 7I_E$

$$= 3.977 > 0.2$$

\therefore In active mode

(b) [6 marks]


i) M2 : $V_{G1} = V_D \Rightarrow V_{G1} - V_S = V_D - V_S$

$V_{G1} - V_S = V_D - V_S \Rightarrow V_{GS} = V_{DS}$

$V_{GS} = V_{DS} \Rightarrow V_{GS} - V_T < V_{DS}$

\therefore Must be in Saturation!

ii) Set A

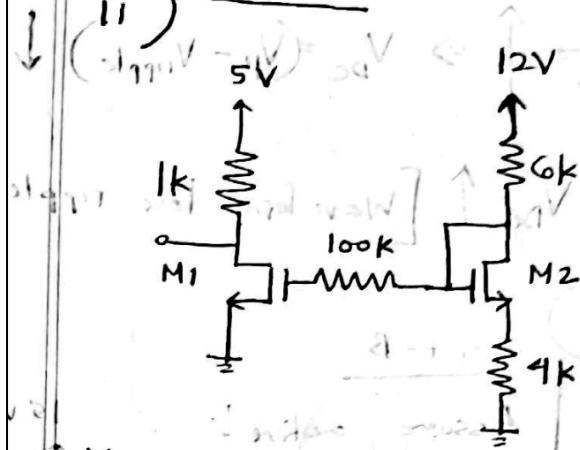

M2 sat:

$$V_G = x, V_D = x, V_S = y$$

$$V_{ov} = x - y - 1, V_{ds} = x - y$$

$$\frac{12 - x}{8k_3} = \frac{y - 0}{1k_2} = I_D$$

$$y = 12 - \frac{2}{3}x \Rightarrow x = 12 - \frac{3}{2}y$$

$$I_D = \frac{k}{2} V_{ov}^2 = (x - y - 1)^2$$

$$\Rightarrow \frac{y}{4} = (12 - \frac{3}{2}y - y - 1)^2$$

$$\Rightarrow \frac{y}{4} = \left[11 - \frac{5y}{2} \right]^2$$

$$\Rightarrow \frac{y}{4} = \frac{1}{16} \left[22 - 5y \right]^2$$

$$\Rightarrow y = 189 - 220y + 25y^2$$

$$\Rightarrow 25y^2 - 221y + 189 = 0$$


$$y = 4.81, 9 \Rightarrow V_G = V_D = 6$$

$$V_G = V_D = 4.71$$

$$V_{GS} = 2 > V_T$$

$$V_{GS} < V_T$$

Set B

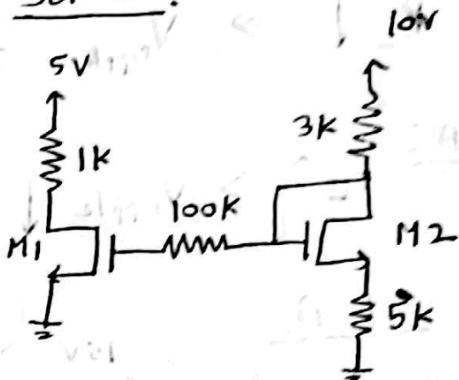

M2 sat:

$$V_G = x, V_D = x, V_S = y$$

$$V_{ov} = x - y - 1, V_{ds} = x - y$$

$$\frac{10 - x}{3k_3} = \frac{y - 0}{1k_2} = I_D$$

$$I_D = \frac{k}{2} V_{ov}^2 = (x - y - 1)^2$$

$$\Rightarrow \frac{y}{5} = (10 - \frac{3}{5}y - y - 1)^2$$

$$\Rightarrow \frac{y}{5} = (9 - \frac{8y}{5})^2$$

$$\Rightarrow \frac{y}{5} = \frac{1}{25} (45 - 16y)^2$$

$$\Rightarrow 5y = 2025 - 720y + 64y^2$$

$$\Rightarrow 64y^2 - 725y + 2025 = 0$$


$$\Rightarrow y = 6.328, 5$$

$$V_G = V_D = 6.203$$

$$V_G = V_D = 7$$

$$V_{GS} < V_T \quad V_{GS} = 2 > V_T$$

✓

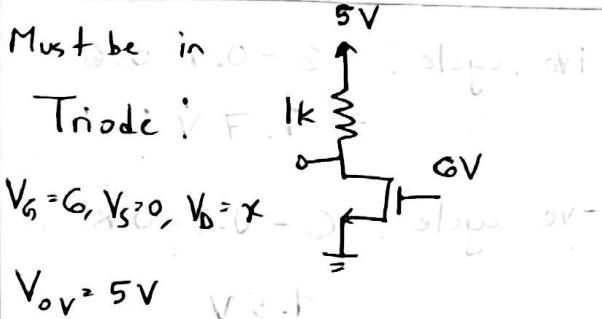

$$I_D = k \left[V_{DS} V_{OV} - \frac{1}{2} V_{DS}^2 \right]$$

~~$\Rightarrow \frac{5-x}{1} = \frac{1}{2} \left[5x - \frac{x^2}{2} \right]$~~

$\Rightarrow 5-x = \frac{1}{2} \left[10x - x^2 \right]$


$\Rightarrow 20 - 10x = 10x - x^2$

$\Rightarrow x^2 - 19x + 20 = 0$

$\Rightarrow x = 12.385V, 1.615V$

~~$V_{DS} > V_{OV}$~~

~~$V_{DS} < V_{OV}$~~

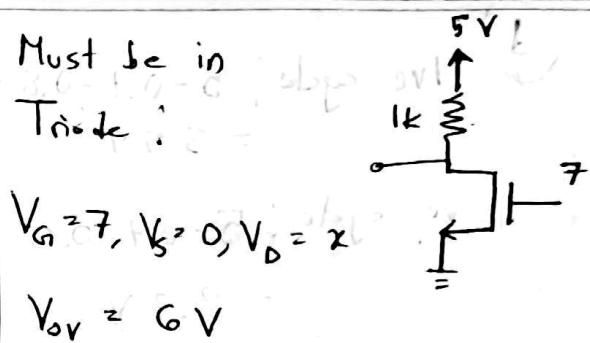

$$I_D = 5-x = \frac{1}{2} \left[6x - \frac{1}{2}x^2 \right]$$

$\Rightarrow 20 - 10x = 12x - x^2$

$\Rightarrow x^2 - 16x + 20 = 0$

$\Rightarrow x = 14.633, 1.366$

$V_{DS} < V_{OV} \checkmark$

(c) [2 marks]

Set - A

Q (C) $R = 5k$, $f = 1kHz$, $V_{D_0} = 0.5V$

$$f_{out} = \frac{1}{1 \times 10^{-3}} = 1kHz \rightarrow HW$$

(half wave)

$$V_{max} = 5V, V_{avg} = 2.5V$$

$$V_{ripple} = 2.5V, C = \frac{V_p}{f_{out} R} V_{ripple}$$

$$V_p = 5 - 0.5 = 4.5V$$

$$3.6 \times 10^{-9} F$$

Set - B

$R = 5k$, $f = 0.5kHz$, $V_{D_0} = 0.55V$

$$f_{out} = \frac{1}{1 \times 10^{-3}} = 1kHz \Rightarrow 2f \rightarrow FW$$


(full wave)

(d) [2 marks]

d


$$+ve \text{ cycle: } 5 - 0.7 - 0.8 \\ = 3.5 \text{ V}$$
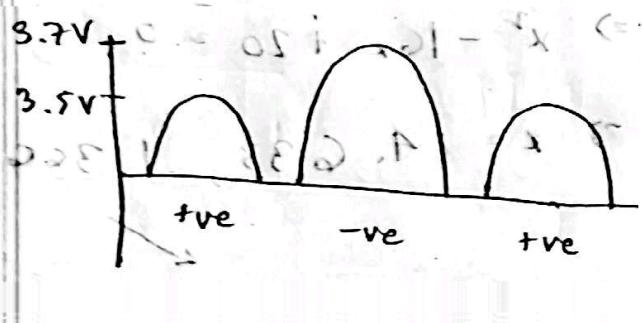
$$-ve \text{ cycle: } 5 - 0.7 - 0.6 \\ = 3.7 \text{ V}$$







$$+ve \text{ cycle: } 16 - 0.7 - 0.6 \\ = 1.7 \text{ V}$$

$$-ve \text{ cycle: } 16 - 0.7 - 0.8 \\ = 1.5 \text{ V}$$

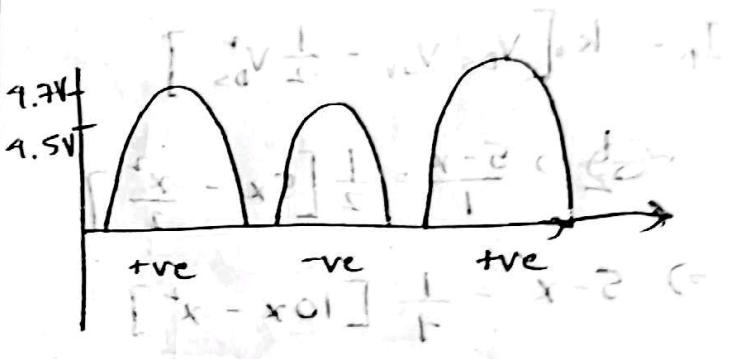

Question 3

(a) [3 marks]

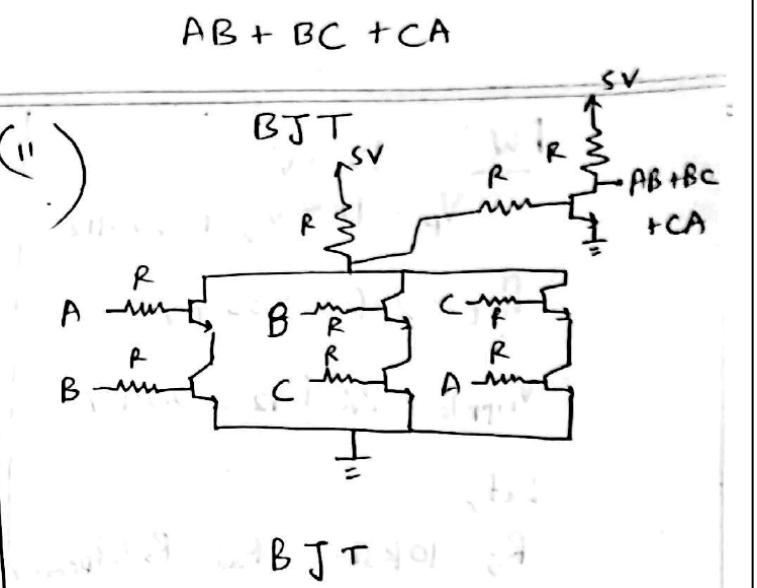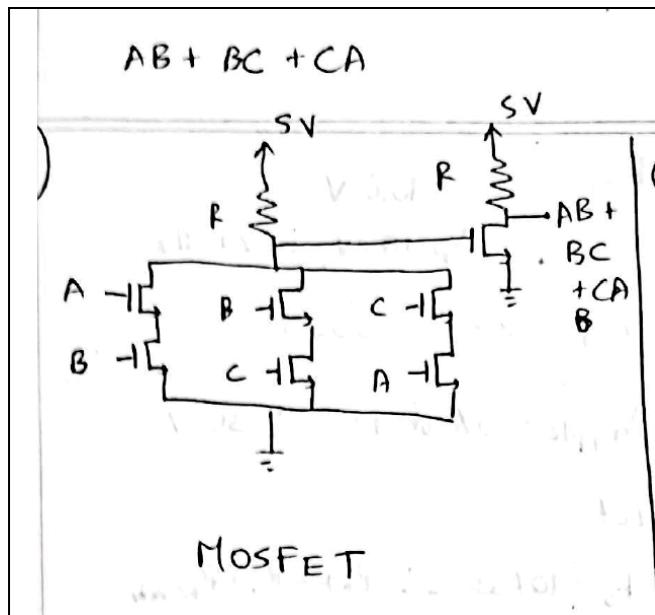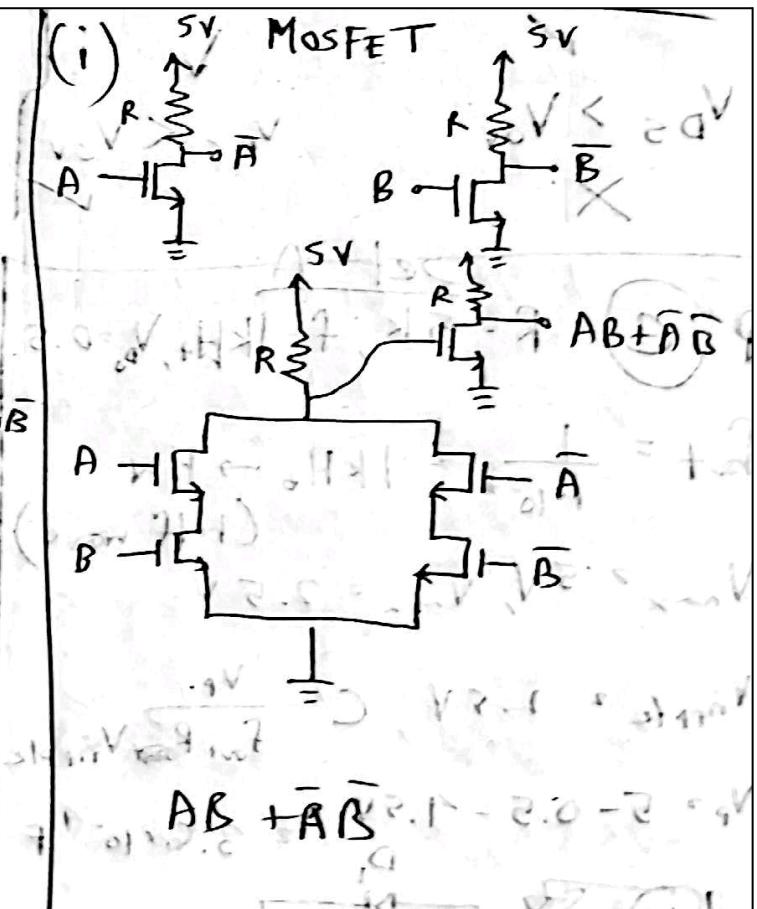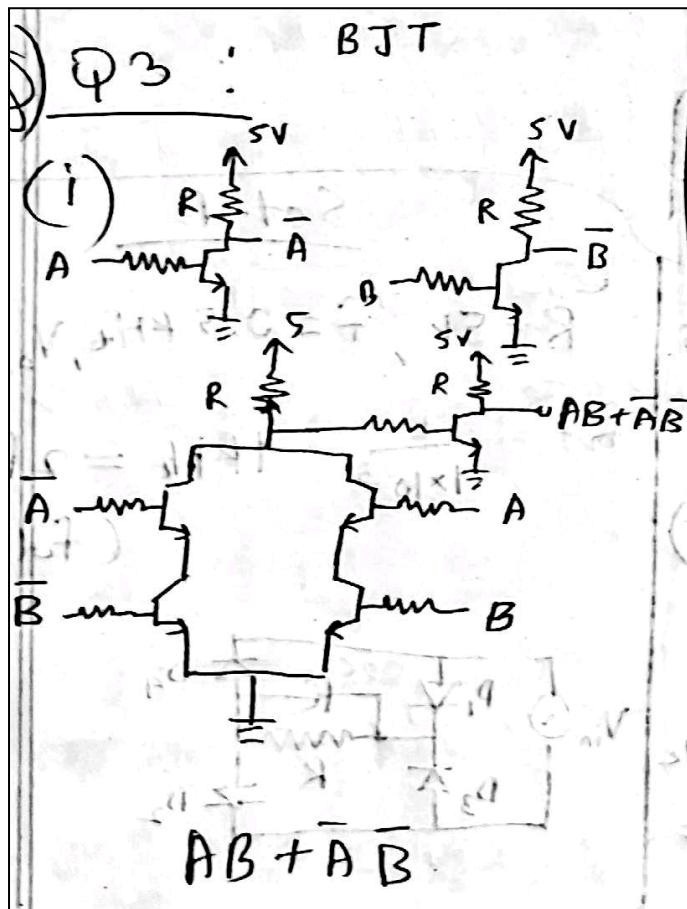

(b) [5 marks]

b) $V_{in} = 12 \sin(500\pi t)$

$V_m = 12, f = 250 \text{ Hz}$


HW: $V_p = 11.3 \text{ V}, f_{out} = 250 \text{ Hz}$

$V_{ripple} = 2\% \text{ of } 12 = 0.24 \text{ V}$

Let, $R_s = 10 \text{ k}\Omega = 10,000 \Omega, R_{motor} = 10 + 0.05 = 10,050 \Omega$

$$C = \frac{V_p}{V_{ripple} f (R_s + R_{motor})} = \frac{1.879 \times 10^{-5}}{18.79 \mu\text{F}} = 1.879 \times 10^{-5} \text{ F}$$

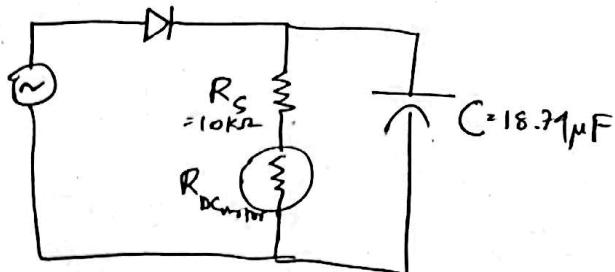$\therefore R_s = 10 \text{ k}\Omega, C = 18.79 \mu\text{F}$



$V_{in} = 12 \sin(500\pi t)$

$V_m = 12, f = 250 \text{ Hz}$


HW: $V_p = 11.3 \text{ V}, f_{out} = 250 \text{ Hz}$

$V_{ripple} = 3\% \text{ of } 12 = 0.36 \text{ V}$

Let, $R_s = 10 \text{ k}\Omega = 10,000 \Omega, R_{motor} = R_s + R_{motor} = 10,050 \Omega = 10,050 \Omega$

$$C = \frac{V_p}{V_{ripple} f_{out} (R_s + R_{motor})} = \frac{1.25 \times 10^{-5}}{12.5 \mu\text{F}} = 12.5 \mu\text{F}$$

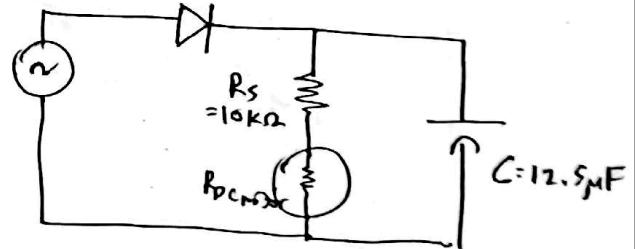$\therefore R_s = 10 \text{ k}\Omega, C = 12.5 \mu\text{F}$



FW: 10.6 V

$$V_p = 14.8 V, f = 250 \text{ Hz}$$

$$f_{\text{out}} = 2 \times f = 500 \text{ Hz}$$


$$V_{\text{ripple}} = 2\% \text{ of } 12 = 0.24 \text{ V}$$

Let,

$$R_s = 10 \text{ k}\Omega \quad \therefore R_{\text{out}} = R_s + R_{\text{Crotor}} \\ = 10,000 \Omega \quad = 10,050 \Omega$$

$$C = \frac{V_p}{V_{\text{ripple}} f_{\text{out}} (R_{\text{out}})} = 8.79 \mu\text{F}$$
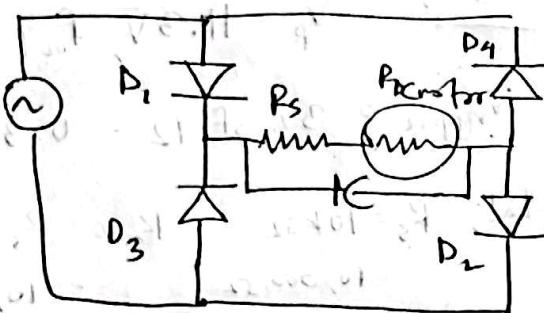
$$R_s = 10 \text{ k}\Omega, C = 8.79 \mu\text{F}$$



FW: 10.6 V

$$V_p = 14.8 V, f = 250 \text{ Hz}$$

$$f_{\text{out}} = 2 \times f = 500 \text{ Hz}$$

$$V_{\text{ripple}} = 3\% \text{ of } 12 = 0.36 \text{ V}$$

Let,

$$R_s = 10 \text{ k}\Omega \quad \therefore R_{\text{out}} = R_s + R_{\text{Crotor}} \\ = 10,050 \Omega$$

$$C = \frac{V_p}{V_{\text{ripple}} f_{\text{out}} R_{\text{out}}} = 5.86 \mu\text{F}$$

$$R_s = 10 \text{ k}\Omega, C = 5.86 \mu\text{F}$$

