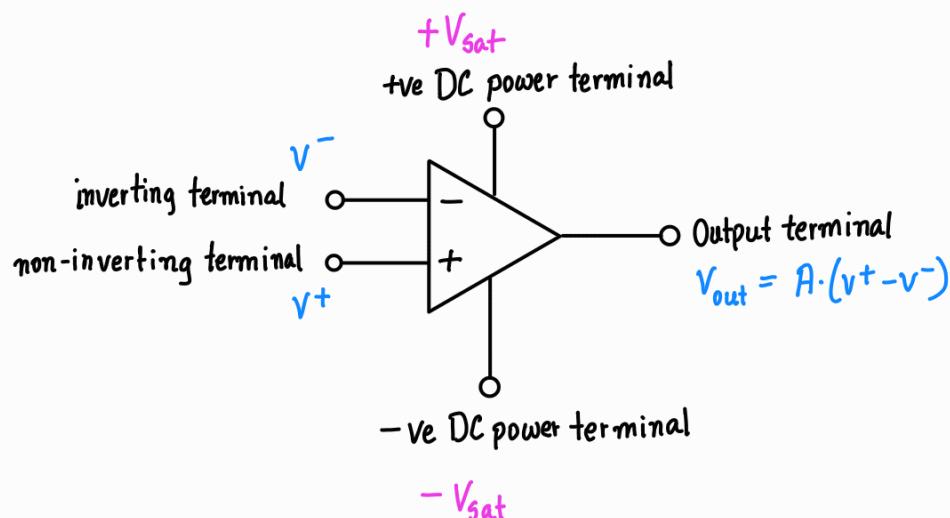


Op-amp (Operational amplifier) is a differential (refers to voltage difference) amplifier. It has 5 terminals —



The A in $v_{out} = A(v^+ - v^-)$ stands for gain. The difference, $v^+ - v^-$ is why op-amp is called a differential amplifier.

The inverting and non-inverting terminals are used as inputs and the output terminal provides the amplified output.

So what do the other 2 terminals do?


What you have to realize is that amplification needs energy beyond the input values as you cannot magically increase the energy of a signal. For op-amps we supply this extra energy through two DC voltage sources — one connected as $+V_{sat}$ (@ +ve DC power terminal) and other connected as $-V_{sat}$ (@ -ve DC power terminal). This DC power allows amplification of the input signal.

Question — If amplification is dependent on $+V_{sat}$ & $-V_{sat}$, can you ever amplify an input voltage signal beyond the range $[-V_{sat}, +V_{sat}]$?

NO! Remember that you cannot create energy beyond what you supply.

So, for an op-amp, $v_{out} = \begin{cases} A(v^+ - v^-) & \text{if } -V_{sat} \leq A(v^+ - v^-) \leq +V_{sat} \\ -V_{sat} & \text{if } A(v^+ - v^-) < -V_{sat} \\ +V_{sat} & \text{if } A(v^+ - v^-) > +V_{sat} \end{cases}$

Lets take a small example —

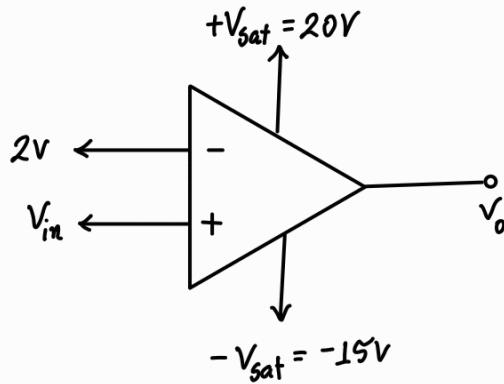


Lets consider $A=5$

Now lets see how V_o changes with change in V_{in}


V_{in}	$V_d = V^+ - V^-$	$A V_d$	V_o	Remarks
-3V	-5V	-25V	-15V	$A V_d < -V_{sat}$, so $V_o = -V_{sat}$
-2V	-4V	-20V	-15V	"
-1V	-3V	-15V	-15V	$-V_{sat} \leq A V_d \leq +V_{sat}$, so $V_o = A V_d$
0V	-2V	-10V	-10V	"
1V	-1V	-5V	-5V	"
2V	0V	0V	0V	"
3V	1V	5V	5V	"
4V	2V	10V	10V	"
5V	3V	15V	15V	"
6V	4V	20V	20V	"
7V	5V	25V	20V	$A V_d > +V_{sat}$, so $V_o = +V_{sat}$
8V	6V	30V	20V	"

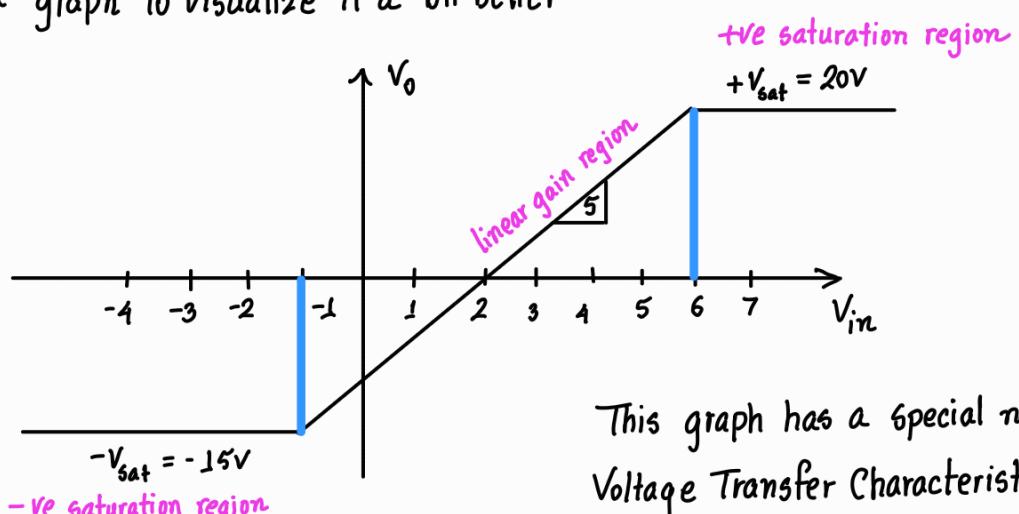Now understanding the relation from the table maybe a bit hard. Lets try plotting V_o vs V_{in} on a graph to visualize it a bit better —



This graph has a special name —
Voltage Transfer Characteristics (VTC) graph

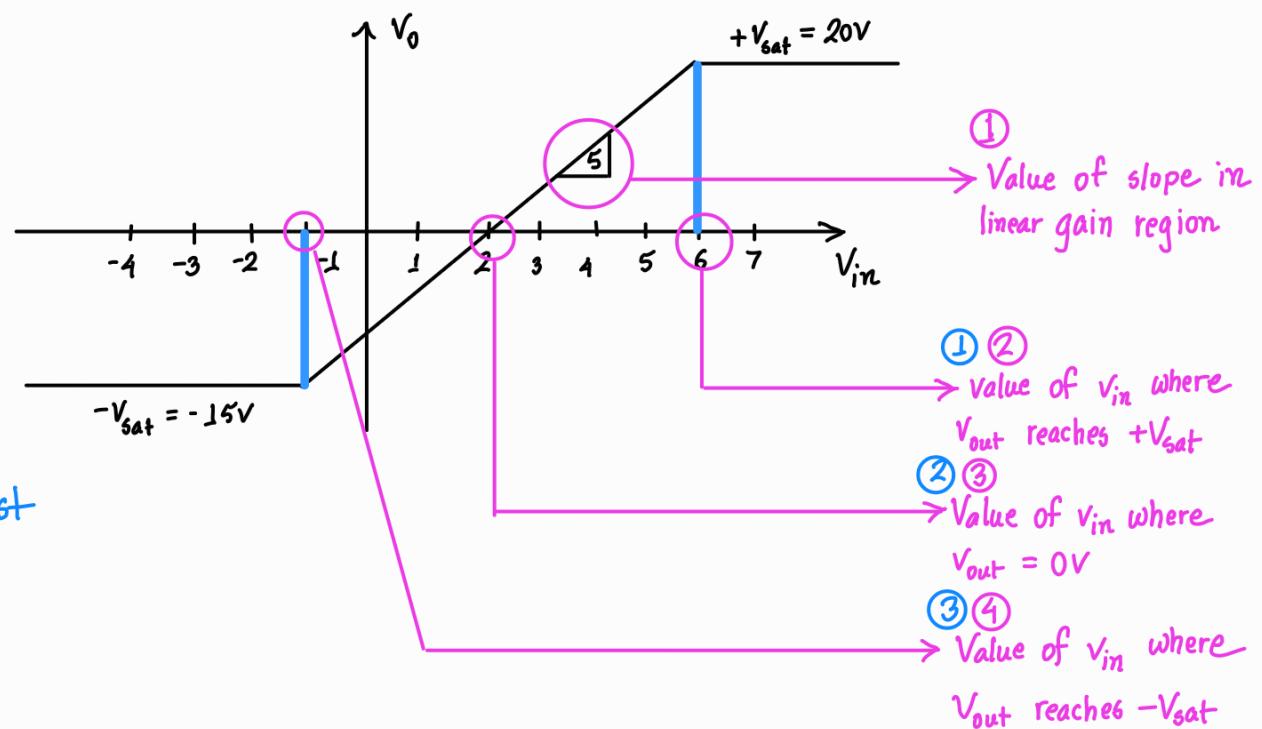The VTCs of an op-amp will always be similar to this graph. To fully define an op-amp VTC, you need to mark 4 things (slope + 3 points of interest). Let's see them in the plotted VTC graph —




Now you will be asked to draw the VTCs to show relationships between V_{in} & V_{out} .

But it is clearly not feasible to draw the table every time. So can we draw the VTC without constructing the table?

Yes, just use the 3 points of interests.

Let me show you an example —

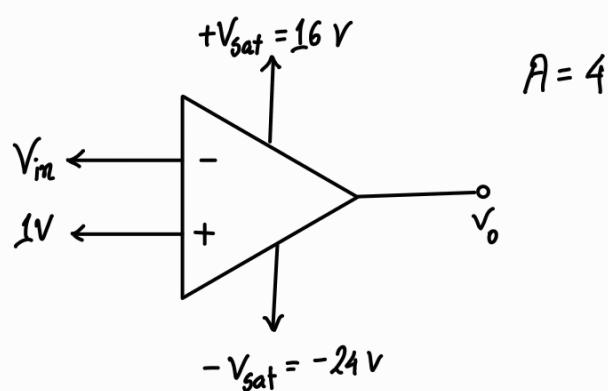

first find V_o in terms of V_{in} for the linear gain region —

$$\text{here, } V_o = A(V^+ - V^-) = 4(1 - V_{in})$$

$$\therefore V_o = 4(1 - V_{in}) \quad \text{--- (1)}$$

then we use this equation to find the V_{in} value for the 3 points of interest —

① Value of V_{in} when V_o reaches $+V_{sat}$

substitute $V_o = +V_{sat} = 16V$ in equation ① —

$$16 = 4(1 - V_{in}) \Rightarrow V_{in} = -3V$$

② Value of V_{in} when $V_o = 0$

substitute $V_o = 0$ in equation ① —

$$0 = 4(1 - V_{in}) \Rightarrow V_{in} = 1V$$


③ Value of V_{in} when V_o reaches $-V_{sat}$

substitute $V_o = -V_{sat} = -24V$ in equation ① —


$$-24 = 4(1 - V_{in}) \Rightarrow V_{in} = 7V$$

$+V_{sat}$ point $-V_{sat}$ point
0 point

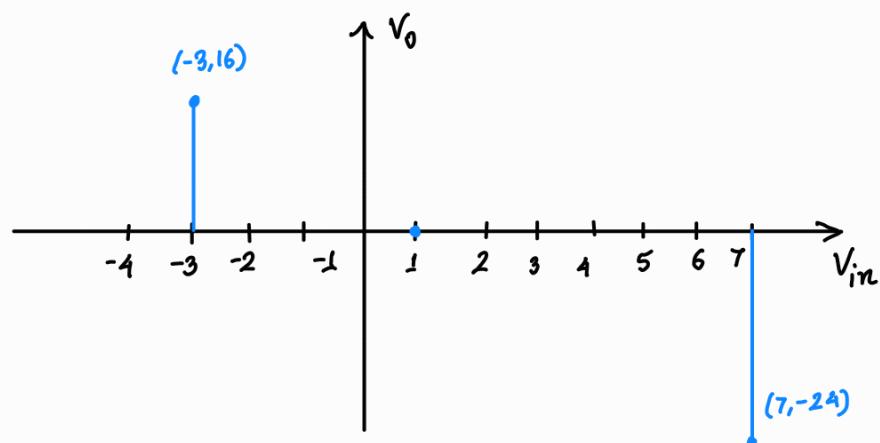
Now plot these points in the graph — $(V_{in}, V_o) \leftrightarrow (-3, 16), (1, 0), (7, -24)$



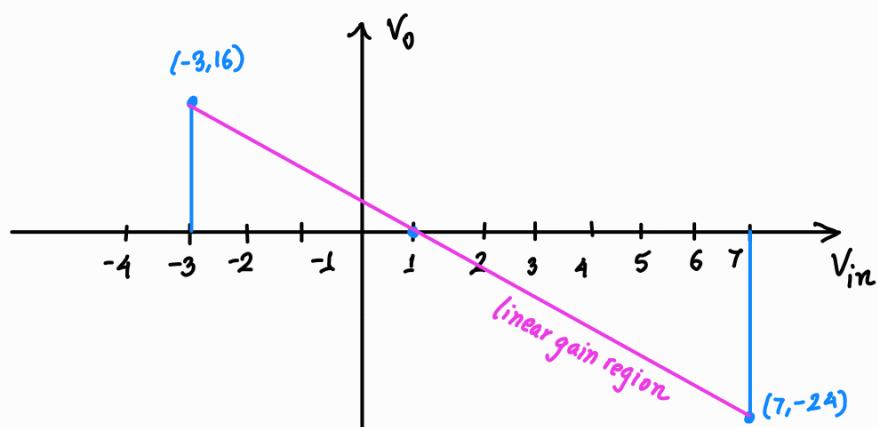
Now join these points to form the linear gain region —



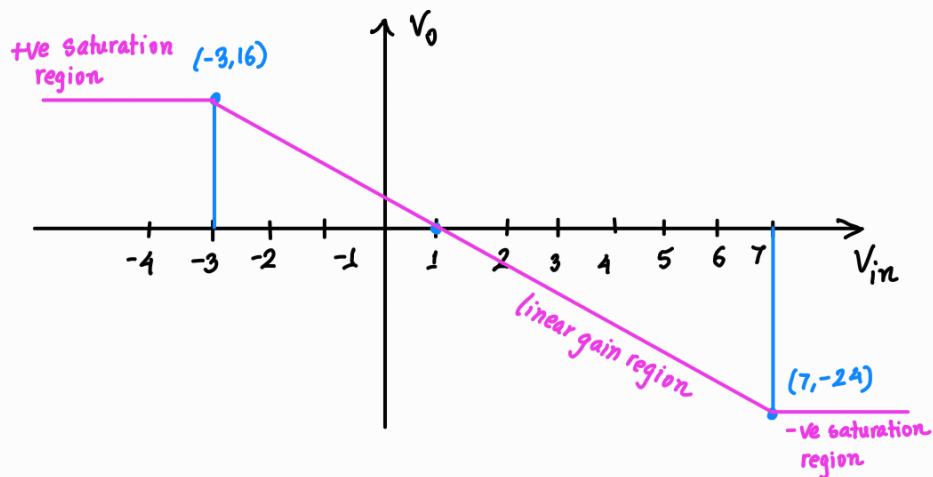Then complete the +ve & -ve saturation regions —




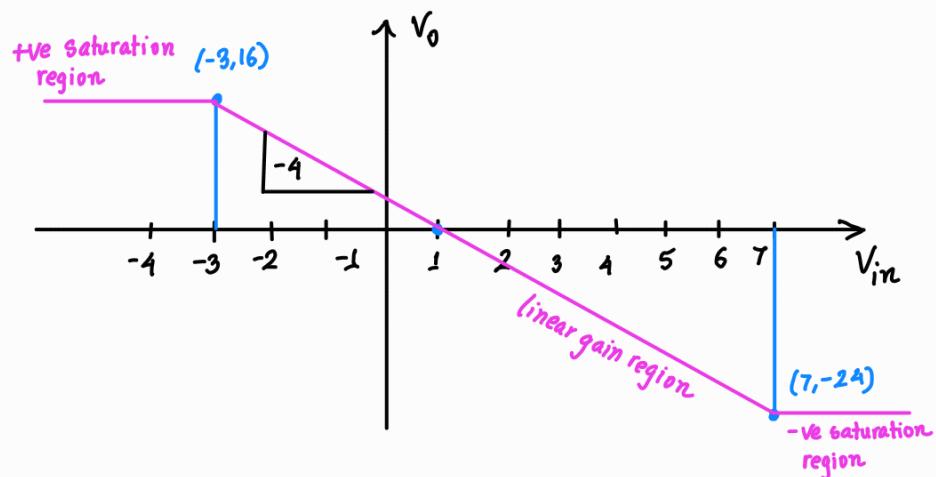Finally place the value of the slope and you are done with the VTC —



NOTE — This method drawing the VTC and the graph itself is applicable only for finite gain. For infinite gain (as you will soon see) the VTC is a bit different in the linear gain region. We will come back to this method when we study closed loop op-amp configs. For now we will talk about open-loop config and comparators after discussing about ideal op-amps.

Op-amp internal ckt simplified —

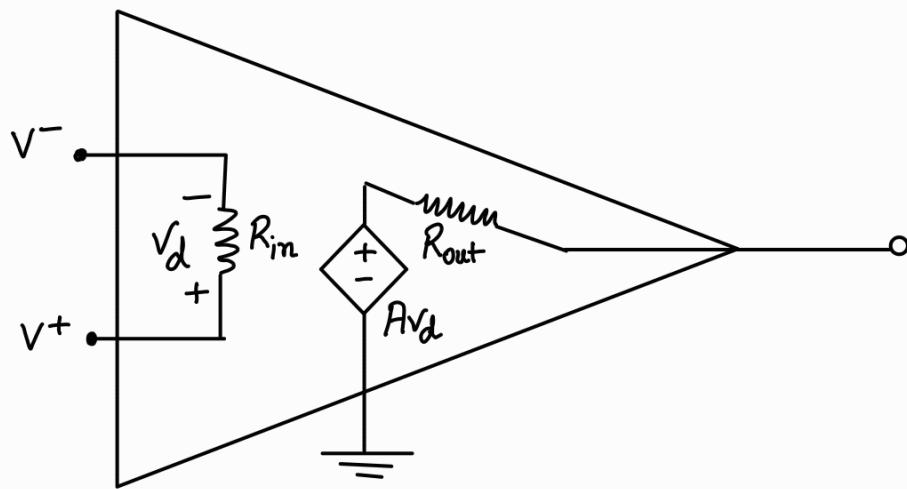

for an ideal op-amp —




- ① $R_{in} = \infty \Omega$
 - ② $A = \infty$
 - ③ $R_{out} = 0 \Omega$
- May be asked in the exam*

From now on we will only work with ideal op-amps. But in doing so, we get a gain of ∞ .

As such if $v^+ - v^- = \Delta v$ such that $\Delta v \rightarrow 0^+$, V_{out} becomes saturated @ $+V_{sat}$.




and if $v^+ - v^- = \Delta v$ such that $\Delta v \rightarrow 0^-$, V_{out} becomes saturated @ $-V_{sat}$.

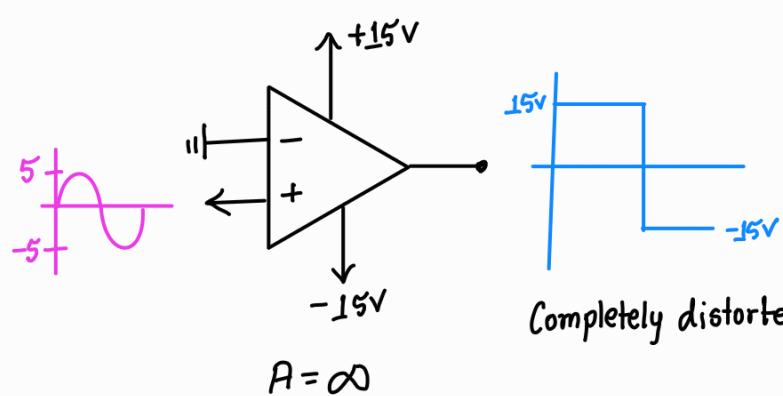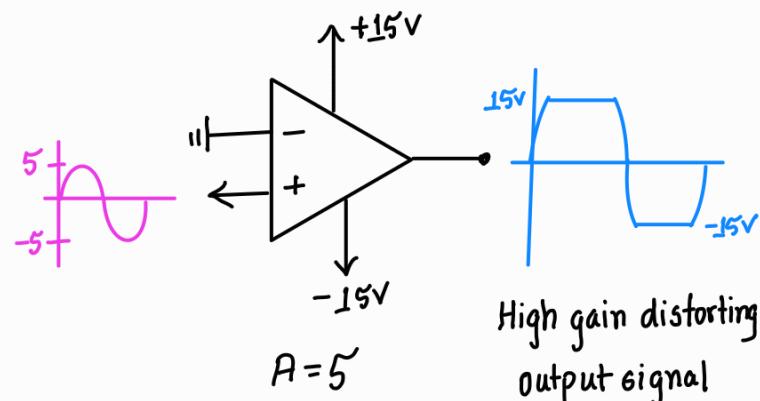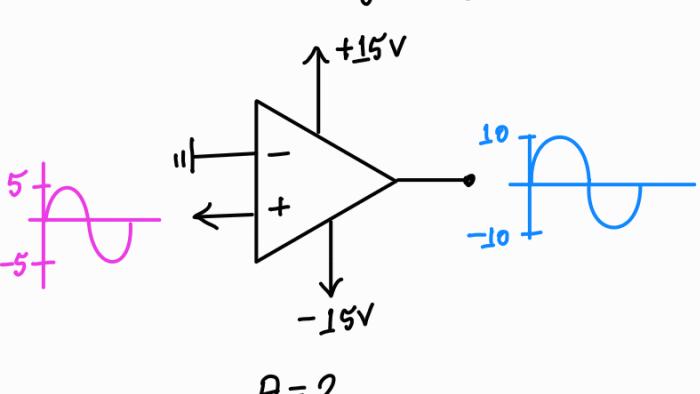As such we do not get any linear gain region, resulting in no proper amplification. For example —




So if we cannot amplify our signal with an ideal op-amp (at least in this configuration), is there even any purpose for this configuration?

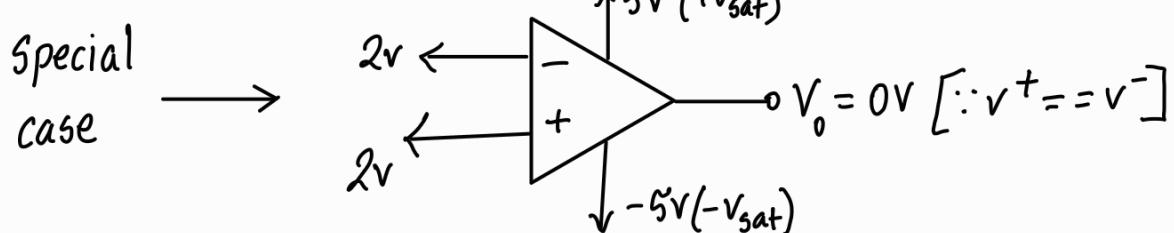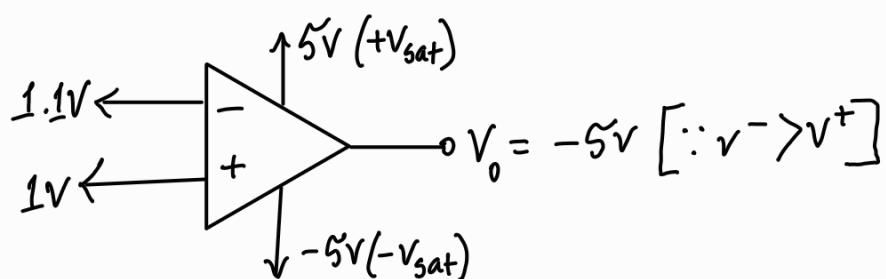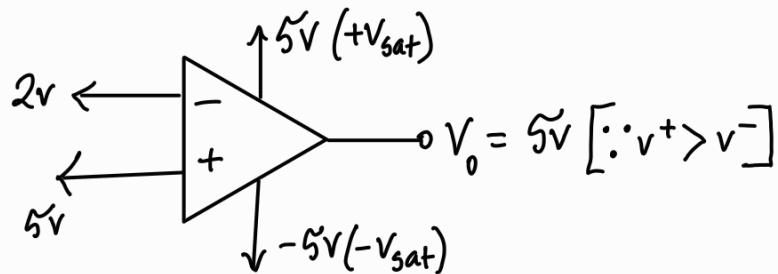
Yes, we use this configuration (open loop configuration) as comparator to check which one of v^+ & v^- is larger.



NB — for reference —

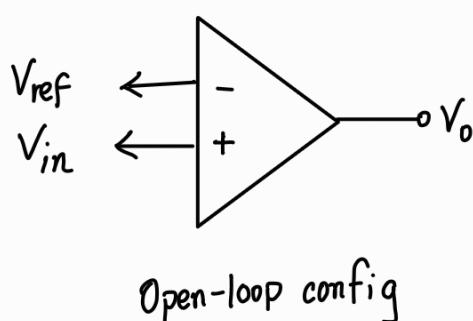


Open-loop config

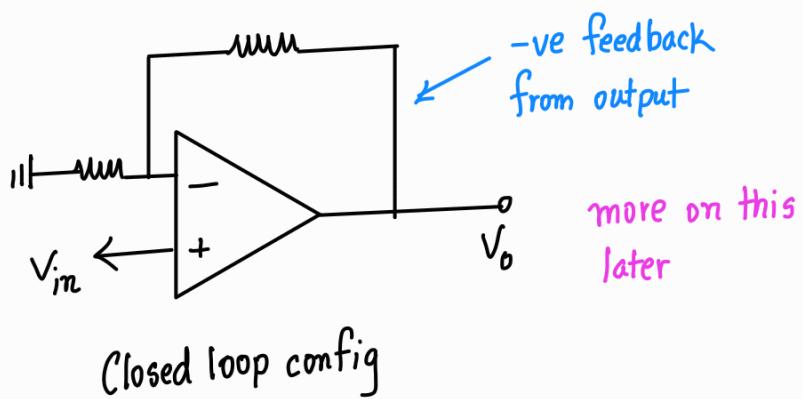


Closed loop config

NB — for an example of comparator ckt in practical sector, go through the smoke detector example in the slides.

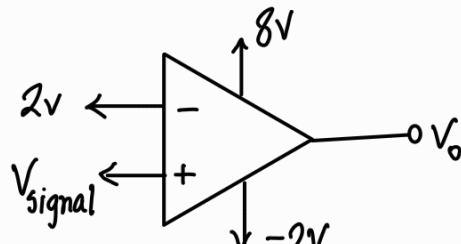
for this note let us look at some examples of comparators —



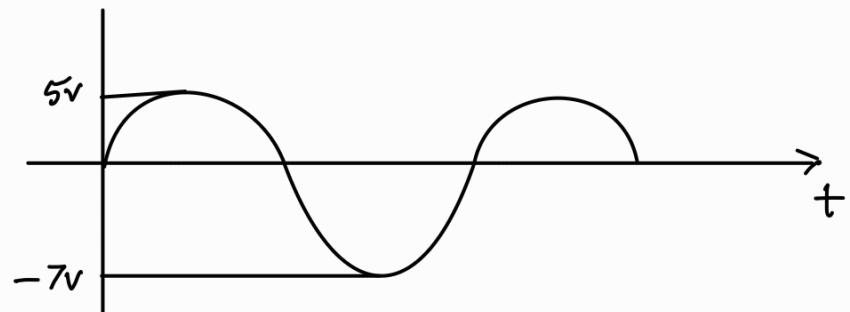
for V_{signal} graph given below, draw the V_0 graph —



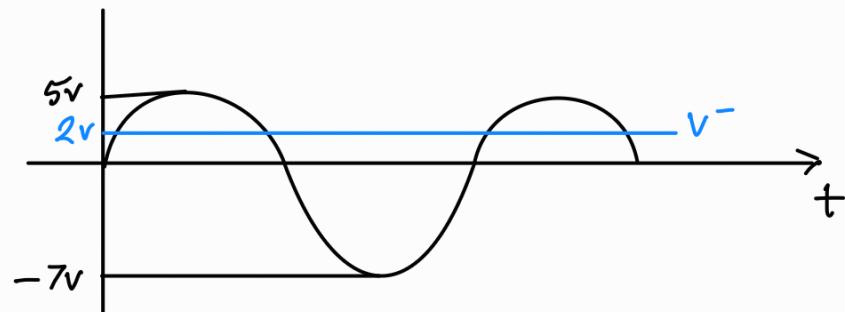
The V_{signal} is basically the v^+ . On the same graph plot v^- —



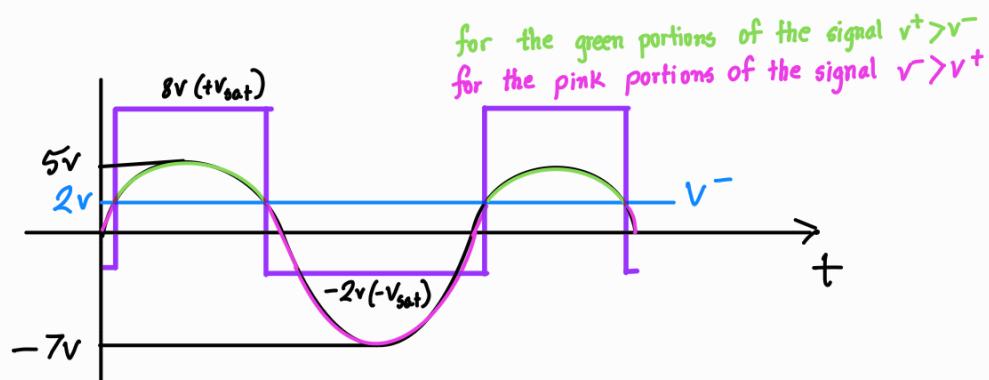
Now for each time point compare v^+ & v^- and draw the output (V_0) on the same graph



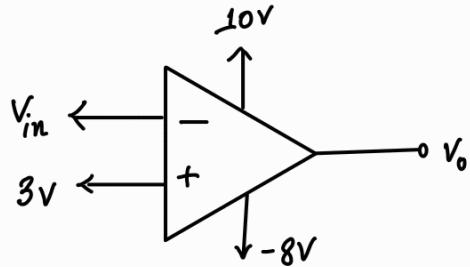
Lets do an example with a more complicated waveshape —



The V_{in} signal —


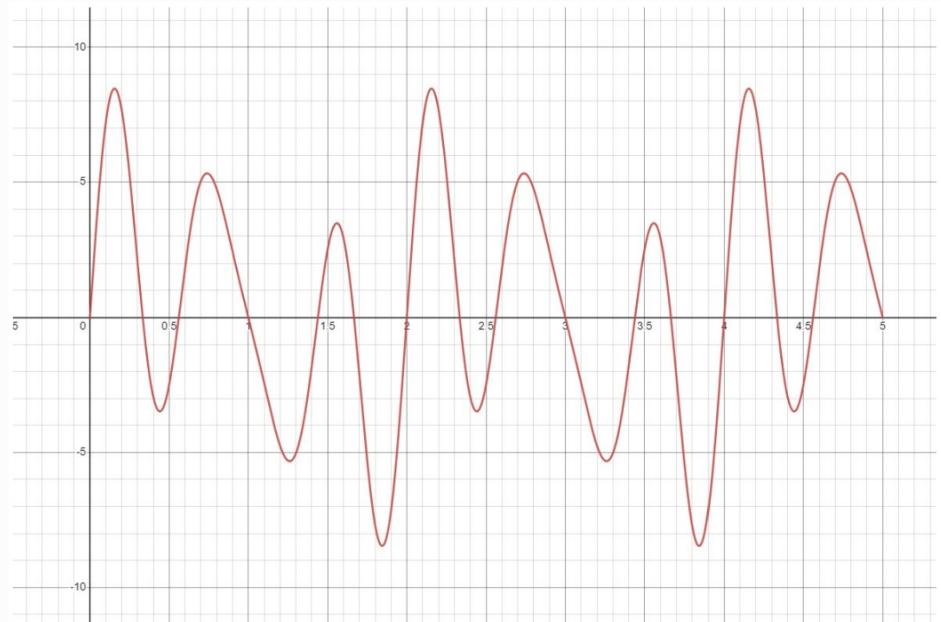


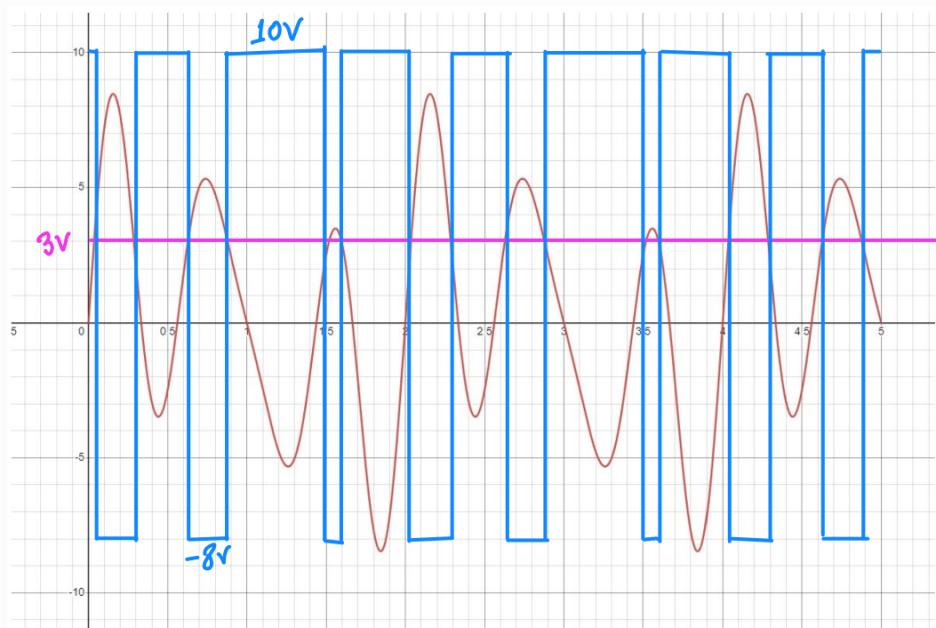first draw the 3V, V_{ref} on the graph. Also notice V_{ref} is now V^+ and so we adapt accordingly —




This might feel a bit hard to understand at first but with practice it will become easier for you.

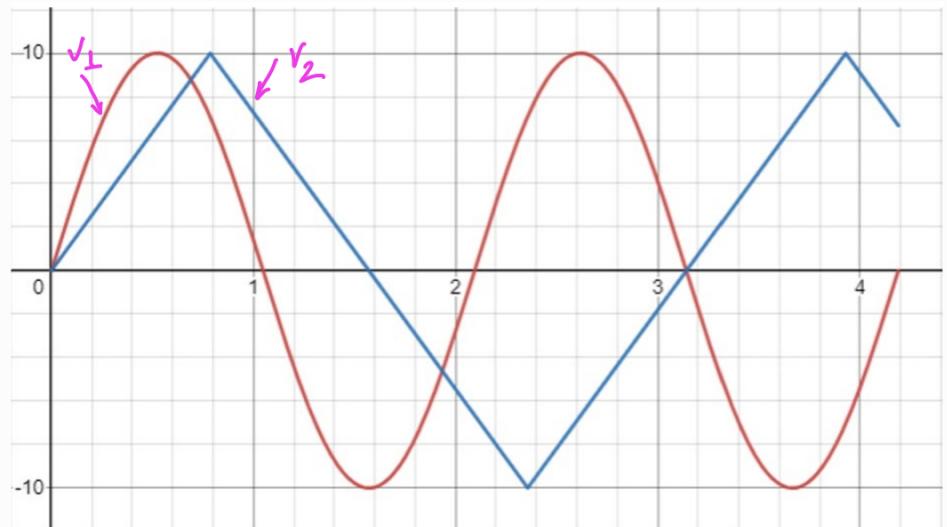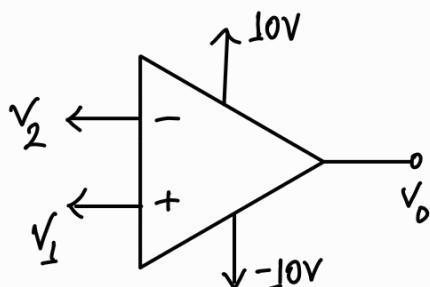Now let's make v_{ref} an AC signal as well —



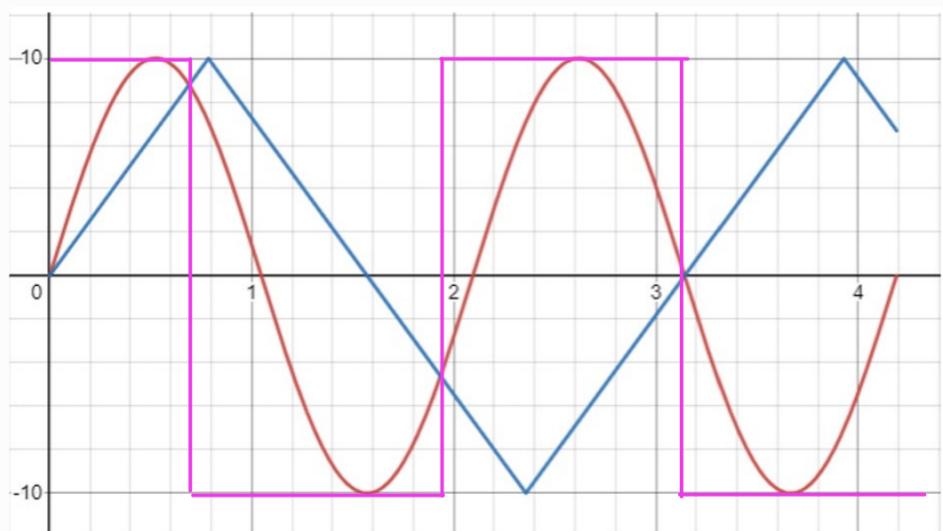
v_1 is the v^+ . So to draw the output just check when v_1 is greater than v_2 . In such cases $v_0 = 10V$ and in other cases $v_0 = -10V$



red $\rightarrow v_1 \rightarrow v^+$
blue $\rightarrow v_2 \rightarrow v^-$

Graph-based comparator problems will not be harder than this.




One concept that maybe tested —

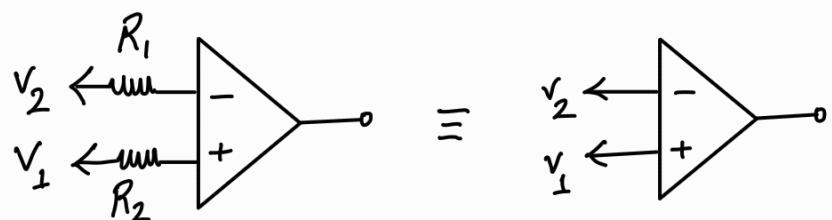

Proof —

Remember how $R_{in} = \infty$ for ideal op-amps?

∴

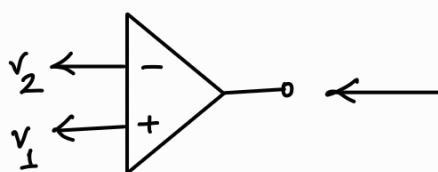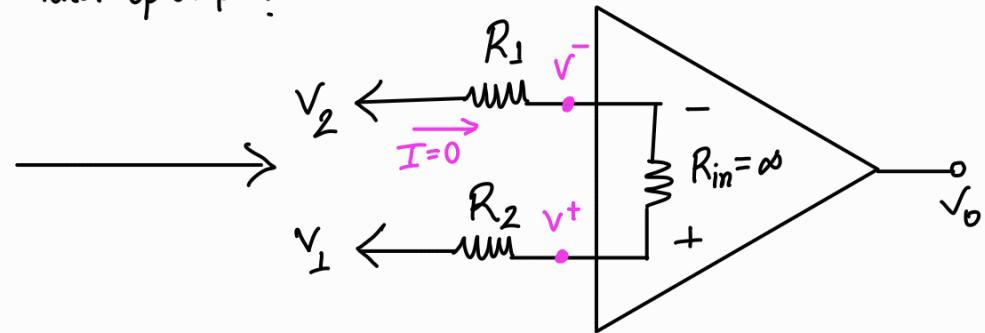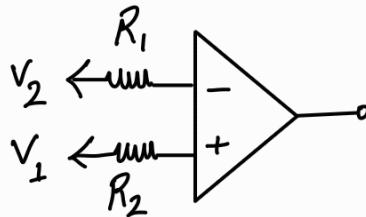


$$V^- = V_2 - 0V$$

$$= V_2$$


$$\& \quad V^+ = V_1 + 0V$$

$$= V_1$$

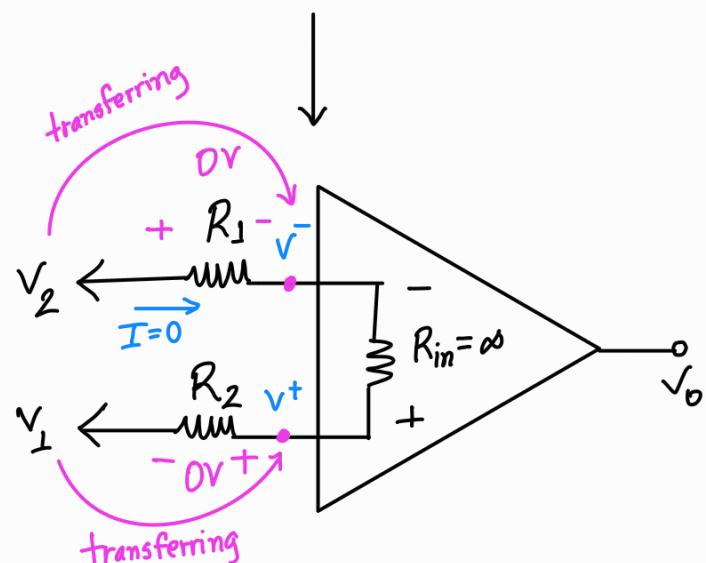


Terminologies regarding comparators —

non-inverting comparator

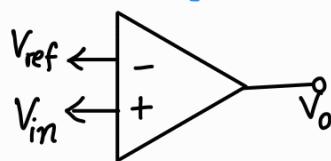


When V_{in} is connected to
non-inverting terminal

inverting comparator

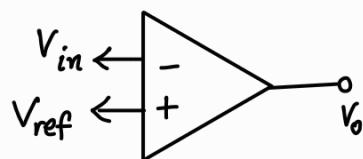

When V_{in} is connected to
inverting terminal

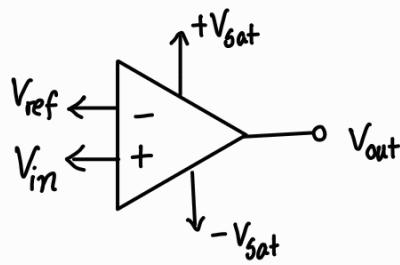Finally, the last topic from open loop configs — VTC of a comparator





for non-inverting comparator —

when $V_{in} < V_{ref} \rightarrow V_{out} = -V_{sat}$

when $V_{in} = V_{ref} \rightarrow V_{out} = 0$

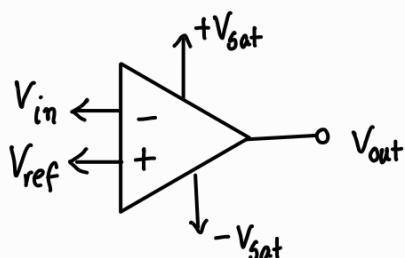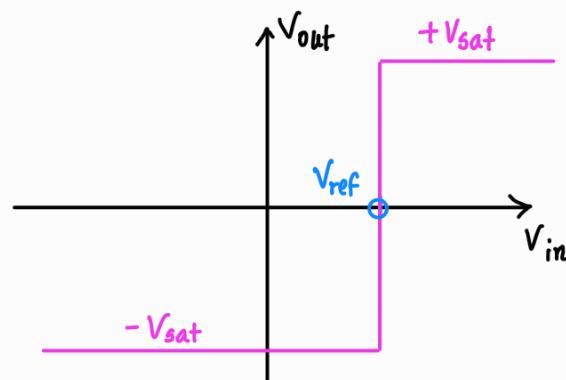when $V_{in} > V_{ref} \rightarrow V_{out} = +V_{sat}$




for non-inverting comparator —

when $V_{in} < V_{ref} \rightarrow V_{out} = +V_{sat}$


when $V_{in} = V_{ref} \rightarrow V_{out} = 0$

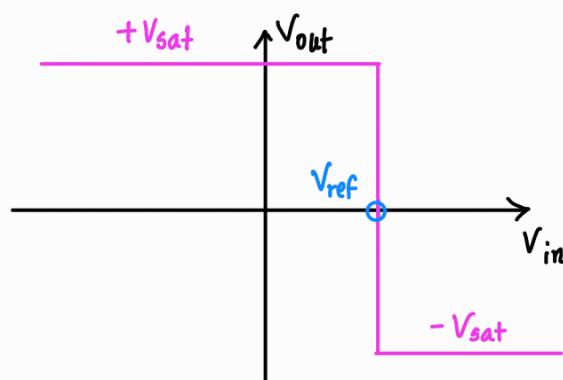when $V_{in} > V_{ref} \rightarrow V_{out} = -V_{sat}$




One final example (rare) —

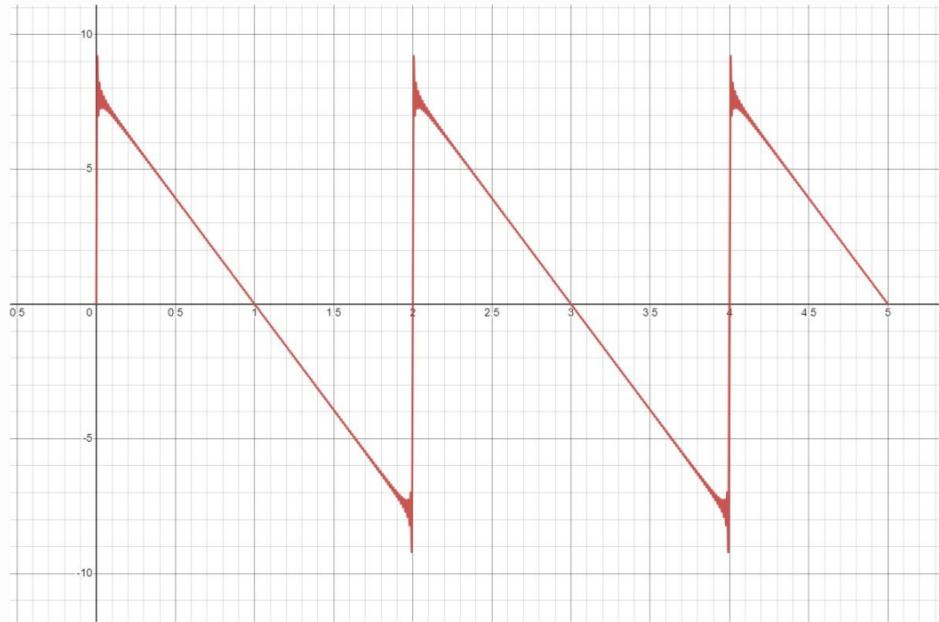for an inverting op-amp comparator, $V_{ref} = 1V$. If V_{in} is provided in the graph below, draw the V_{out} . $[+V_{sat} = 10V, -V_{sat} = -10V]$



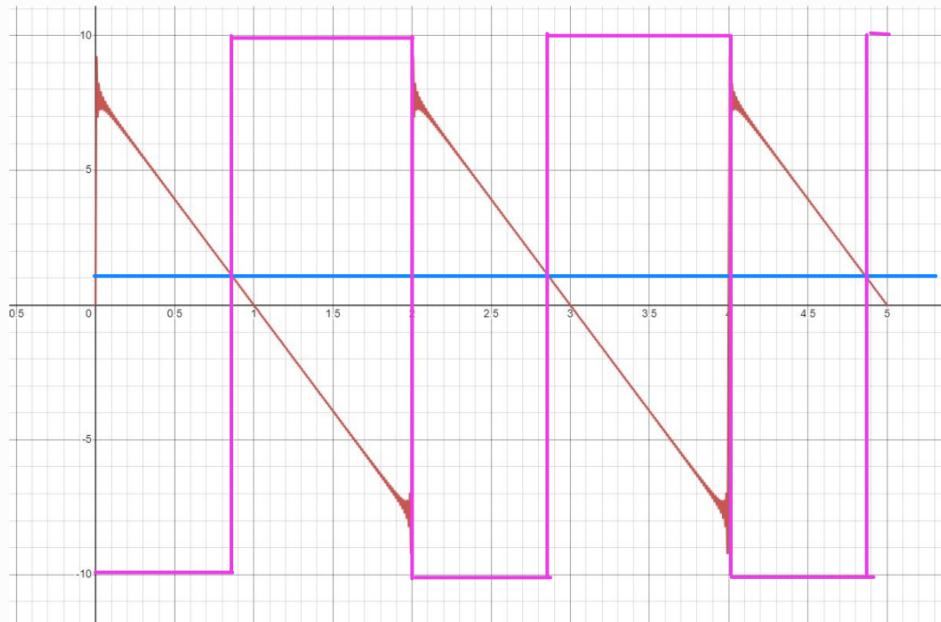Since the comparator is inverting in nature, $V_{in} = V^-$. So the V_{out} —



final note — even if it isn't mentioned in the question that the op-amp is ideal in nature, for comparators, always consider ideal op-amps.